

# Design Guide for AHB Circuit With Controller NV9801

## Table of contents

1.	Introduction .....	2
2.	Product Highlights .....	3
3.	AHB Circuit Operation Principle .....	4
3.1	AHB Topology Operating Mode .....	4
4.	NV9801 Peripheral Circuit Design.....	6
4.1	Pin Configuration .....	6
4.2	Peripheral Circuit Design.....	7
5.	AHB Main Circuit Design .....	14
5.1	Design Tool Introduction.....	14
5.2	140W AHB Design Example .....	15
6.	PCB Layout Guideline.....	19

## 1. Introduction

NV9801 is an Asymmetrical Half-Bridge (AHB) flyback controller that can implement high-efficiency and high-density AC/DC power supplies.

The whole control strategy contains four operation modes, namely ZSM/VSM/DCM/Burst mode, to achieve better conversion efficiency in each load segment.

When the system works under heavy load, NV9801 realizes zero-voltage turn-on of the main FET by adaptively controlling the conduction width of the auxiliary FET.

As the load decreases, NV9801 works in VSM mode. In this mode, the current magnetizing inductor is discontinuous. By the unique valley turn-on control, NV9801 can minimize the switching loss.

As the load decreases further, NV9801 will enter DCM mode. In this mode, the chip only retains valley turn-on control due to the very low switching frequency.

If the output load is extremely light, the chip will enter burst mode. In this mode, most of the block circuits of NV9801 are disabled to save quiescent current and thus reduce the standby power loss of the system.

Together with GaNSense™ technology (loss-less current sensing), NV9801 provides higher system reliability and better system efficiency.

## 2. Product Highlights

### Operation Mode

- Zero-voltage switch mode (ZSM) at heavy load
- Valley-voltage switch mode (VSM) at middle load
- Discontinuous conduction mode (DCM) at light load
- Burst mode at extremely light load/standby operation

### Power Supply

- Built-in high voltage start-up function
- Integrated Boost power supply for VCC
- Integrated LDO for half-bridge
- Integrated power switch for PFC stage power supply

### Key Features


- X-Capacitor discharge
- PFC enable/disable control
- Built-in Main FET soft start
- Resonant valley lock in VSM mode
- Peak current jitter for better EMI performance
- Programmable resonant period
- Slope compensation during high duty-cycle switching
- High switching frequency up to 1MHz

### Protection


- Brown-in/out
- CS pin open/short protection
- Output overload protection
- Output OVP/UVP
- Auxiliary FET  $I_{SAT}$  protection
- Programmable external over-temperature protection
- Short-circuit protection

### Package

- SOP14

 

**Fig. 1: Package SOP14**

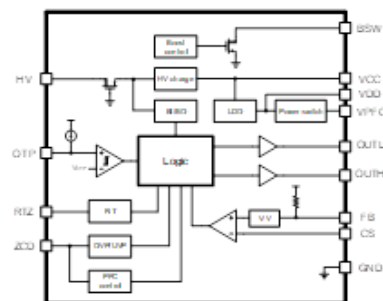

**Fig. 2: Simplified schematics**

### 3. AHB Circuit Operation Principle

#### 3.1 AHB Topology Operating Mode

 


Fig. 3: working mode1

 


Fig. 4: working mode2

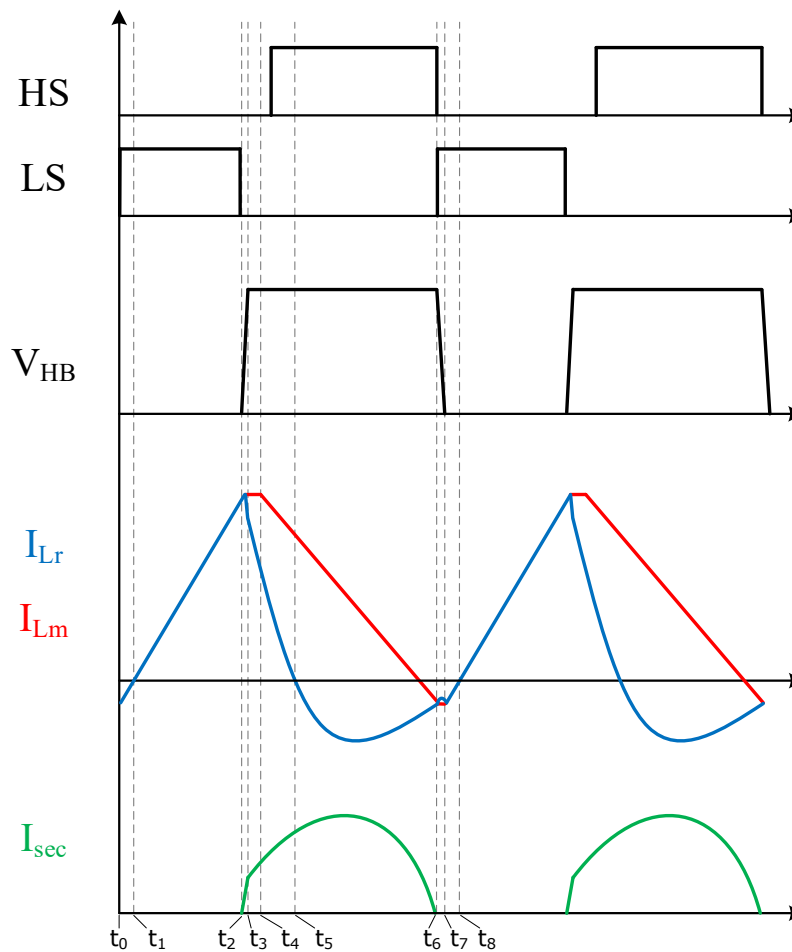


Fig. 5: working waveform

[1] Due to the volt-second balance of  $L_m$ :

$$\frac{1}{T} \int_0^T v_{Lm} dt = 0$$

So we could obtain:

$$\frac{V_{in} - V_{cr}}{L_m + L_r} DT = \frac{V_{cr}}{L_m + L_r} (1 - D)T \Rightarrow:$$

$$v_{cr} = DV_{in}$$

When S1 turn on and  $L_m \gg L_r$ :

$$V_{out} = \frac{L_m}{L_m + L_r} \frac{v_{cr}}{n} \approx \frac{v_{cr}}{n}$$

So we could obtain the gain equation for  $V_{in}$  and  $V_{out}$ :

$$V_{out} = \frac{DV_{in}}{n}$$

[2] Due to the ampere-second balance of  $C_r$ :

$$\frac{1}{T} \int_0^T i_{Cr} dt = 0$$

So, we could obtain:

$$\frac{1}{T} \int_0^T i_{Lm} - \frac{i_{sr}}{n} dt = 0 \Rightarrow:$$

$$\int_0^T i_{Lm} dt = \int_0^T \frac{i_{sr}}{n} dt$$


$$I_{Lm\_av} = \frac{1}{T} \int_0^T i_{Lm} dt = \frac{1}{T} \int_0^T \frac{i_{sr}}{n} dt = \frac{I_{out}}{n}$$

So, we could obtain the average current equation between  $I_{Lm}$  and  $I_{out}$ :

$$I_{out} = n \frac{I_{Lm\_max} + I_{Lm\_min}}{2}$$

## 4. NV9801 Peripheral Circuit Design

### 4.1 Pin Configuration

 

**Fig. 6: NV9801 pinout**

Pin		I/O	Description
Number	Symbol		
1	HV	P	High voltage start-up pin for the IC. It also implements X-cap discharge and BI/BO functions at the same time.
2	NC		No connection.
3	OTP	I/O	External temperature sensing pin. Connecting an NTC resistor in series with a normal resistor to this pin to set the appropriate temperature protection threshold. It also determines the selection of high/low frequency applications.
4	RTZ	I/O	Set the resonant period of SW node. Also, it can set dead time from OUTH turn off to OUTL turn on at the same time.
5	ZCD	I/O	Auxiliary winding voltage sensing pin. It has multiple functions, such as OVP/UVF protection, PFC boost control, etc. Also, it decides when to turn off OUTH at the same time.
6	FB	I/O	Feedback voltage from opto-coupler connected pin. The voltage is used to implement whole control loop and operation mode switching.
7	GND	G	Ground pin.
8	CS	I	Current sensing pin. Connecting to the sensing resistor of the transformer to implement peak current mode control loop.
9	OUTL	I/O	Main FET driving signal output pin. Besides, it combines OUTH ISAT protection at the same time.
10	OUTH	O	Auxiliary FET driving signal output pin.
11	VPFC	P	PFC boost power supply.
12	VDD	P	LDO output pin for half bridge driver IC power supply.
13	VCC	P	Power supply pin for IC.
14	BSW	P	Switching node voltage input pin of the Boost power supply circuit.

(1) I=Input, O=Output, P=Power, G=Ground

The schematic diagram illustrates a 100W LED driver circuit. It begins with an AC Line input, which is connected to a bridge rectifier. The rectified output is filtered by a capacitor and then passes through an inductor to the DC INPUT of the NV6247C controller. The DC INPUT is also connected to a DC-DC converter stage, which includes a transformer and a diode bridge. The output of the DC-DC converter is connected to the SR Controller, which in turn drives the LED load through a series of resistors and a TL431 voltage divider. The NV6247C controller is configured with various pins: HV, NC, OTP, RTZ, ZCD, FB, GND, BSW, VCC, VDD, VPFC, OUTH, OUTL, and CS. The circuit also includes a PFC BOOST section and a feedback network for the LED current regulation.


Figure 1: Schematic diagram of the HV supply circuit. The circuit starts with an AC Line connected to a transformer. The secondary of the transformer is connected to a bridge rectifier. The positive output of the rectifier is connected to a resistor  $R_{HV1}$ , which is then connected to a diode. The other end of the diode is connected to a resistor  $R_{HV2}$ , which is finally connected to the HV pin of the IC. The IC pinout is shown on the right: HV, NC, OTP, RTZ, ZCD, FB, GND, BSW, VCC, VDD, VPFC, OUTH, OUTL, CS.

- p7 of 20

$I_{HV\_BI}$	HV Current Threshold for Brown in	1.1	1.17	1.25	mA	
$I_{HV\_BO}$	HV Current Threshold for Brown out	0.92	1	1.08	mA	
$T_{DEB\_BO}$	Debounce Time for Brown-Out	36	40	44	ms	

- 2) Brown-in setting voltage:  $V_{BI}=1.17mA*(R_{HV1}+ R_{HV2})$   
Brown-out setting voltage:  $V_{BO}=1.0mA*(R_{HV1}+ R_{HV2})$
- 3) BI condition: Detect  $I_{HV}$  every 2 ms until  $I_{HV}>1.17mA$  is detected
- 4) BO condition: Detect  $I_{HV}<1mA$  and debounce for 40ms

## 2. OTP Pin

 

- 1) Function: External temperature sensing pin. And it combines the selection of high/low frequency applications.
- 2) NV9801 OTP pin provides 60μA current
- 3) Trigger OTP:  $V_{otp}$  is below 0.55V for 100μs
- 4) Use  $C_{otp}$  to set low frequency or high frequency  
If  $F_{sw}>300kHz$ , it needs to place  $C_{otp}$  and  $C_{otp} > 2.2nF$   
If  $F_{sw}<300kHz$ ,  $C_{otp}$  is not required

## 3. RTZ Pin

- 1) Function: RTZ pin is used to set a reference time referring to the resonant time after ILM cross zero. and Also, it can set dead time from OUTH turn off to OUTL turn on at the same time.
- 2) The larger is the RTZ, the smaller the  $I_{neg}$  will be.




The smaller is the RTZ, the greater the Ineg will be.

- 3) For low frequency application;  $R_{tz} = T_{ring}/5 \cdot 0.8$  to achieve good ZVS result.

For high frequency application;  $R_{tz} = T_{ring}/5$  to avoid larger Ineg.

$T_{ring}$ : the resonance period of Lm and equivalent capacitance

#### 4. ZCD PIN – Output ovp

 


- 1) Function: ZCD pin can be used to detect Output OVP.

When NV9801 starts to detect OVP, Rzcd\_L will be shorted to GND. And it will detect the Iovp through Rzcd\_H

$$V_{OUT\_OVP} = 500\mu A \times R_{zcd\_H} \cdot \frac{N_s}{N_A}$$

- 2) Trigger condition: 3 cycles to trigger during the on-time of OUTH

#### 5. ZCD PIN – Output uvp and PFC EN

 

- 1) Function: ZCD pin can be used to detect Output UVP and enable PFC stage.

When OUTL turns off, NV9801 starts to detect Vzcd

And If  $V_{zcd} < 0.25V$  for 3cycles, it will trigger UVP

And If  $V_{zcd} > 1V$  for 1cycle, it will immediately enable PFC. Once the PFC is triggered, it will be enabled for at least 200ms.

$$V_{OUT\_UVP} = 0.25 \times \frac{(R_{zcd\_H} + R_{zcd\_L}) \cdot N_S}{R_{zcd\_L} \cdot N_A}$$

$$PFC\ EN = 1 \times \frac{(R_{zcd\_H} + R_{zcd\_L}) \cdot N_S}{R_{zcd\_L} \cdot N_A} = 4V_{OUT\_UVP}$$


## 6. FB AND CS PIN

1) FB Rise, Burst  $\rightarrow$  DCM  $\rightarrow$  VSM  $\rightarrow$  ZVS


FB Fall, ZVS  $\rightarrow$  VSM  $\rightarrow$  DCM  $\rightarrow$  Burst

$V_{cs\_max} = 0.6V$   $FB\_max = 3.6V$  and if FB exceeds 3.6V for 80ms, it will trigger OLP protection

## 7. VCC、VDD、BSW and VPFC

 

1) Startup waveform

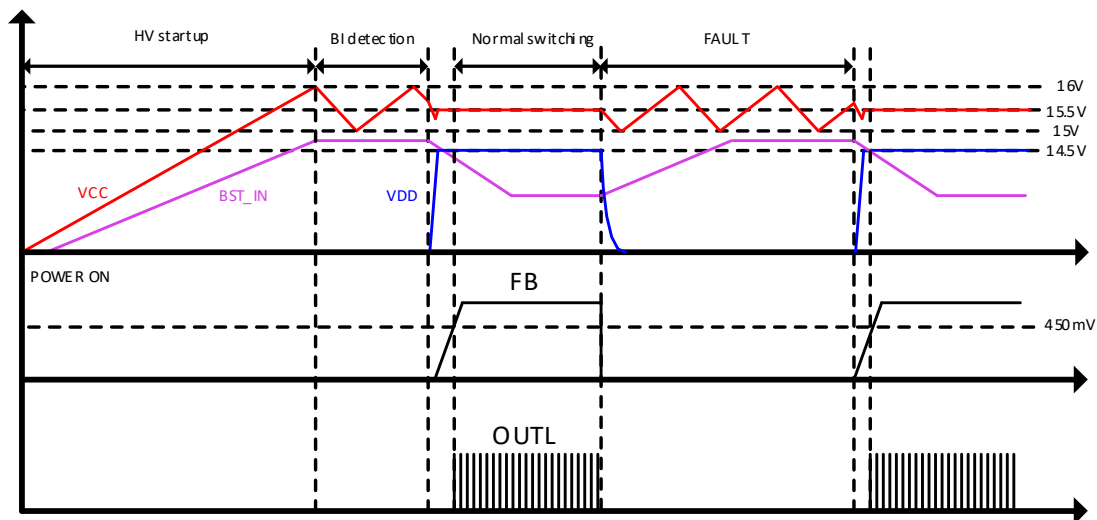

## 2) Maximum rating

$V_{BSW}$  and  $V_{CC}$  are 75V;  $V_{DD}$  and  $V_{PFC}$  are 20V

## 3) $V_{CC}$ , $V_{DD}$ and $V_{PFC}$

The typical  $V_{cc}$  is 16V when boost works. And the UVLO of  $V_{CC}$  is 10V. NV9801 integrated LDO and the typical  $V_{DD}$  voltage is 14.5V. the maximum load capability of LDO is 48mA. NV9801 integrated PFC control circuit and the typical  $V_{PFC}$  is 14.5V.

Tips for capacitance Relationship:

$$C_{VCC} > 4C_{VDD}$$

$$C_{VDD} > 4C_{V_{PFC}}$$

This can help keep  $V_{cc}$  and  $V_{DD}$  more stable.

## 4) Integrated Boost circuit

If  $V_{CC}$  voltage is below 15.5V, boost circuit will be enabled. The working frequency is 1.5MHz and peak current is 300mA. In burst mode, Boost circuit will enter LPM mode to improve efficiency.

a) LPM mode: peak current will be reduced from 300mA to 200mA.

b) LPM mode:  $f_{sw}$  will be reduced from 1.5MHz to 500kHz.

LPM mode: if boost- $V_{in}$  drops very low and triggers 500ns  $T_{ONMAX}$  for 5 consecutive cycles, the boost will stop operating and recover after the next OUTL pulse comes.



Tips 1.  $L_{boost}$  will affect the minimum  $V_{boost\_in}$

$$V_{boost\_in} = L_{boost} \frac{i_{boost}}{T_{on\_max}} = L_{boost} \frac{0.2}{0.5}$$

$L_{boost}=4.7\mu H$ , Minimum  $V_{boost\_in} = 1.9V$  during LPM


$L_{boost}=10\mu H$ , Minimum  $V_{boost\_in} = 4V$  during LPM

 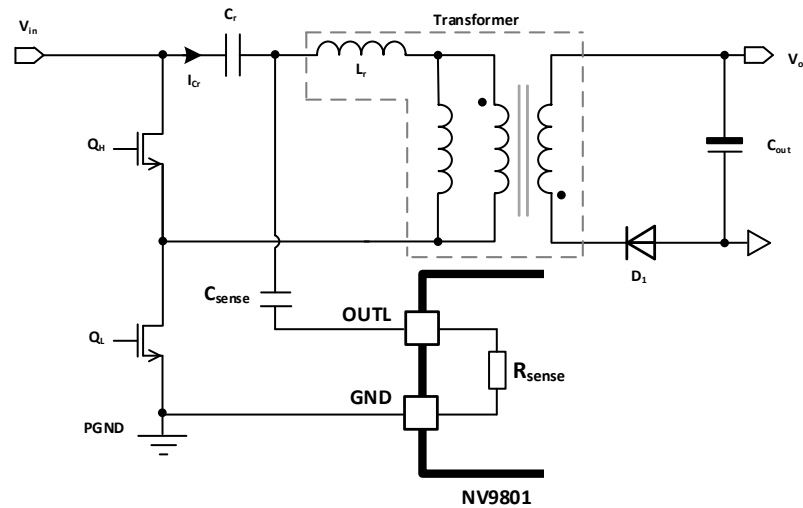Tips 2.  $N_a$ :  $N_s > 1.5$  to improve boost efficiency.



- [1] Function: OUTL is PWM signal of low-side switch and it combines ISAT-protection at the same time.
- [2] If it works in low frequency mode, the  $R_{sense}$  is 2k, if it works in high frequency mode, the  $R_{sense}$  is 1k.
- [3] I-sat protection enable condition:
  - 1) Startup and  $OUTL > 0.25$ .
  - 2)  $FB < 200mV$  debounce 5ms and  $OUTL > 0.25$ .
  - 3) Maximum discharge cycle:  $10 \times 7$ .

## 8. PFC EN CONTROL

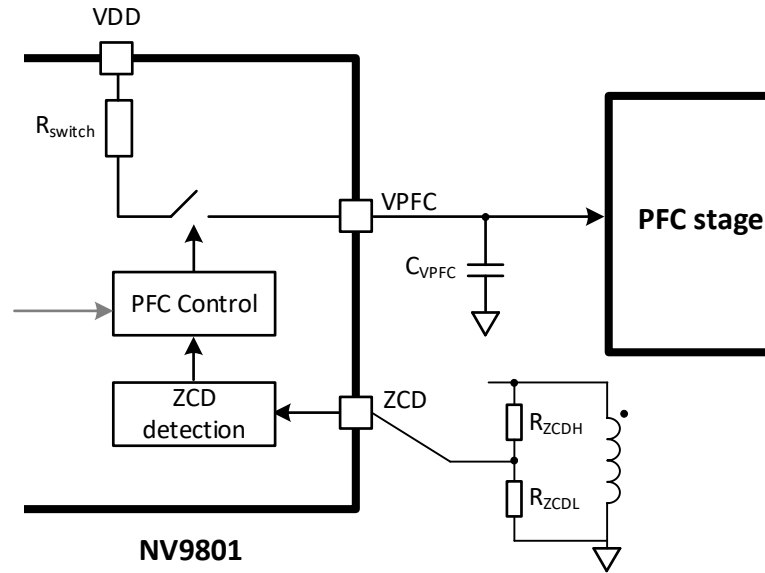

- 1) VPFC is used to supply external PFC stage.
- 2) PFC Enable condition:
  - a) In startup, PFC will be enabled for 200ms
  - b) In normal work, the PFC enable condition is  $V_{zcd} > 1V$
  - c) once PFC is enabled, PFC will debounce for 200ms.

## 5. AHB Main Circuit Design

### 5.1 Design Tool Introduction

Step.1 System Information Input			
VO_MAX	Max nominal output voltage	20	V
PO_MAX	Max nominal output power	100	W
VIN_MIN	Min input voltage	260	V
VIN_MAX	Max input voltage	400	V
VIN_selected	Select the input voltage	260	V
VDS_SR	Expected SR drain-to-source voltage rating	100	V
K_VDS_SR	SR drain-to-source voltage de-rating factor	0.85	
D_MAX	Max suggested duty cycle	0.7	
AE	Selected transformer AE	98	mm <sup>2</sup>
B_MAX	Designed max flux density	0.3	T
Coss_T	Total equivalent Coss of primary side	150	pF
Tring	Resonant period of SW node, Need to be adjusted according to Fre	1.6	μS
Td	Expected dead time from HS to LS @CRM	480	ns
C_SR	Total equivalent Cds of SR	2200	pF

Step.2: Parameters design of NV9801_INPUT			
Brown-in	Brown-in voltage/DC Voltage	100	V
Brown-out	Brown-out voltage/DC Voltage	85.47	V
Aux ratio_selected	turn ratio between Naxu and Ns/Naux:Ns	1.50	
Naux	Winding turns for Aux	6.00	Ts
Output OVP	OVP setting voltage	24	V
Output UVP	UVP setting voltage	2.5	V
PFC EN	The PFC enables setting voltage	10.00	V
I-sat Current	Max iLr current to trigger I-sat protection	10	A

INPUT	
OUTPUT	Selected

## 5.2 140W AHB Design Example

### Basic system information:

- 1) Maximum output power:140W
- 2) Output voltage:5V-28V Maximum output current:5A
- 3) Bus voltage:300V-400V
- 4) SR MOS: the breakdown voltage of SR is 100V
- 5) Maximum duty cycle:0.75
- 6) AHB TX core: ATQ23.7, JPP95, AE=100mm<sup>2</sup>
- 7) Bmax:0.3T
- 8) HB GaN: NV6257; CS ratio=3200; Coss<sub>eq</sub>=150pF
- 9) Brown-in setting voltage:100V (BO will be 85V)
- 10) Naux:Ns=1.5 (Np:Naux:Na=22:6:4)
- 11) Ovp setting voltage:33V
- 12) Uvp setting voltage:2.5V (PFC EN voltage will be 10V)
- 13) The target iLr current to trigger I-sat protection:10A
- 14) HB GaN: NV6257;CS ratio=3200;Coss<sub>eq</sub>=200pF

### System Calculation and parameters design

1. Calculate the maximum N<sub>ps</sub>:

$$N_{ps} \leq \frac{D_{max} \times V_{bus\_min}}{V_{out\_max}} = \frac{0.75 \times 300}{28} = 8$$

Calculate the minimum N<sub>ps</sub>:

$$N_{ps} \geq \frac{V_{bus\_max}}{k \times V_{SR}} = \frac{400}{0.85 \times 100} = 4.7$$

N<sub>ps</sub> is turn ratio between primary winding and secondary winding. In this case, N<sub>ps</sub> is chosen to be 5.5 to achieve better efficiency, and Ns is chosen to be 4, which is suitable for the ATQ23.7's bobbin.

So we can obtain the final turn ratio of AHB TX:

$$N_p: N_s = 22:4$$

2. Calculate the negative  $L_m$  current-- $i_{Lm\_neg}$ :

$$i_{Lm\_neg} = \frac{C_{oss\_eq} \times V_{bus\_max}}{T_{dead}} = \frac{400 \times 150 \times 10^{-12}}{450 \times 10^{-9}} = 0.13A$$

$$C_{oss\_eq} = 150pF; T_{dead} = 450ns$$

Calculate the peak  $L_m$  current-- $i_{Lm\_peak}$ :

$$i_{Lm\_peak} = \frac{2 \times I_{out}}{N_{ps} \times \delta} + i_{Lm\_neg} = \frac{2 \times 5}{5.5 \times 0.9} + 0.13 = 2.15A$$

&:The correction coefficient of dead time

3. Maximum allowed magnetic inductance-- $L_{m\_max}$

$$L_m \leq \frac{N_p \times A E \times B_{max}}{i_{Lm\_peak}} = \frac{22 \times 100 \times 0.3}{1.95} = 338\mu H$$

In this case,  $L_m$  is chosen to be 300 $\mu$ H.

4. Calculate the switching frequency:

$$T_{on\_HS} = \frac{L_m \times (i_{Lm\_peak} + i_{Lm\_neg})}{N_{ps} \times V_{out}} = \frac{300 \times (2.15 + 0.13)}{5.5 \times 28} = 4.44\mu s$$

$$T_{on\_LS} = \frac{L_m \times (i_{Lm\_peak} + i_{Lm\_neg})}{V_{bus} - N_{ps} \times V_{out}} = \frac{300 \times (2.15 + 0.13)}{400 - 5.5 \times 28} = 2.78\mu s$$

$$T_{sw} = T_{on\_HS} + T_{on\_LS} + T_{dead} = 4.44 + 2.78 + 0.45 = 7.67\mu s$$

$$F_{sw} = \frac{1}{T_{sw}} = 130kHz$$

5. Calculate the resonant capacitor:

$L_k = 3\mu H$  (the leakage inductance of TX, based on measured value)

$$T_{on\_LS} = \frac{(1.1 \times T_{on\_HS})^2}{4\pi^2 \times L_k} = \frac{1.21 \times 4.44^2}{3.14^2 \times 3} = 0.81\mu F$$

In this case,  $L_m$  is chosen to be 820 $\mu$ F.



6. Calculate the HV charge resistor:  $R_{HV1}$ ;  $R_{HV2}$

$$R_{HV1} = R_{HV2} = \frac{V_{brown\_in}}{I_{BI} \times 2} = \frac{100}{1.17 \times 2} = 42.7k\Omega$$

7. Calculate the upper divided resistor of ZCD pin:

$$R_{zcd\_H} = \frac{V_{ovp} \times N_{as}}{I_{ovp}} = \frac{33 \times 1.5}{0.5} = 99k\Omega$$

8. Calculate the lower divided resistor of ZCD pin:

$$R_{zcd\_L} = \frac{V_{zcd\_uvp} \times R_{zcd\_H}}{V_{uvp} \times N_{as} - V_{zcd\_uvp}} = \frac{0.25 \times 100}{2.5 \times 1.5 - 0.25} = 7.1k\Omega$$

9. Calculate the RT resistor of RTZ pin:

$$T_{ring} = 2\pi\sqrt{L_m C_{oss\_eq}} = 2 \times 3.14 \times \sqrt{300 \times 10^{-6} \times 200 \times 10^{-12}} = 1.54\mu s$$

$$R_{tz} = \frac{T_{ring} \times 1000}{5} \times 0.8 = 246k\Omega$$

10. Calculate the Rcs resistor of cs pin:

$$GaNsense\_ratio = 3200$$

$$R_{cs} = \frac{V_{cs\_limit} \times GaNsense\_ratio}{1.1 \times i_{Lpeak}} = \frac{0.6 \times 3200}{1.1 \times 2.15} = 811\Omega$$

11. Calculate the  $C_{sense}$  to trigger I-sat protection:


$$R_{cs} = \frac{0.25 \times C_r \times 2 \times 1.4}{I_{sat} \times R_{sense}} = \frac{0.25 \times 0.82 \times 2 \times 1.4}{10 \times 2000} \times 10^6 = 28.7pF$$

12. Cotp: Fsw<300kHz, we did not need to place Cotp and If the fsw exceeds 300kHz, we suggest placing 3.3nF Cotp.


In our 140W demo, the actual parameters are as follows:

AHB transformer	$L_m=300\mu\text{H}$ ; $N_p:N_a:N_s=22:6:4$
$C_r$	470nF/250V MLCC *4
RHV1、RHV2	43k $\Omega$
Rzcd_H	100 k $\Omega$
Rzcd_L	6.8 k $\Omega$
Rtz	250k $\Omega$
Rcs	820 $\Omega$
Csense	30pF/1000V

### Demo board working waveform

 

115Vac 28V5A

 


230Vac 28V5A

## 6. PCB Layout Guideline

Efficient PCB layout is critical for stable operation and EMI performance. In this chapter, we will give some layout suggestions and practical examples.

### PCB layout Tips:

 - 1) High frequency power loop should be as small as possible.
- 2)  $R_{zcd\_H}$  and  $R_{zcd\_L}$  should be close to NV9801.
- 3) External Boost inductor should be close to NV9801.
- 4) FB and CS signal should be kept away from switching node.
- 5) It is best to use single-point connection to improve loop-stability.



## Additional Information

DISCLAIMER Navitas Semiconductor (Navitas) reserves the right to modify the products and/or specifications described herein at any time and at Navitas' sole discretion. All information in this document, including descriptions of product features and performance, is subject to change without notice. Performance specifications and the operating parameters of the described products are determined in the independent state and are not guaranteed to perform the same way when installed in customer products. The information contained herein is provided without representation or warranty of any kind, whether express or implied. This document is presented only as a guide and does not convey any license under intellectual property rights of Navitas or any third parties. Navitas' products are not intended for use in applications involving extreme environmental conditions or in life support systems. [Terms and Conditions](#).

Navitas, GaNFast, GaNSense, GeneSiC, and the Navitas logo are trademarks or registered trademarks of Navitas Semiconductor and subsidiaries. All other brands, product names, and marks are or may be trademarks or registered trademarks used to identify products or services of their respective owners.

Copyright ©2024 Navitas Semiconductor. All rights reserved.

Contact: [info@navitassemi.com](mailto:info@navitassemi.com)

