

How to Improve Power Adapter Density?

Traditional Travel Adapter and Chargers





USB PD and Quick Charge



- Added power in USB PD and Quick Charge requires dramatically higher power density (>20 W/in³)
- Higher efficiency and lower power loss are required in high density adapters
- How to dramatically improve the power density?


ACF Enables ZVS and High Frequency Switching

Lossless snubber

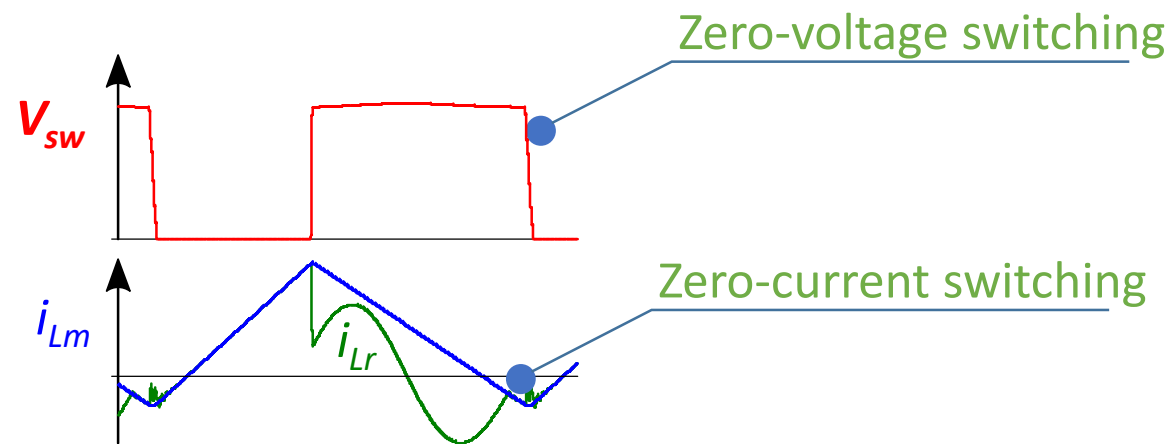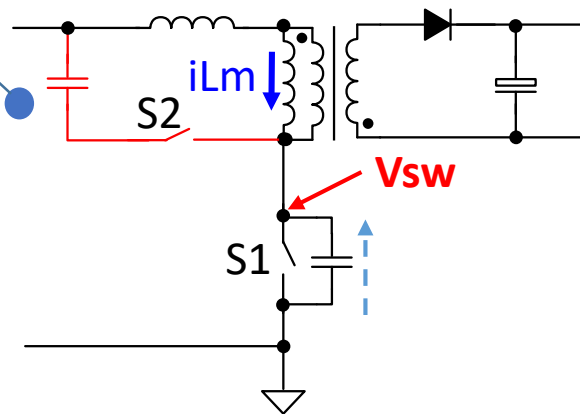

- No snubber losses, all leakage energy is recovered
- ZVS soft switching over entire operation range
- ZCS soft turn-off for output rectifier
- Clean waveforms reduce EMI
- Enable small adapter design with high-frequency switching


Towards Highly Efficient ACF

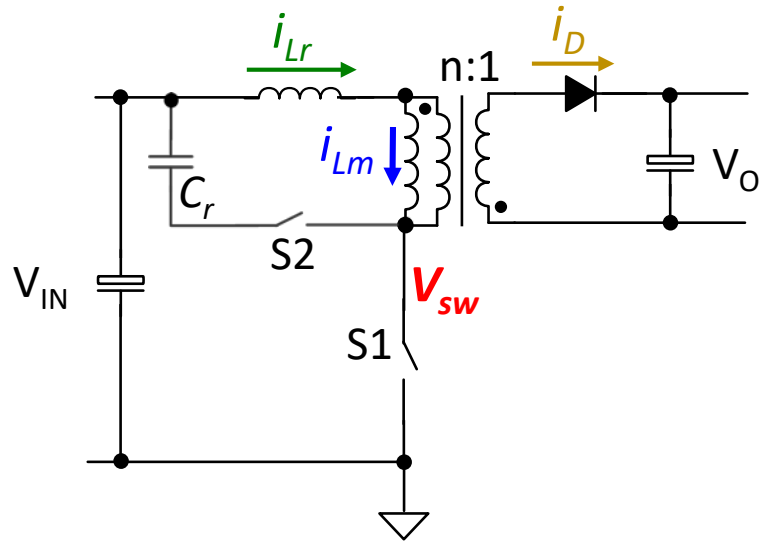

- Soft-switching is achieved, conduction loss dominates
- Circulating energy to the input source and clamping capacitor C_r , increasing current RMS
- Reduce both parts of circulating energy for highly efficient ACF

Energy from source

Energy circulated to source

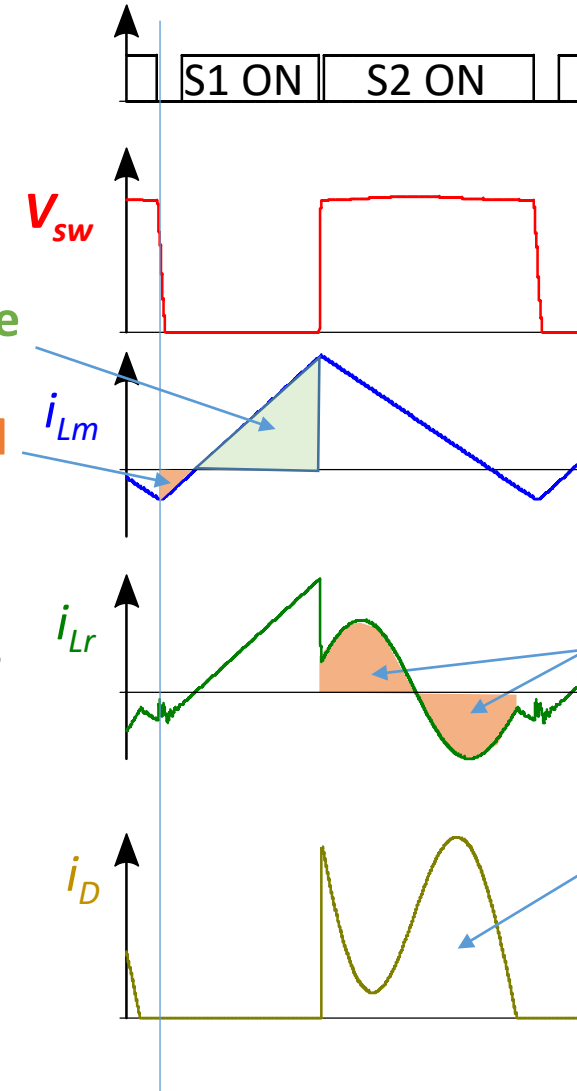

Energy circulated within C_r


Energy to load

Minimizing Energy Circulated Back to Source



- Minimize negative i_{Lm} for ZVS
 - → Depending on $C_o(tr)$
 - GaN has only $\frac{1}{2} C_o(tr)$ even with $\frac{1}{2} R_{DS(ON)}$
 - GaN needs less circulating energy

	IPA60R299CP	IPA60R385CP	NV6115
Voltage Rating (V)	650	650	650
$R_{DS(ON)}$	270	350	160
$C_o(tr)$ (pF)	120	96	50
Q_g (nC)	22	17	2.5
Q_{rr} (nC)	3900	3100	0

Energy circulated to source

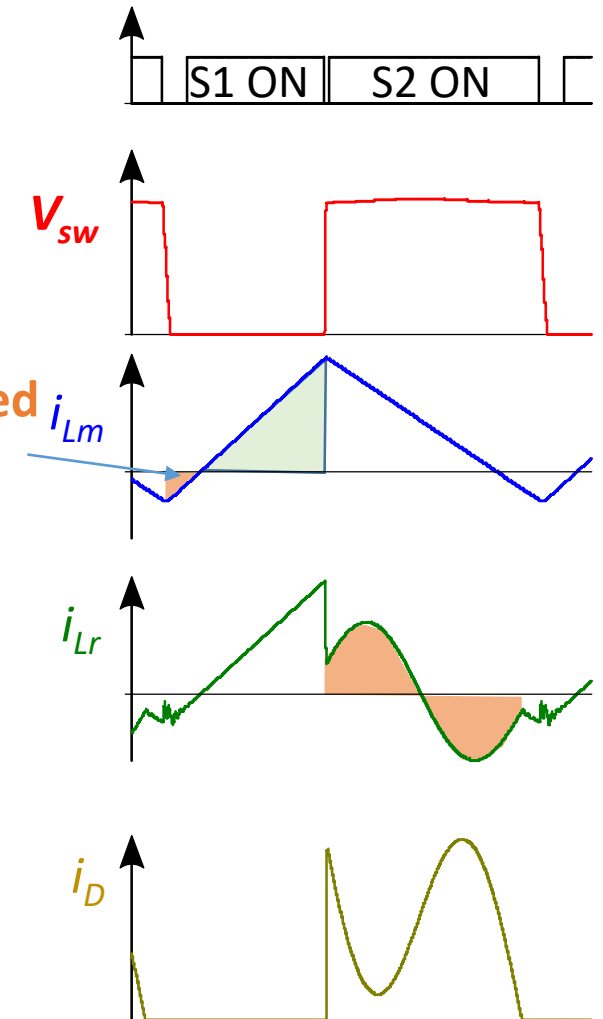


GaN ACF Minimized Negative i_{Lm}

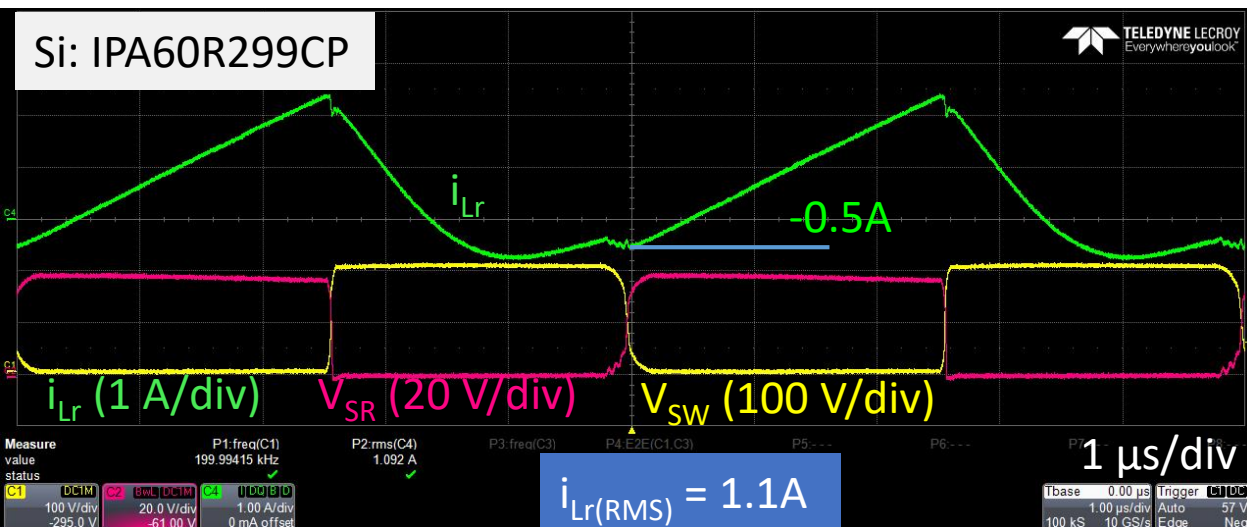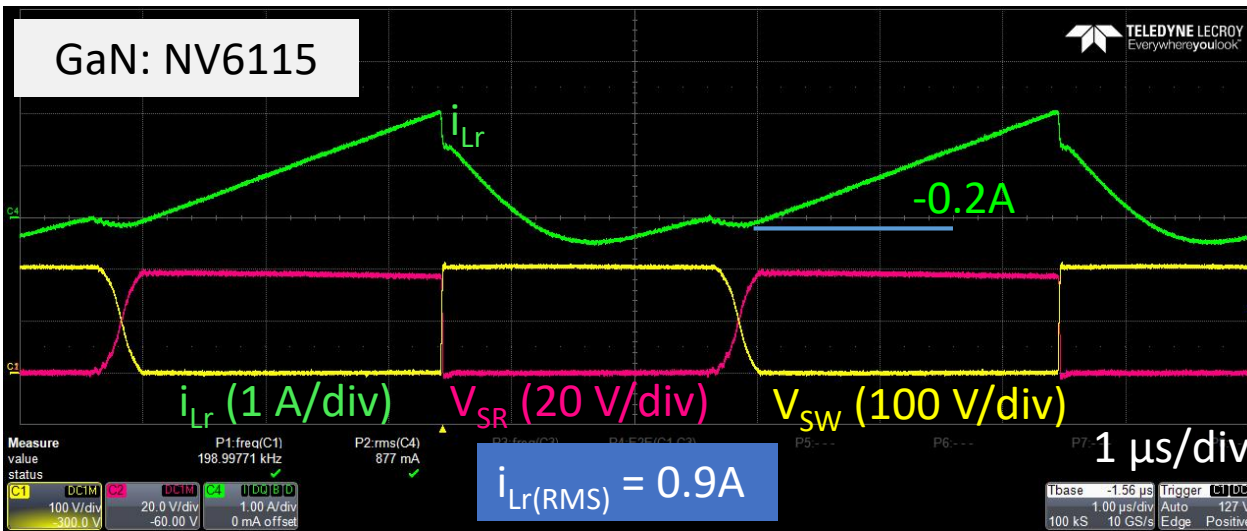

- GaN ACF needs only 0.2A negative current for ZVS vs. Si's 0.5A
- GaN ACF RMS is only 0.9A vs. Si's 1.1A
- Besides,
 - GaN has no body diode loss
 - Low high-frequency gate-charge loss




Minimizing Energy Circulated in Cr

- Minimizing the shaded area
- Two methods identified
 - Creating deeper current dip
 - Using secondary resonant scheme

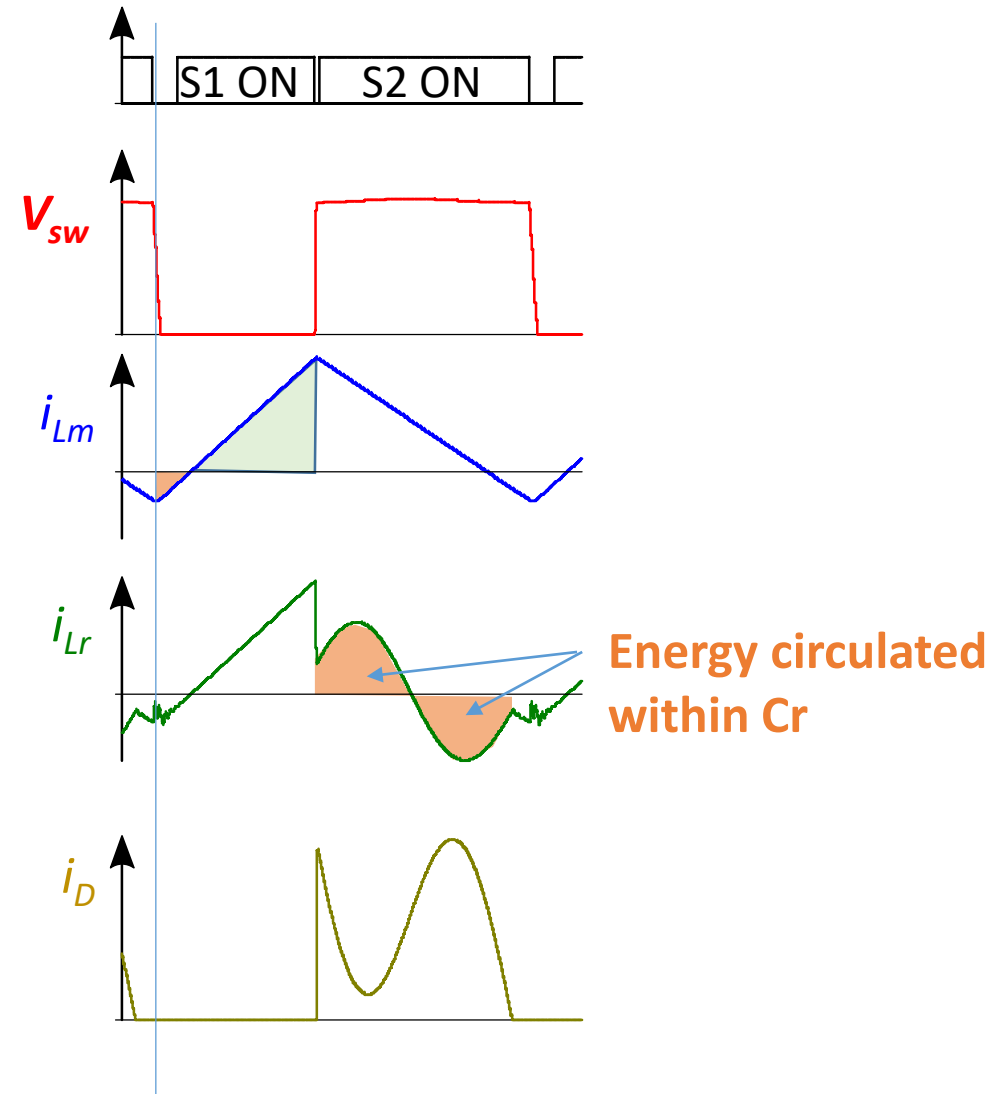


Method 1

GaN Increases Current Dip

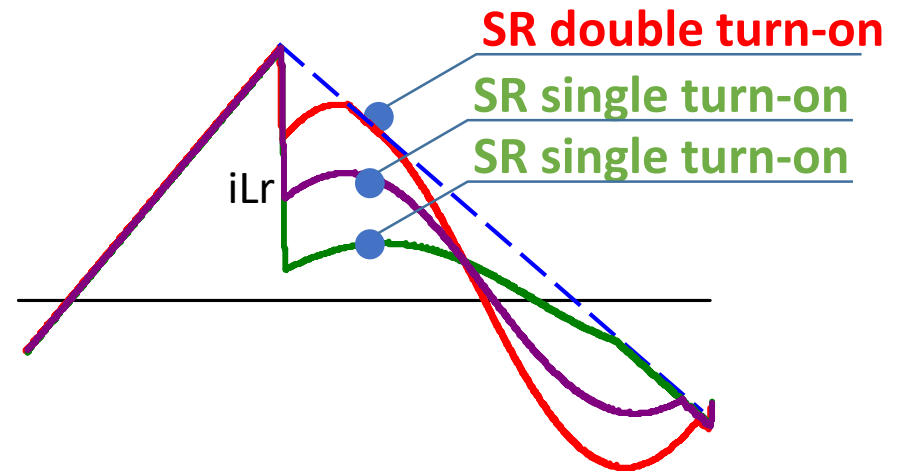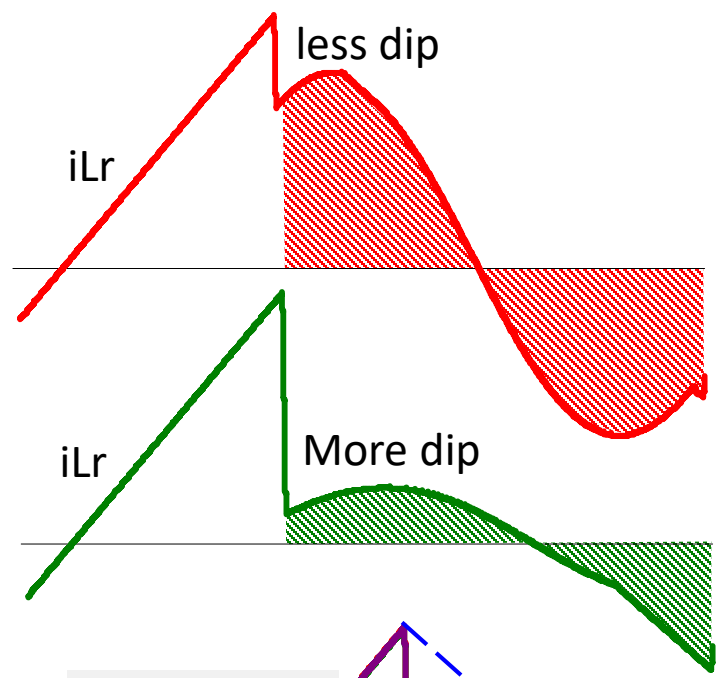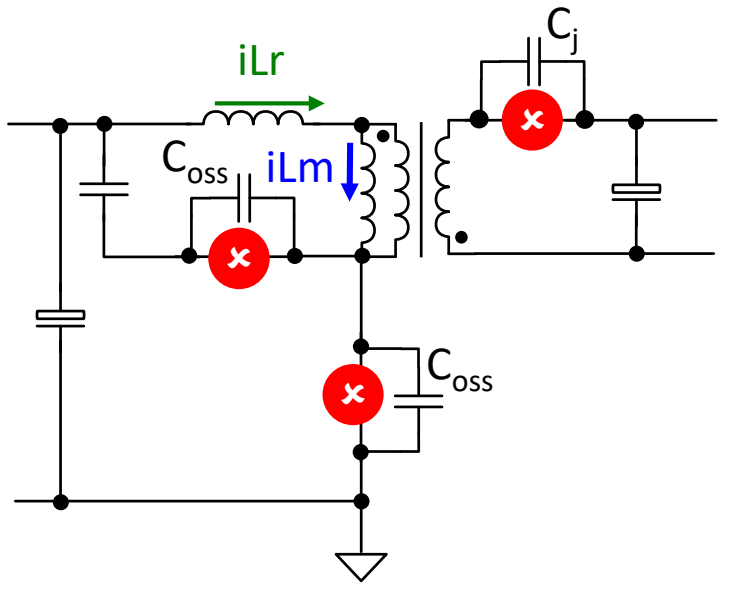

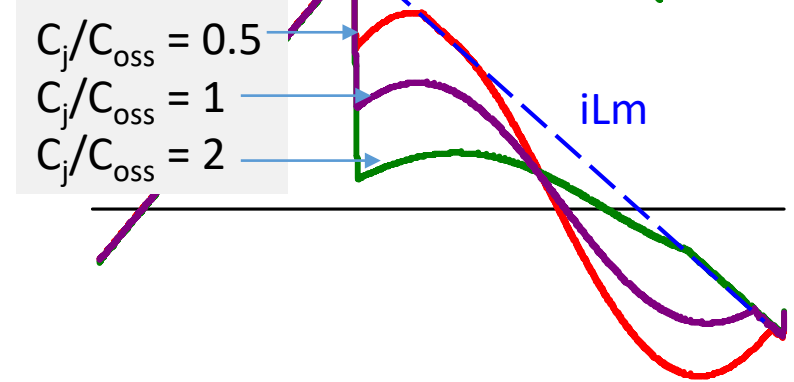
- Current dip \uparrow
- RMS value $i_{Lr(RMS)}$ \downarrow
 - Less SR double turn-on \downarrow




$C_j \uparrow$ \rightarrow Circulating Energy \uparrow

$C_{oss} \downarrow$ \rightarrow Use better device: GaN

Method 2 Secondary Resonance Scheme*

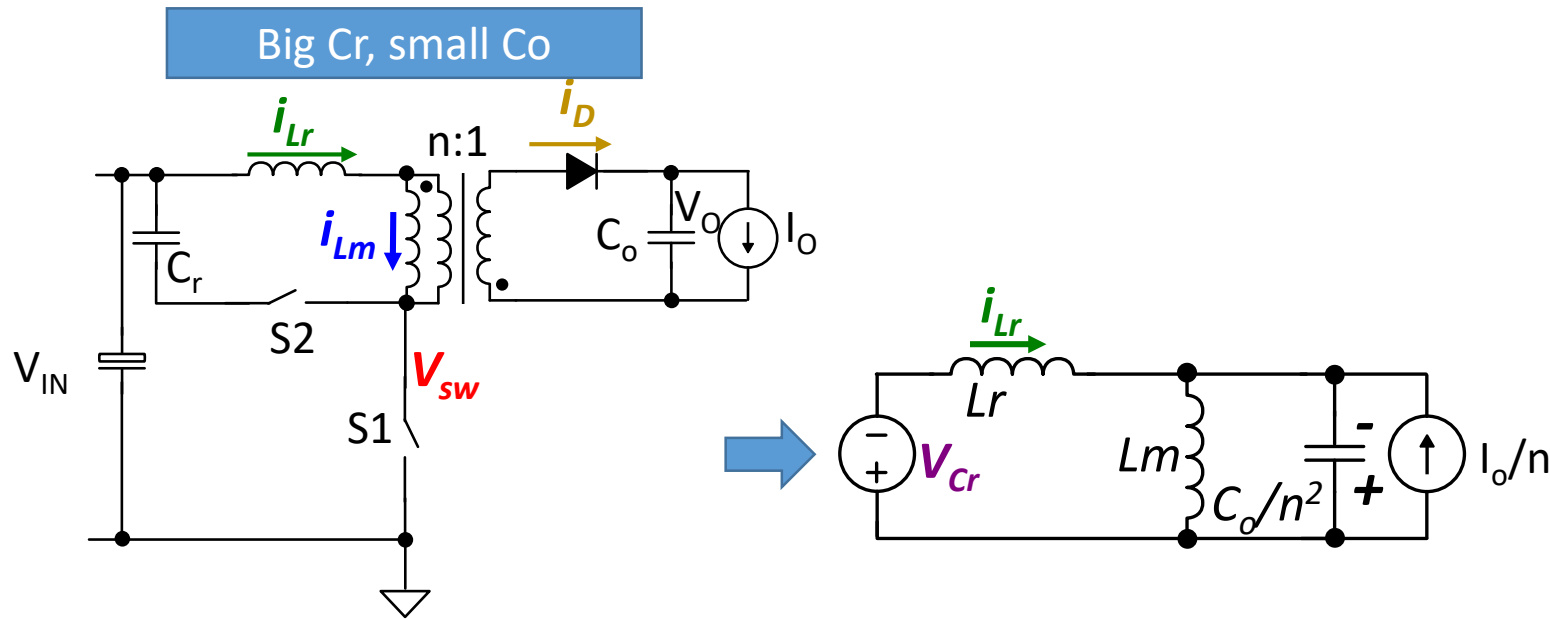




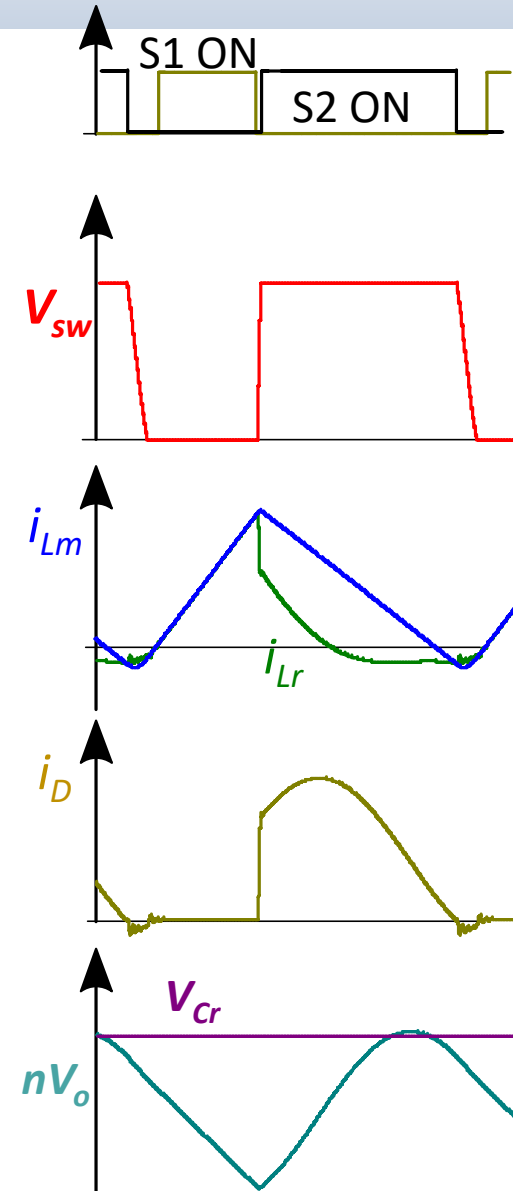
- Output capacitor to resonate with transformer leakage
- Clamping capacitor C_r has low voltage ripple
- More current pushed to the secondary side



*Navitas Patent Pending



Method 2

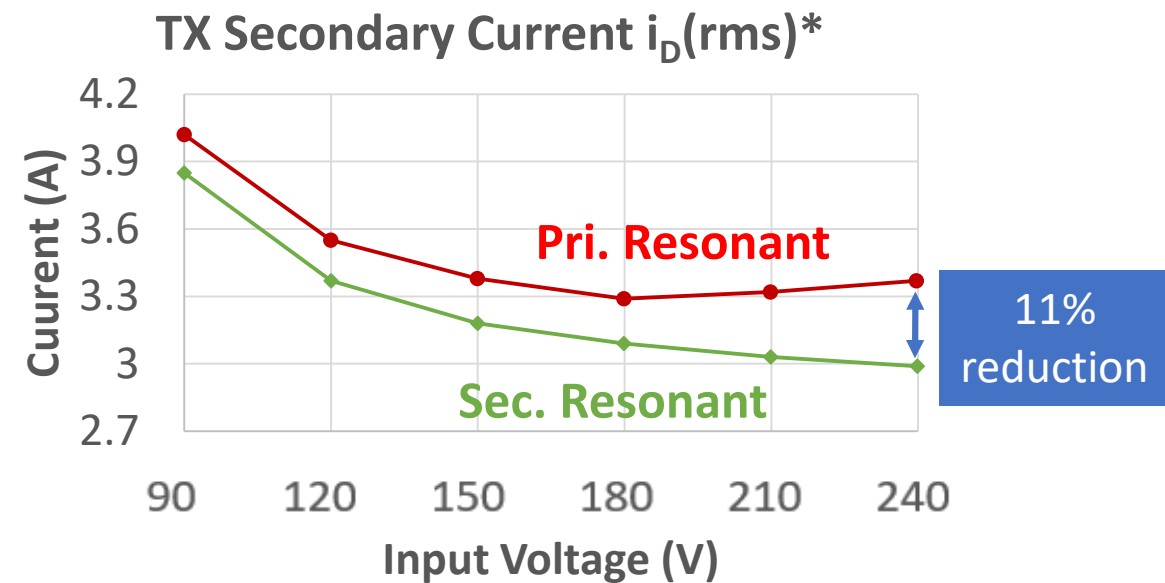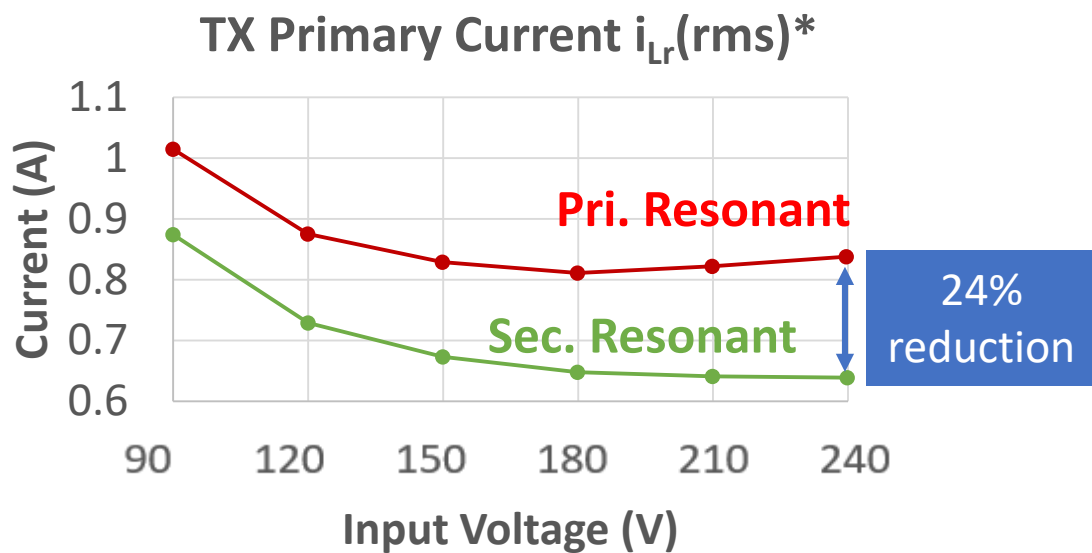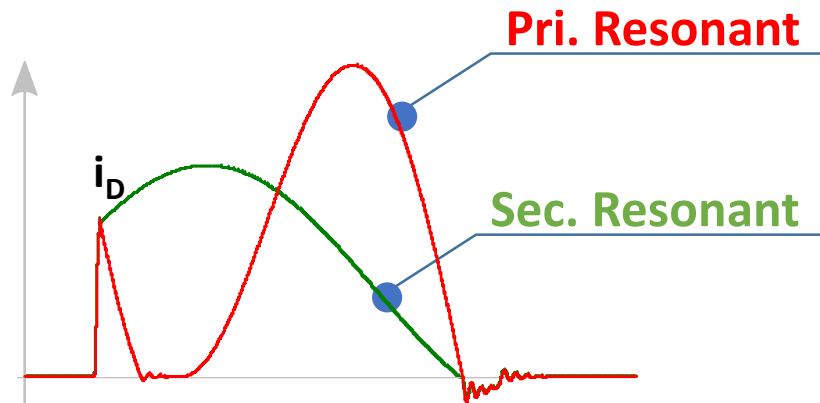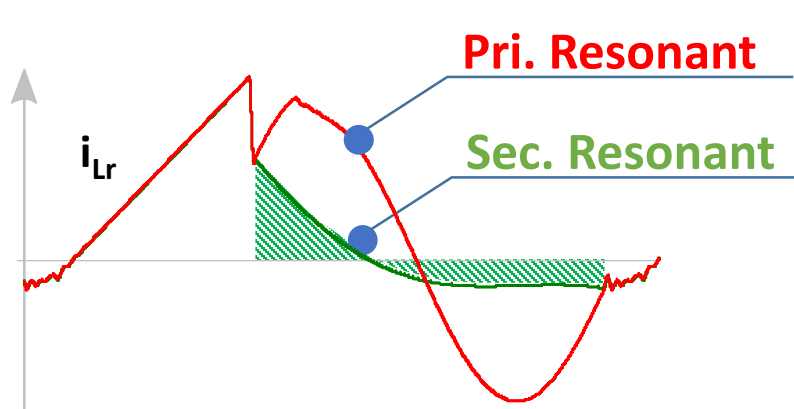Secondary Resonance Reduces Circulating Energy



*Measured results of 45W ACF


65W USB-PD ACF Using GaNFast™ Power ICs

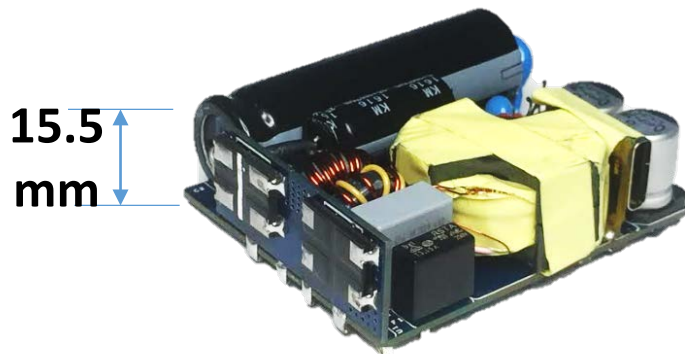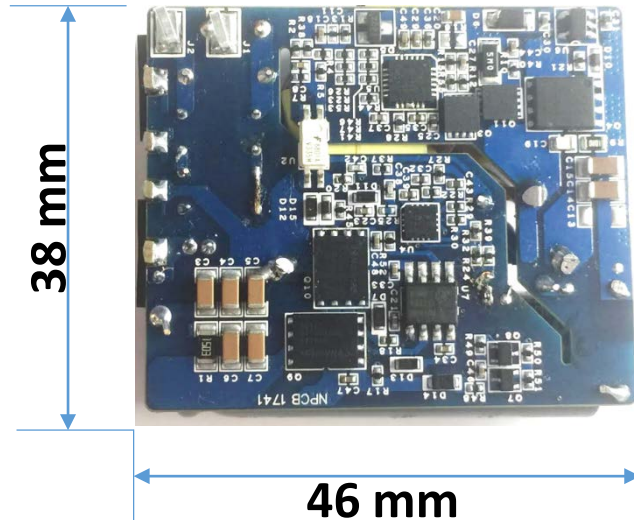


Input	Universal AC (85-265V _{AC} , 47-63Hz)
Output	Type C, USB-PD 2.0 (5-20V)
Frequency	250-350 kHz
Power Density	2.4 W/cc (39 W/in ³) uncased 1.5 W/cc (24 W/in ³) cased
Construction	4-layer, 2-oz Cu PCB, “No heatsink” design

Efficiency Meets CoC Tier 2 and DOE LV VI

Efficiency: 4-Points Average

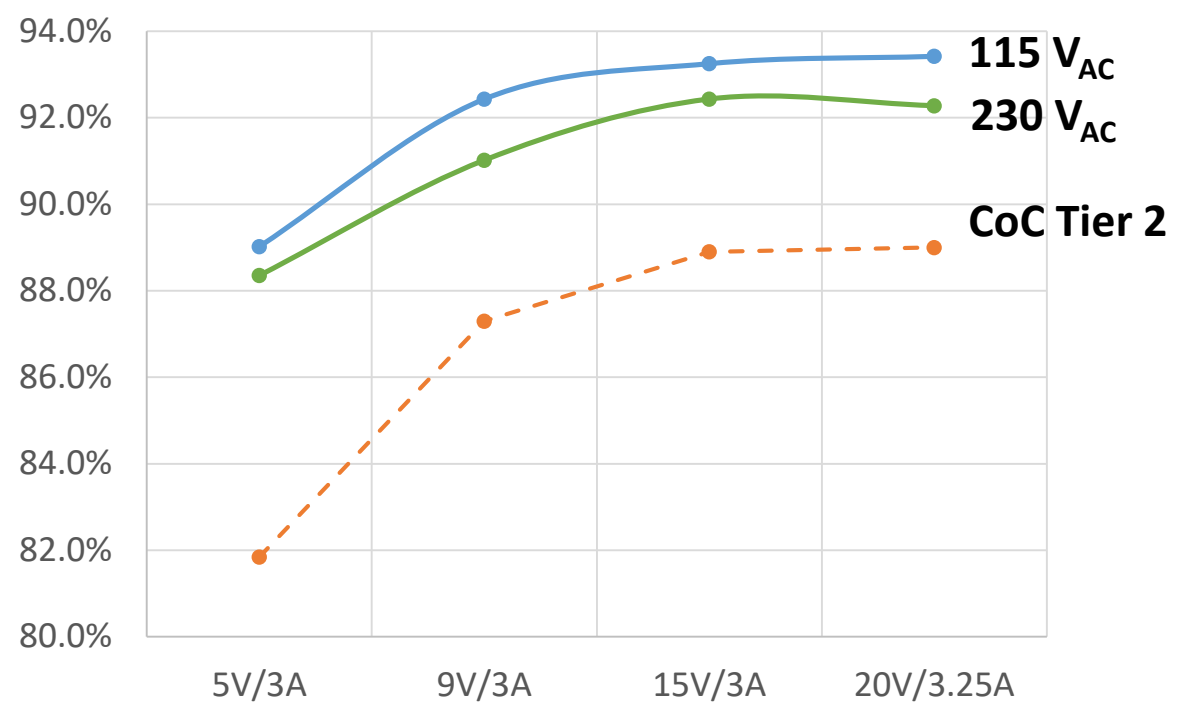


Efficiency: 10% Load

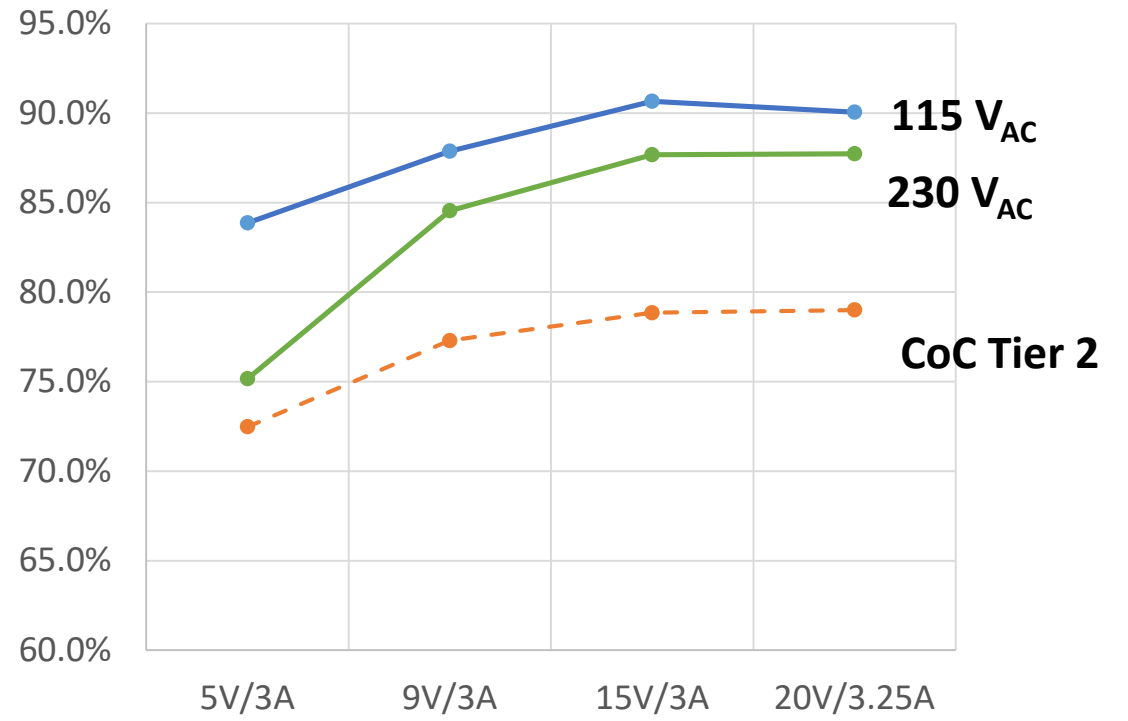


Integration Eases ACF Design




Powertrain ON/OFF

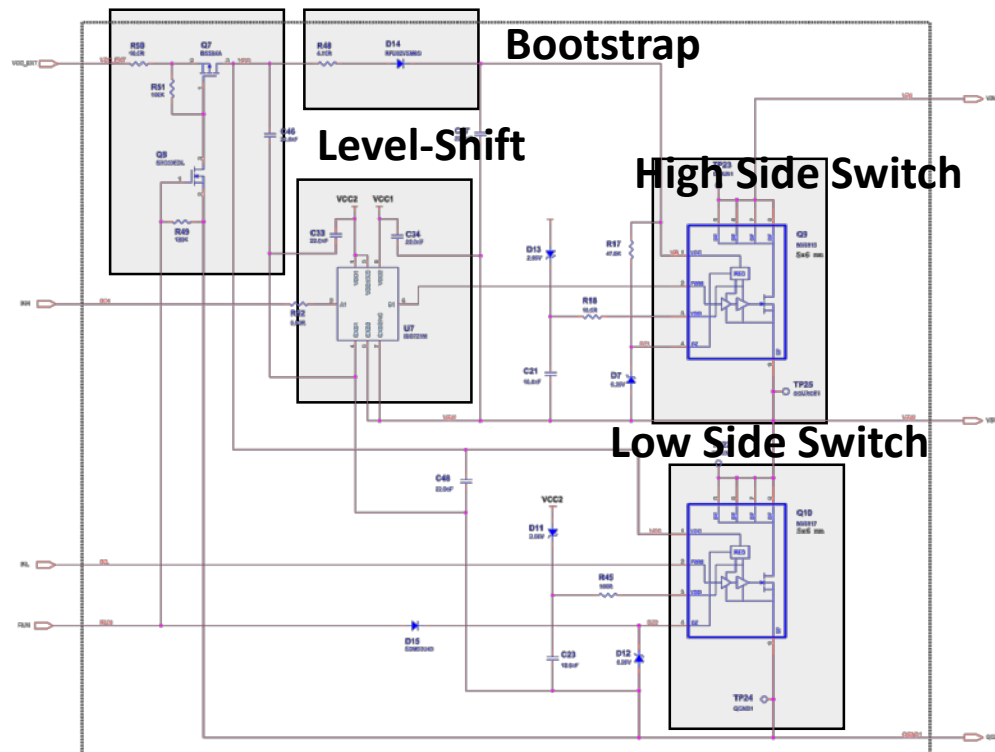

GaNFast™
NV6252 Half-Bridge



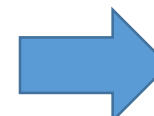


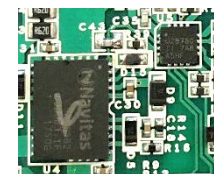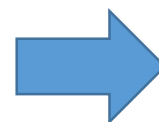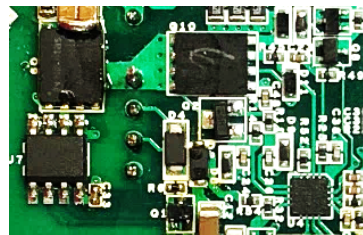- Saved PCB space
- Avoided powertrain layout mistakes -> Noise confined
- Reduces standby loss





GaNFast™ Half-Bridge Power IC

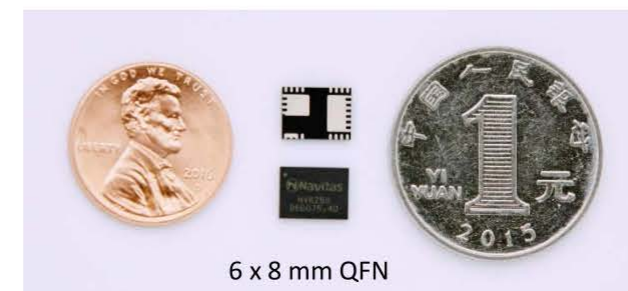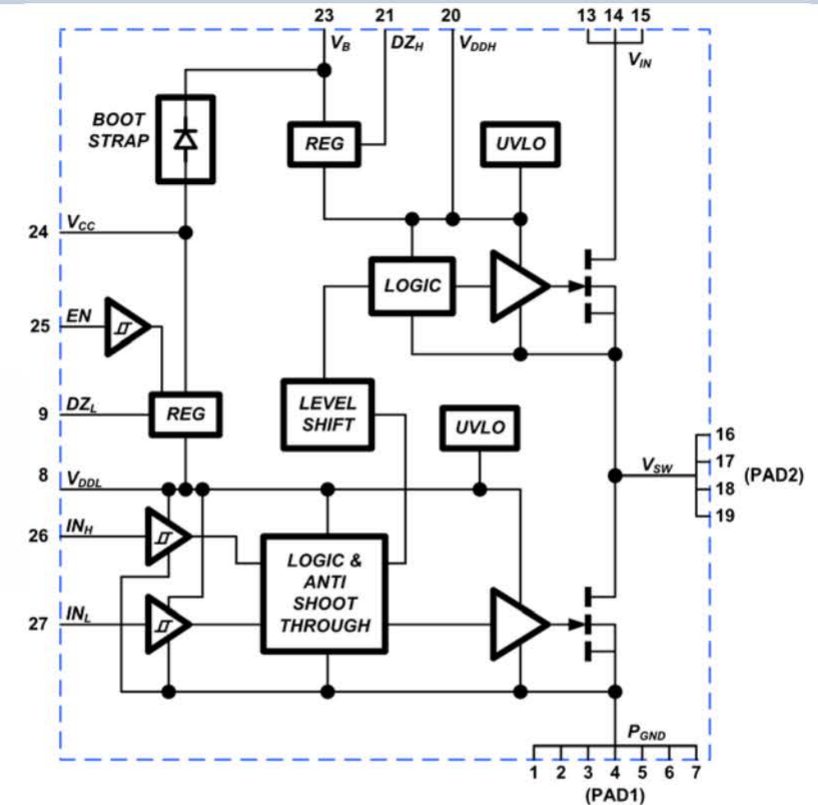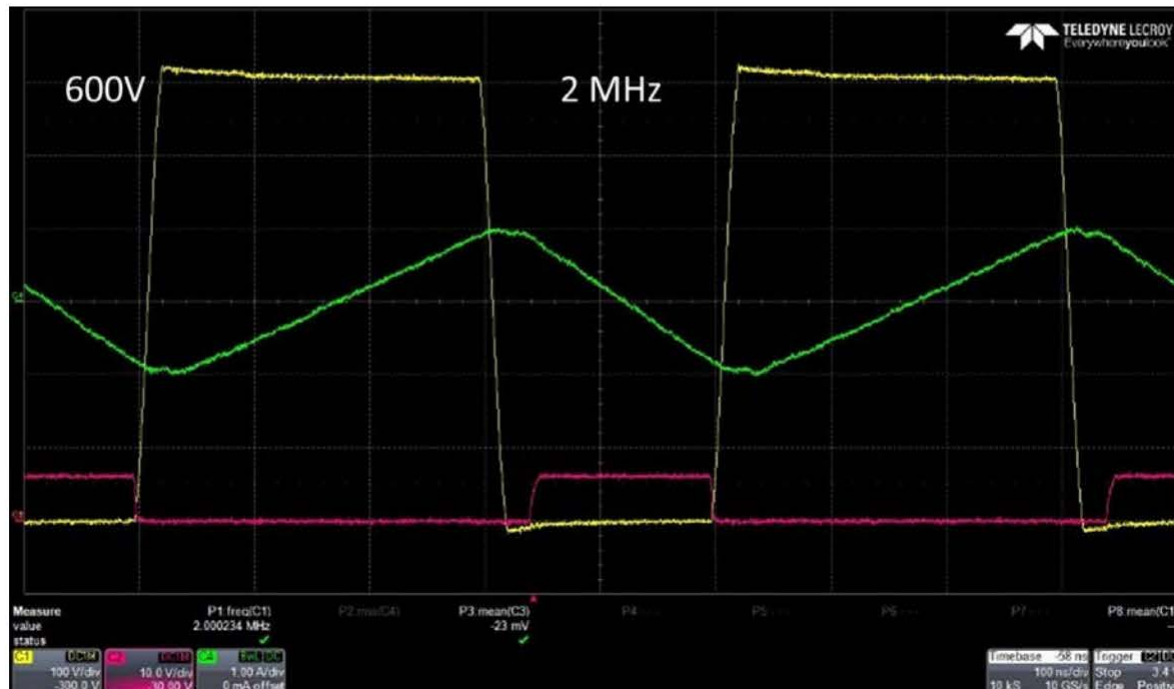- Asymmetric Half-Bridge for ACF
 - 2x GaN FETs (High-side 600 mΩ + Low-side 300 mΩ)
 - 2x GaN drivers
 - GaN Logic (level-shift, bootstrap, UVLO, shoot-through, ESD)



27W USB-PD 3.0 Using GaNFast™ HB Power IC

GaNFast™
NV6252 Half-Bridge

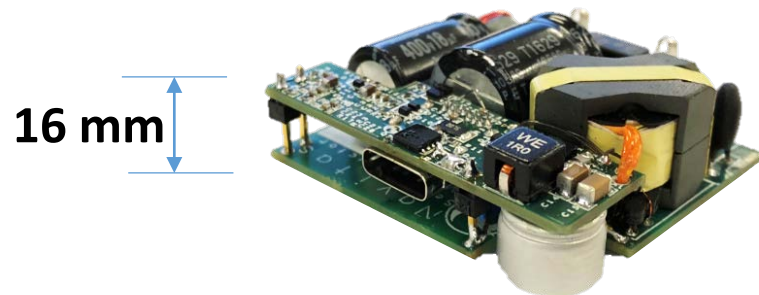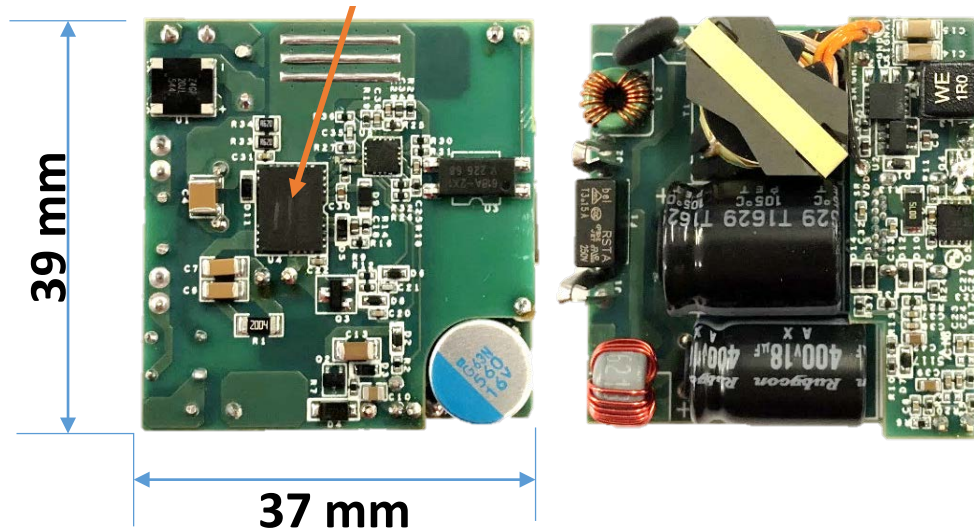


Input	Universal AC (85-265V _{AC} , 47-63Hz)
Output	Type C, USB-PD 3.0 (27W)
Frequency	200-400 kHz
Power Density	1.2 W/cc (19 W/in ³) uncased 0.7 W/cc (11 W/in ³) cased
Construction	4-layer, 2-oz Cu PCB, “No heatsink” design


Efficiency:

Meets CoC Tier 2 and DOE LV VI


Efficiency: 4-Points Average

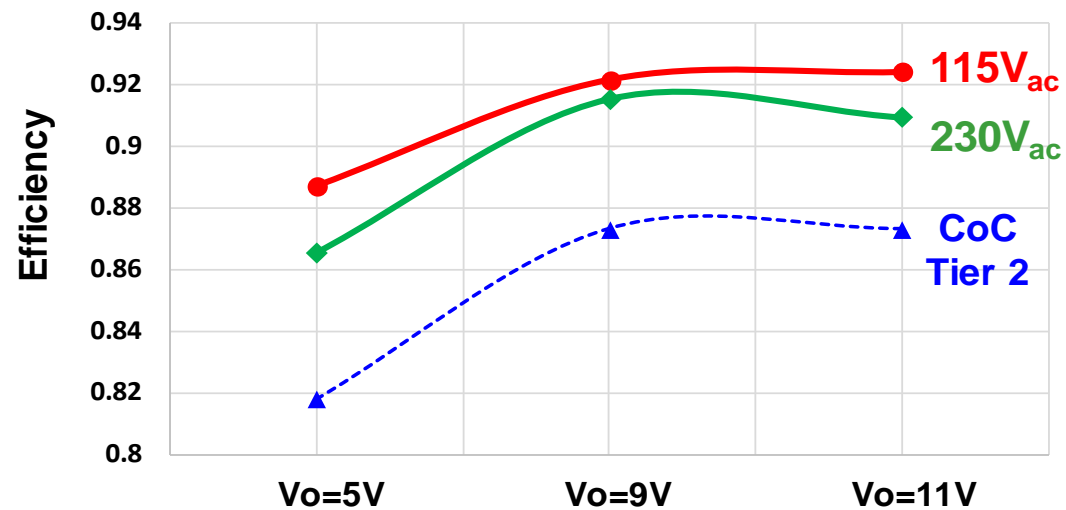

Efficiency: 10% Load

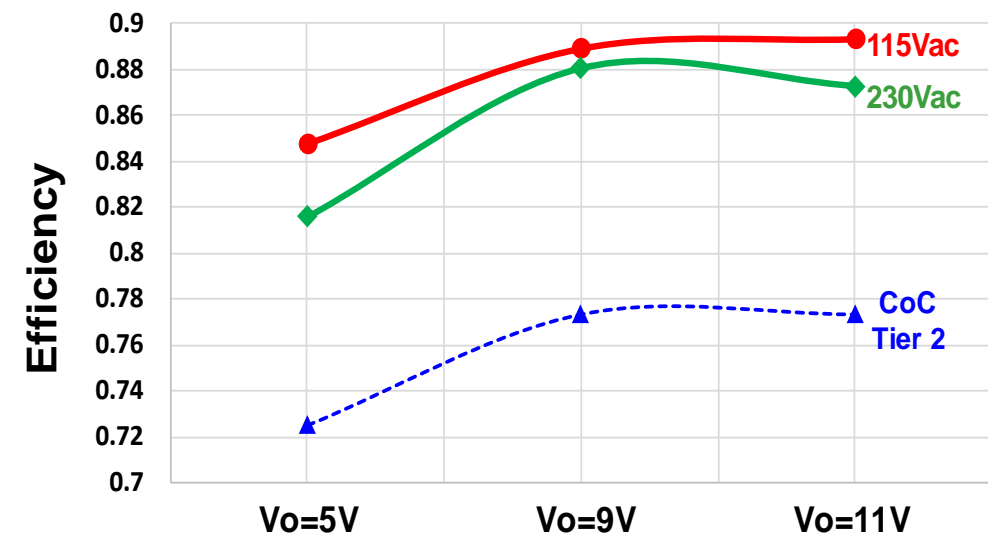


High Frequency 65W ACF with GaN ICs

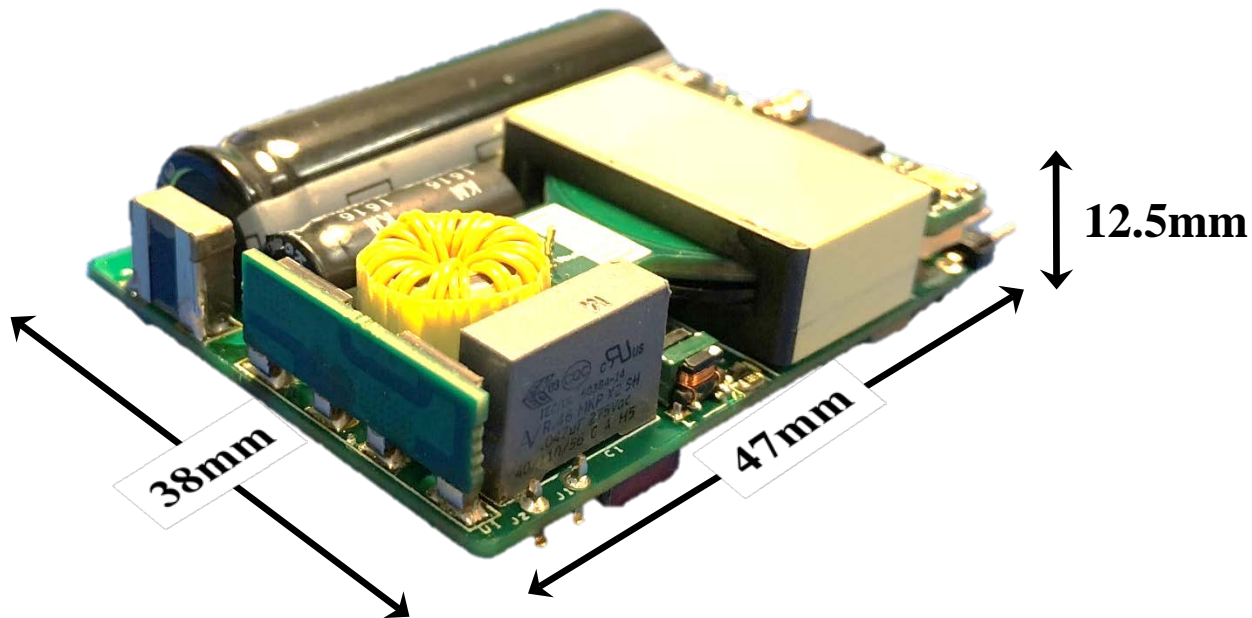

Full Load F_{sw} : 500-600 kHz

Power Density: 47 W/ in³ (Uncased)

→ 26 W/ in³ (2.5mm case)

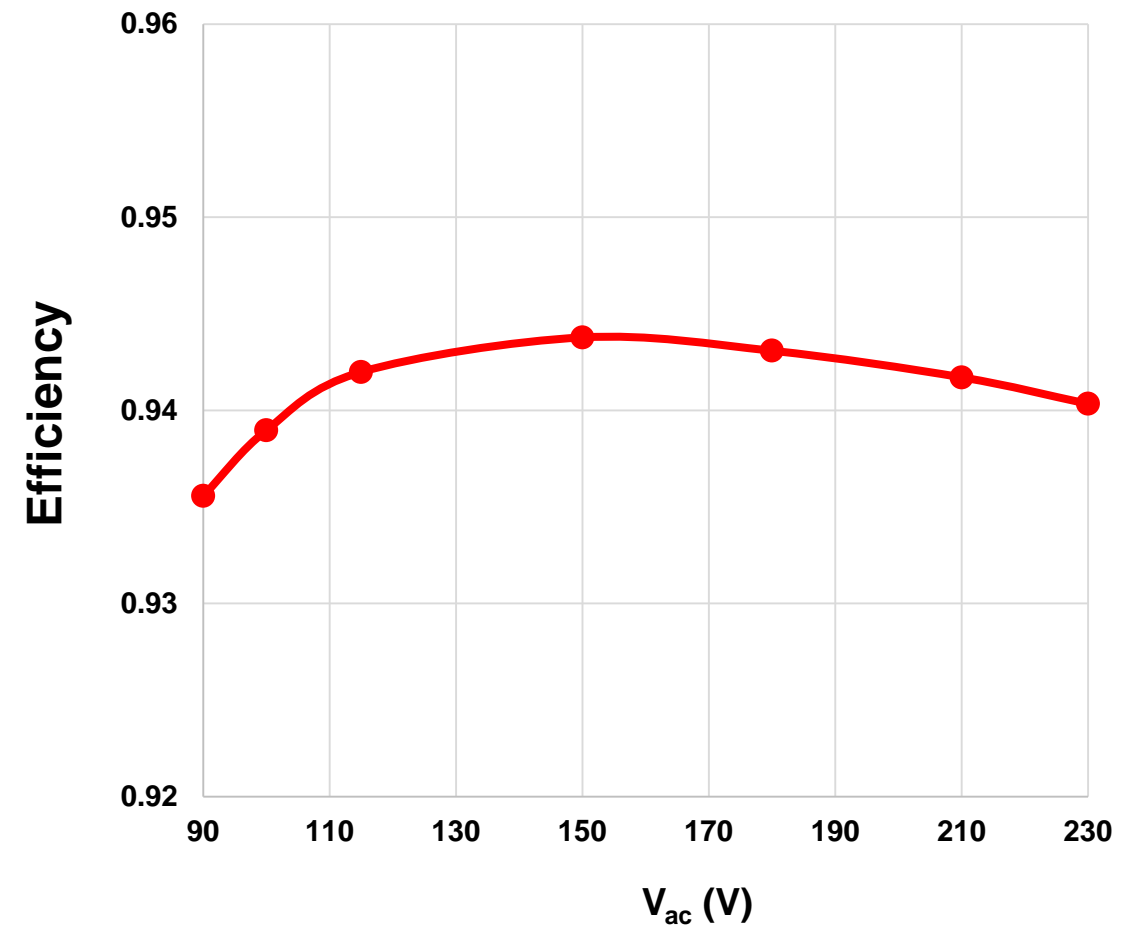

Average Efficiency= **93.4% @115 V_{AC}**, **92% @230 V_{AC}**

Conclusion

- Highly-efficient ACF should minimize the circulating energy
- GaN is uniquely suitable for high frequency ACF operation
- Half-Bridge GaNFast Power IC simplifies ACF design and improves density
- Examples of 27W and 65W PD designs are given showing high efficiency/density