

# Design Guide for GaNSlim Serial Products Used in LLC Circuit

## Scope and purpose

This design guide is to help customers design LLC circuit using GaNSlim power IC. It provides guidelines on reference design, parameters related to special points, to void using risk.

## Table of Contents

Table of Contents .....	1
1. Introduction.....	2
2. Product highlights.....	2
3. Application with NXP LLC controller .....	3
3.1 Reference design .....	3
3.2 Start-up .....	3
3.3 Turn off .....	4
3.4 Quickly on/off .....	4
3.5 Summary.....	4
4. Application with Onsemi LLC controller .....	5
4.1 Reference design .....	5
4.2 Start-up .....	6
4.3 Turn off .....	8
4.4 Load transient.....	8
4.5 Summary.....	9
5. Application with MPS LLC controller .....	9
5.1 Reference design .....	9
5.2 Start-up .....	10
5.3 Turn off .....	11
5.4 Load transient.....	11
5.5 Attention for SHB LLC topology application for HR1275 with GaNSlim .....	12
5.6 Summary.....	13
6. Notes.....	13

## 1. Introduction

This feature-rich 700 V GaNSlim™ Power IC includes a high performance eMode GaN FET, integrated gate drive, and extended features to create the fastest, smallest, most efficient, and most robust integrated powertrain in the world.

Integrated lossless current sensing eliminates external current sensing resistors and increases system efficiency, over-temperature protection increases system robustness, auto standby and sleep mode increase light/tiny/no-load efficiency.

The highest dV/dt immunity, high-speed integrated drive and industry-standard low-profile, low-inductance, DPAK package combine to enable designers to exploit Navitas GaN technology with simple, quick, reliable solutions achieving breakthrough power density and efficiency.

Navitas's GaNSlim™ power ICs extend the capabilities of traditional topologies and enable the commercial introduction of breakthrough designs.

## 2. Product highlights

- Integrated gate drive
- 3.3V/5V/15V PWM logic input compatible
- Programmable accurate GaN current sensing
- Over-temperature protection
- Wide  $V_{CC}$  range (6.2V to 24V typical)
- Low standby current (< 50uA typical)
- Sleep mode current (<10uA max)
- Built-in turn-on dV/dt optimization
- Built-in turn-off di/dt optimization
- Reliable hard and soft switching
- Zero reverse recovery charge


### DPAK-4L package with grounded cooling pad

- Grounded cooling pad
- Minimized package inductance
- Low thermal resistance

### 3. Application with NXP LLC controller

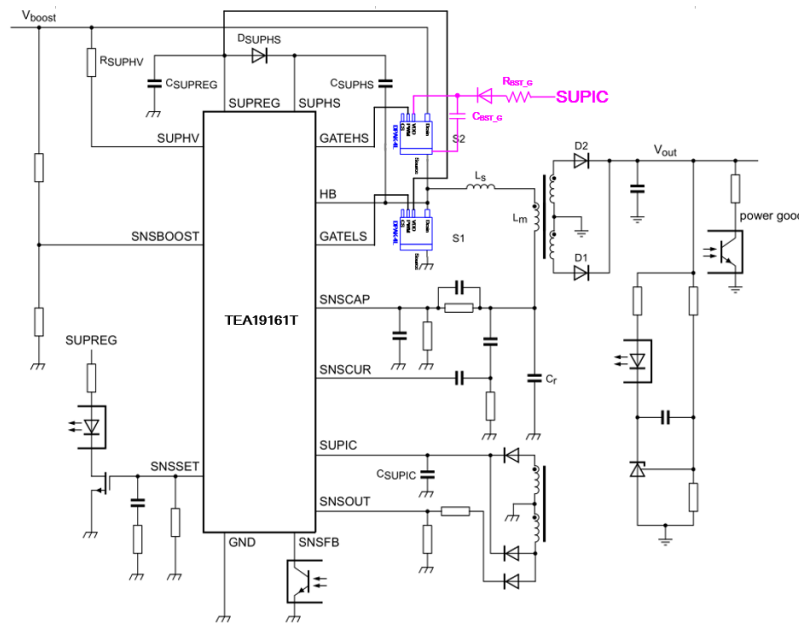
#### 3.1 Reference design

- LLC IC: TEA19161T(NXP)
- LLC Switch: NV6148CQ01(high side) + NV6148CQ01(low side)
- $V_{cc}$  capacitor for high side supply: 10uF
- $V_{cc}$  voltage for high side switch:19V




Typical applications circuit

#### 3.2 Start-up

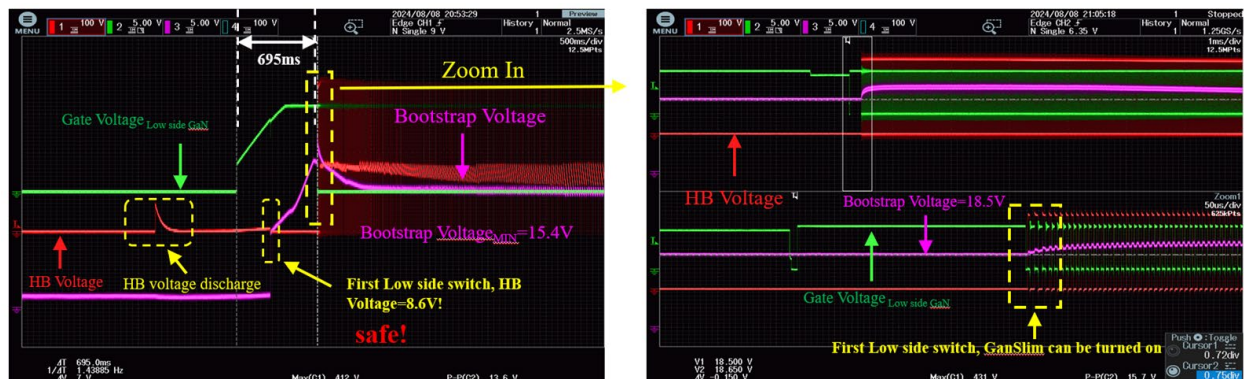


No Load Start-up @Vbus=0V

### 3.3 Turn off

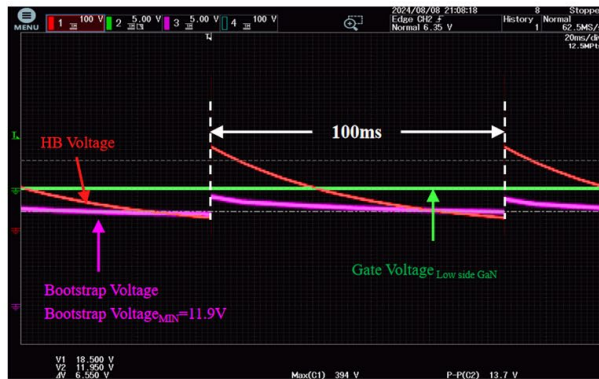


No load operation

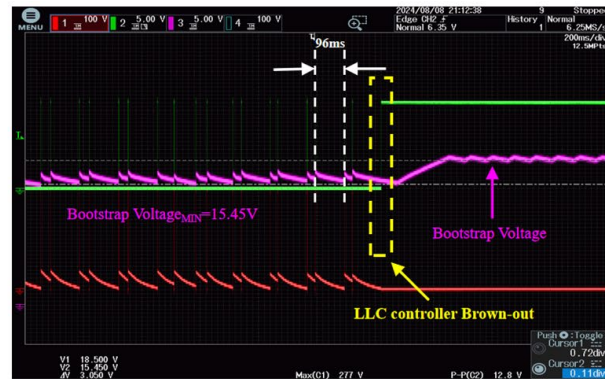


Turn off @ No load

### 3.4 Quickly on/off

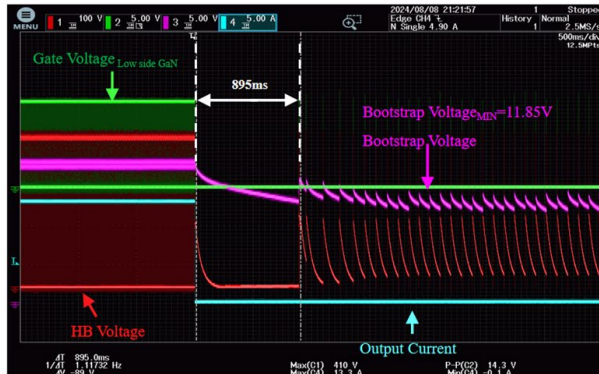

Full Load to No-Load

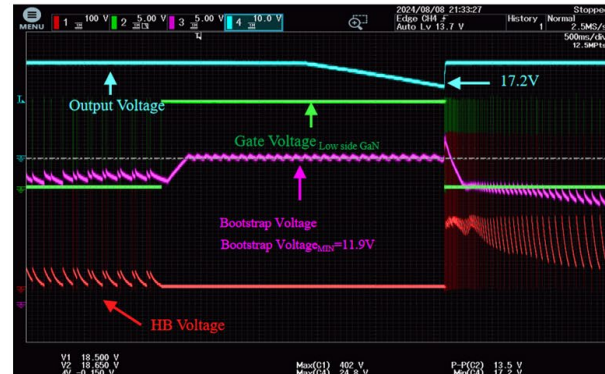

No-Load Start-up @ High Output Voltage


### 3.5 Summary

Before driver signal, the HB voltage was pulled down to GND. It has plenty of time high  $V_{CC}$  capacitor. That the GaNSlim was applied on LLC circuit with NXP controller is no problem.

## 4. Application with Onsemi LLC controller

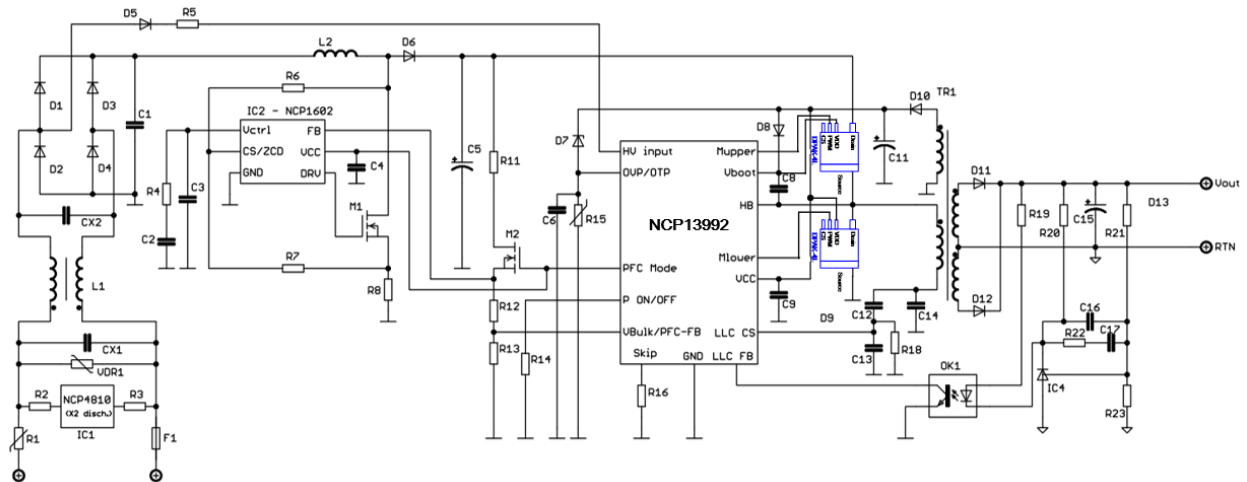
### 4.1 Reference design

- LLLC IC: Onsemi NCP13992 except version (AB, AD, AH, AR, AS)
- LLC Switch: NV6148CQ01(high side) + NV6148CQ01(low side)
- $V_{cc}$  capacitor for high side switch: 10uF
- $V_{cc}$  voltage for high side switch:16V



Typical applications circuit

## 4.2 Start-up

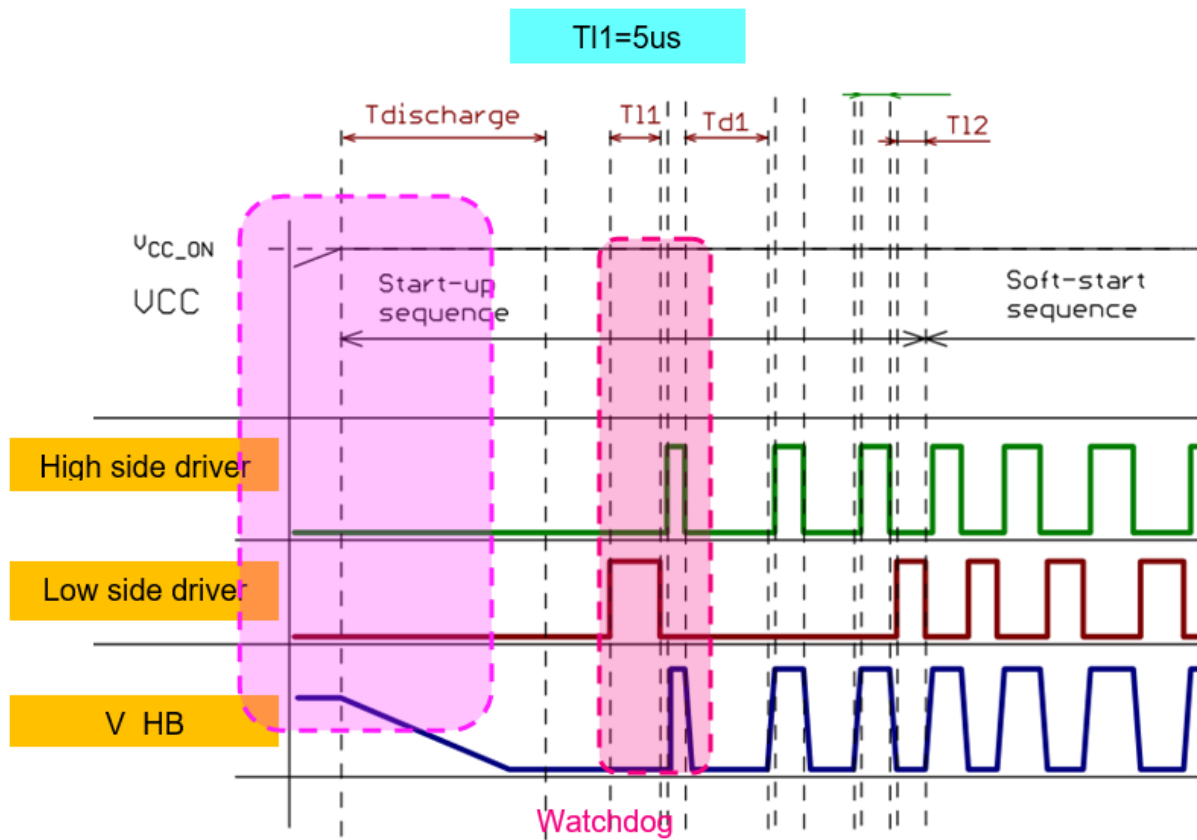




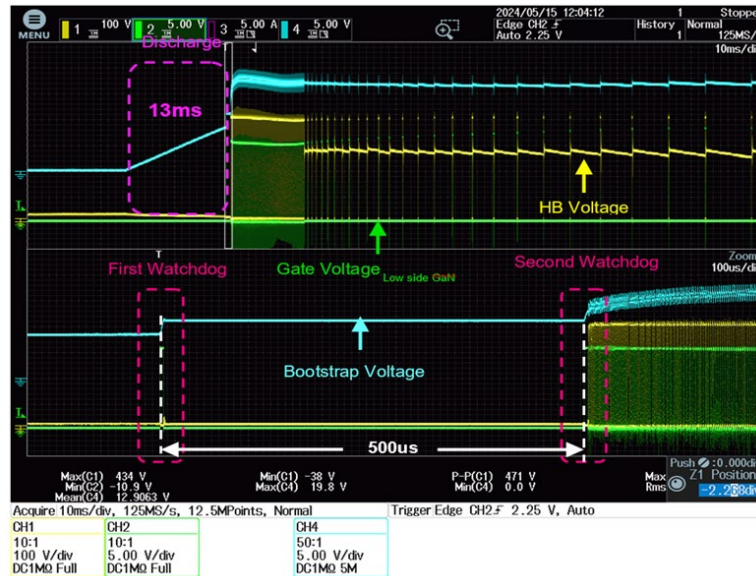
## Start-up flow

The first step is to release  $V_{HB}$  below  $V_{HB\_MIN}$  (10V), during this period can charge the Bootstrap capacitor.


The second step is to program check, consisting of a 5 $\mu$ s low side gate and 500ns high side gate. If the high side gate is not opened, it will wait for another 500 $\mu$ s to check again.



No Load Start-up @Vbus=0V

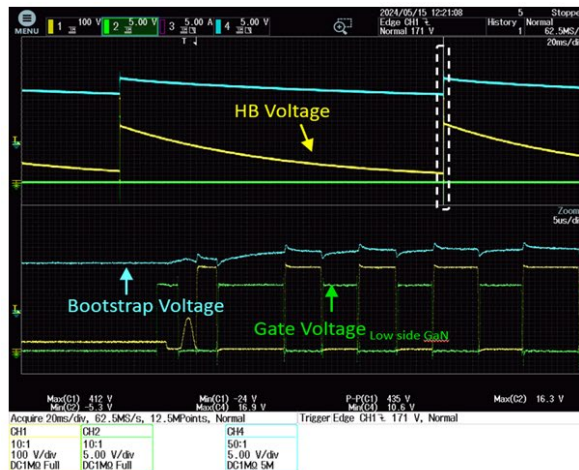

Quiet skip mode

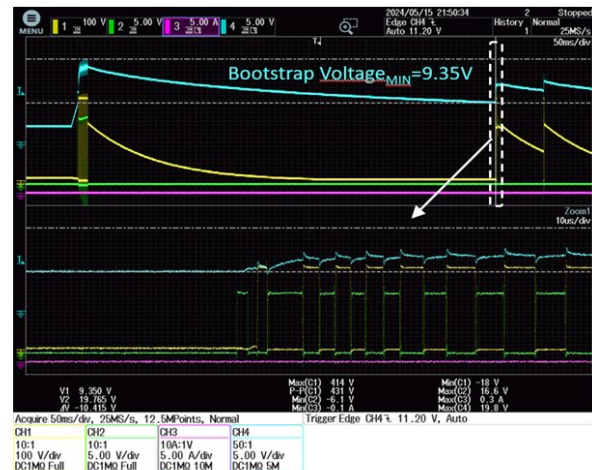

Start-up @ High Output Voltage

## 4.3 Turn off



## 4.4 Load transient





## 4.5 Summary

During normal soft-startup, high side GaNSlim cannot be opened at the first watchdog signal, but it does not affect the normal operation of the soft-start up. After the IC triggers the protection, the IC goes through a soft startup again, so it can also work well.


Onsemi LLC controller have a HB voltage discharge function before Startup. So, when the Onsemi LLC controller is paired with GanSlim, both the split resonant capacitor and the single resonant capacitor wiring methods are applicable.

In the Onsemi NCP13992 series of LLC controllers, there is a type of controller that cannot be compatible with our GaNSlim serial products. That is NCP13992(AB, AD, AH, AR, AS).

## 5. Application with MPS LLC controller
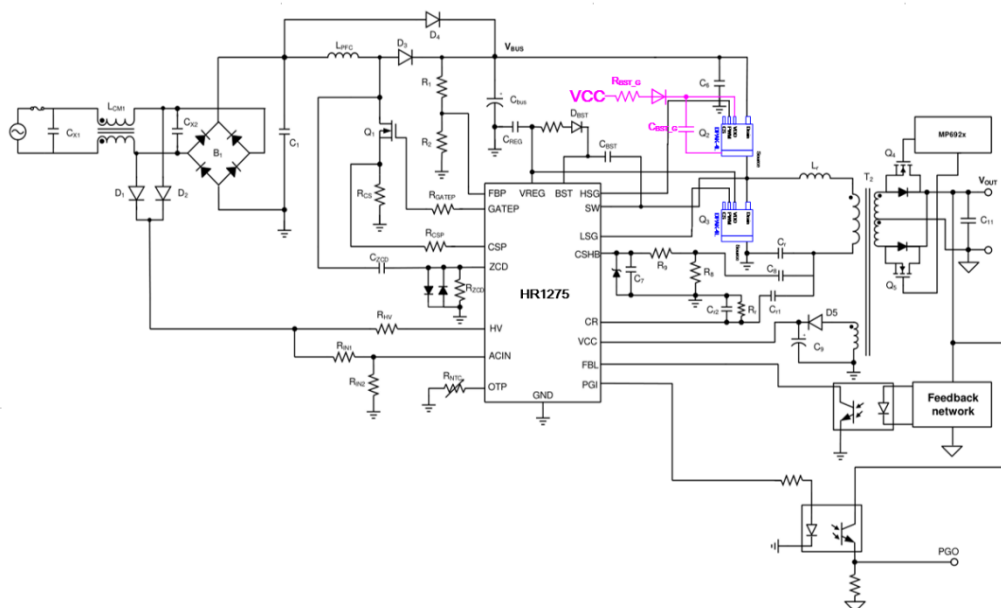
### 5.1 Reference design

- LLC IC: HR1275(MPS)
- LLC Switch: NV6148CQ01(high side) + NV6148CQ01(low side)
- $V_{cc}$  capacitor for high side supply: 10uF
- $V_{cc}$  voltage for high side switch:19V




Typical applications circuit

## 5.2 Start-up

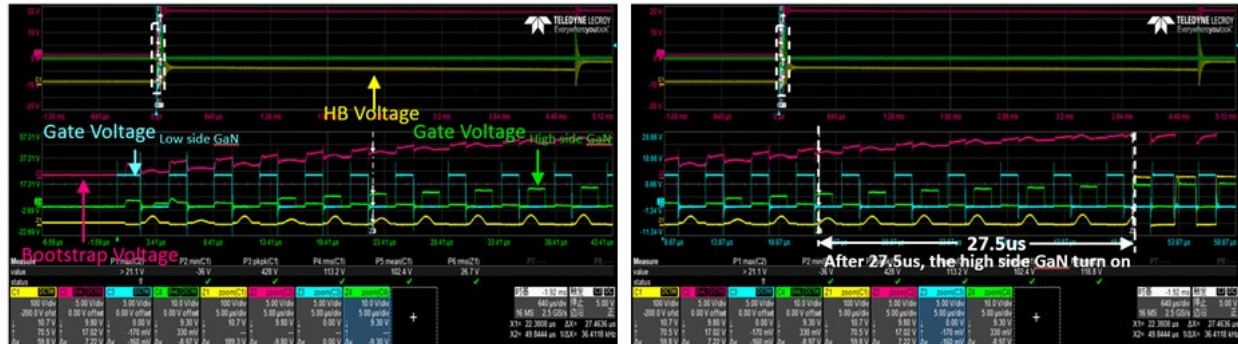
### HR1275 start-up flow

The controller detects Vbst voltage, After the voltage of Vbst is higher than 5V, the high side gate signal was given.

The pulse of low side and high side were always given, and the LLC controller do not go through protection mode.




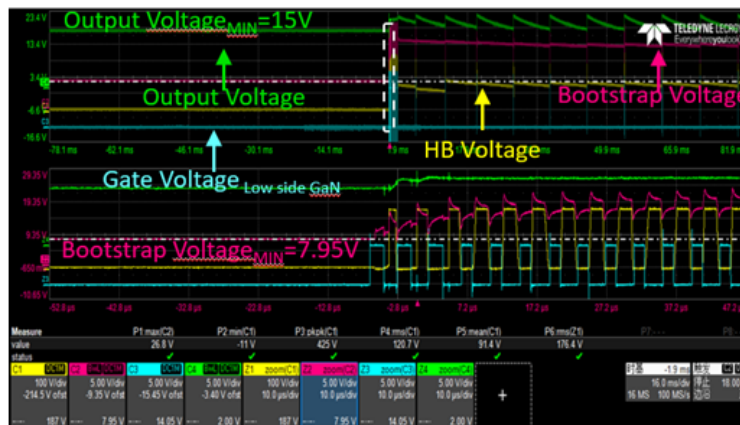NO load start-up when output voltage is 0




Shut down and restart, when output voltage is high voltage

### 5.3 Turn off

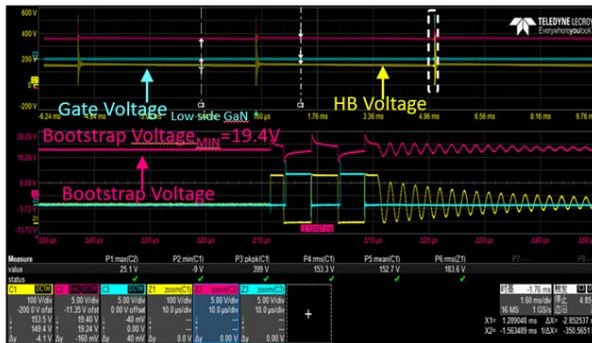


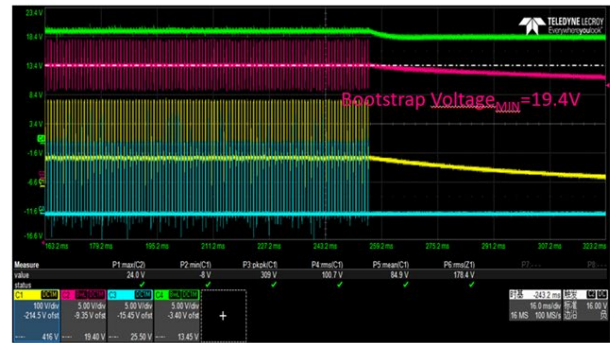In Burst mode, Vbst voltage is around 19V.





When AC is off, the Vbst is steady at 19V.

### 5.4 Load transient

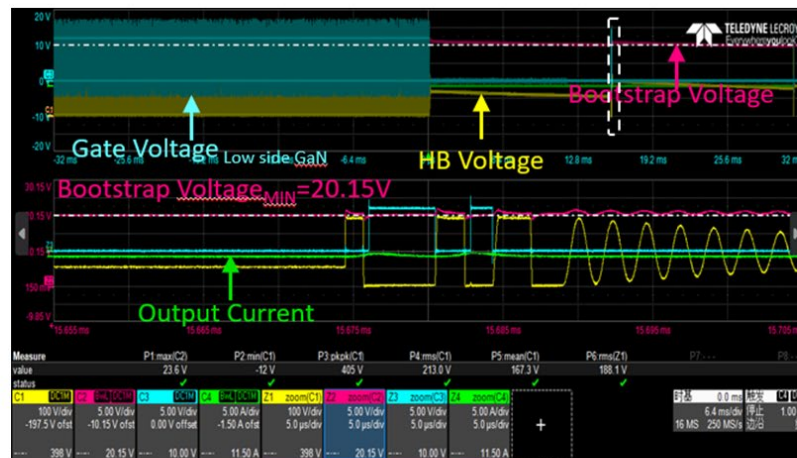


When high load transient to no load, the Vbst is higher than 20V, there is no risk of power failure

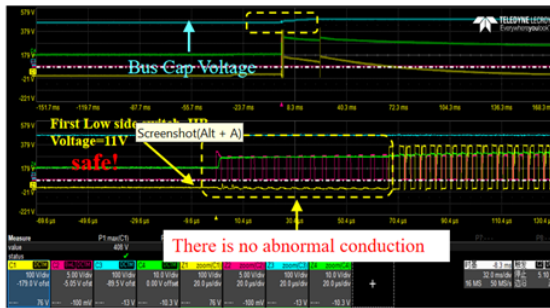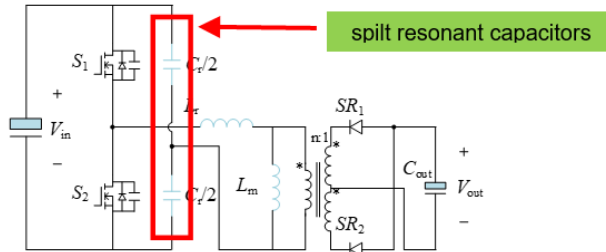
## 5.5 Attention for SHB LLC topology application for HR1275 with GaNSlim



No Load Start-up @Vbus=370V

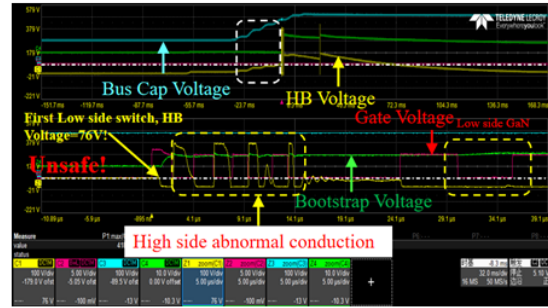

No Load Start-up @Vbus=0V

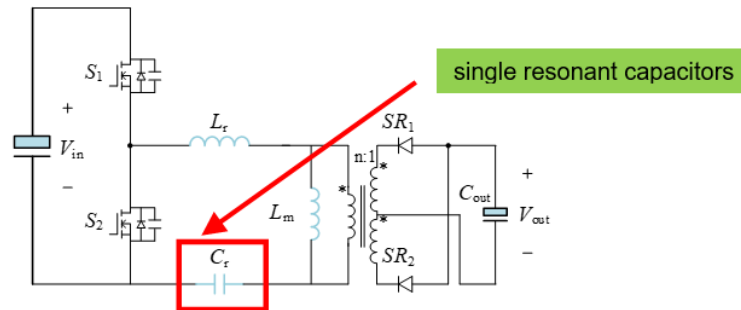

No Load Start-up @Vbus=0V

## 5.6 Summary

Because MPS LLC controller does not have a HB voltage discharge function before Startup, it is not suitable to use the split resonant capacitors.

When the MPS LLC controller is paired with GaNSlim, it is recommended to use the single resonant capacitors.

During normal soft-startup, high side GaNSlim cannot be opened at the first gate signal, but it does not affect the normal operation of the soft-startup.

After the IC triggers the protection, the IC goes through a soft startup again, so it can also work well.

## 6. Notes

- 1) When you use GaNSlim to design LLC circuit, the controller you selected must be able to soft start, even at the first drive signal.
- 2) The controller must be able to keep giving the drive signal until it works properly at start-up. When the controller is started, it must send several high-side and low-side drive signals to ensure the normal power supply of the high-side drive.
- 3) The first high side drive pulse width given by controller must be greater than 350ns.

If you have any questions, please contact Navitas's FAE.

## Additional Information

DISCLAIMER Navitas Semiconductor (Navitas) reserves the right to modify the products and/or specifications described herein at any time and at Navitas' sole discretion. All information in this document, including descriptions of product features and performance, is subject to change without notice. Performance specifications and the operating parameters of the described products are determined in the independent state and are not guaranteed to perform the same way when installed in customer products. The information contained herein is provided without representation or warranty of any kind, whether express or implied. This document is presented only as a guide and does not convey any license under intellectual property rights of Navitas or any third parties. Navitas' products are not intended for use in applications involving extreme environmental conditions or in life support systems. [Terms and Conditions](#).

Navitas, GaNFast, GaNSense, GeneSiC, and the Navitas logo are trademarks or registered trademarks of Navitas Semiconductor and subsidiaries. All other brands, product names, and marks are or may be trademarks or registered trademarks used to identify products or services of their respective owners.

Copyright ©2024 Navitas Semiconductor. All rights reserved.  
Contact: [info@navitassemi.com](mailto:info@navitassemi.com)

