

**APEC**  
**2024**

LONG BEACH  
CALIFORNIA  
CONVENTION CENTER

February 25<sup>th</sup> - 29<sup>th</sup>

# GaN Half-Bridge Power IC and AHB/Totem-Pole Topologies Enable 240W, 150cc, PD3.1 Solution with 96% Efficiency

Tom Ribarich, Sr. Dir. Strategic Marketing,  
Navitas Semiconductor,  
[tom.ribarich@navitassemi.com](mailto:tom.ribarich@navitassemi.com)



# Presentation Outline

---

- 240W GaN Chargers
- Topology Comparisons
- NV6269C GaNSense Half-Bridge IC
- 240W-1C PD3.1 150cc Charger Design
- Conclusions

# 240W USB-C GaN Chargers Are Here!

---



**Anker Prime 240W-3C/1A**  
104.5 x 78.4 x 33.8 mm = 277 cc  
Power Density = 0.87 W/cc  
Efficiency = 92% (90Vac/100%)


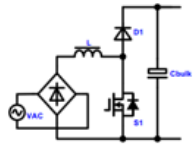
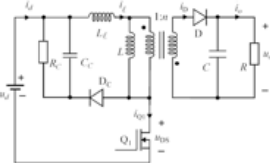
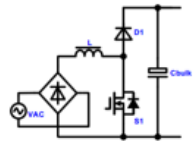
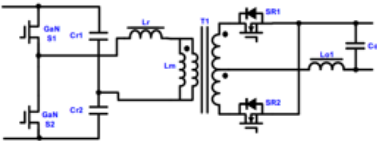
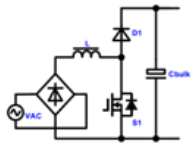
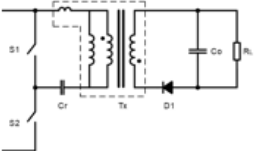
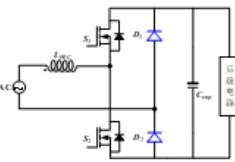


**WOTOBEUS 240W-3C/2A**  
113 x 86 x 32 mm = 311 cc  
Power Density = 0.77 W/cc  
Efficiency = 91.3% (90Vac/100%)

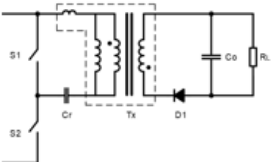

**CHIPOFY 240W-3C/1A**  
90 x 65 x 36 mm = 211 cc  
Power Density = 1.14 W/cc  
Efficiency = 90.5% (90Vac/100%)




# NV6269C Enables Next Gen High-Frequency, High EFF, High Power Density, Half-Bridge Topologies!

Topology	PFC Stage	DC-DC Stage	Pros	Cons	Summary
<b>PFC + QR</b> ( $< 120W$ )			<ul style="list-style-type: none"> <li>• 2x HV Switches</li> <li>• 1x SR Switch</li> <li>• Variable Vout</li> <li>• Low cost</li> <li>• Many controllers</li> </ul>	<ul style="list-style-type: none"> <li>• Low Power Density</li> <li>• Low Efficiency</li> <li>• Low flux cancellation</li> </ul>	Used for low cost, low power density, variable Vout solutions (PD3.1)
<b>PFC + LLC</b> (200-300W)			<ul style="list-style-type: none"> <li>• High flux cancellation</li> <li>• High efficiency</li> <li>• High power density</li> <li>• Many controllers</li> </ul>	<ul style="list-style-type: none"> <li>• 3x HV switches</li> <li>• 2x SR switches</li> <li>• Fixed Vout</li> <li>• Add'l buck for variable Vout</li> <li>• High cost</li> </ul>	Used for high efficiency, high power density, fixed Vout solutions
<b>PFC + AHB</b> (200-300W)			<ul style="list-style-type: none"> <li>• 1x SR Switch</li> <li>• Variable Vout</li> <li>• Good flux cancellation</li> <li>• High efficiency</li> <li>• High power density</li> </ul>	<ul style="list-style-type: none"> <li>• 3x HV switches</li> <li>• Few controllers</li> <li>• Medium cost</li> </ul>	Used for high efficiency, high power density, variable Vout solutions (PD3.1)
<b>TTP + AHB</b> (200-300W)			<ul style="list-style-type: none"> <li>• 1x SR Switch</li> <li>• Variable Vout</li> <li>• Good flux cancellation</li> <li>• Highest efficiency</li> <li>• Highest power density</li> </ul>	<ul style="list-style-type: none"> <li>• 6x HV switches</li> <li>• High cost</li> <li>• Few controllers</li> </ul>	Used for highest efficiency, highest power density, variable Vout solutions (PD3.1)

# NV6269C GaNSense Half-Bridge IC

NV6269C GaNSense Half-Bridge IC		
Features	Simplified Schematic	Package
<p><b>GaNFast™ Power IC</b></p> <ul style="list-style-type: none"> <li>Two independent logic PWM inputs</li> <li>3.3, 5, 12 V PWM input compatible</li> <li>Floating high-side with internal level shift</li> <li>Integrated high-side bootstrap</li> <li>Integrated gate drive &amp; voltage</li> <li>Wide V<sub>CC</sub> range (10 to 24 V)</li> <li>Hi &amp; Lo-side turn-on dV/dt slew rate control</li> </ul> <p><b>GaN Power FETs</b></p> <ul style="list-style-type: none"> <li>150/150 mΩ (NV6267C/M), 70/70 mΩ (NV6269C/M)</li> <li>Zero reverse recovery charge</li> <li>800 V<sub>max_tran</sub> &amp; 650 V<sub>max_cont</sub> ratings</li> </ul> <p><b>GaNSense™ Technology</b></p> <ul style="list-style-type: none"> <li>Integrated loss-less current sensing</li> <li>Over-current &amp; over-temperature protection</li> <li>Autonomous low-current standby mode</li> </ul> <p><b>Small, low-profile SMT PQFN</b></p> <ul style="list-style-type: none"> <li>8x10 mm footprint</li> <li>Minimized package inductance</li> <li>Large cooling pads</li> </ul>		<p>QFN 8x10</p>
<p><b>Key System Benefits</b></p> <ul style="list-style-type: none"> <li>✓ No external half-bridge driver required</li> <li>✓ Loss-less current sensing = +0.5 EFF benefit</li> <li>✓ No ext. RCS resistors, no 85C RCS hot spot</li> <li>✓ OCP, OTP protection features</li> <li>✓ Autonomous low standby current mode</li> <li>✓ Enlarged cooling pads</li> <li>✓ Low RDSON + larger package enables 50% to 67% higher power levels!</li> </ul>		
<p><b>Typical Application Schematic (LLC)</b></p> <p>No RCS</p>		
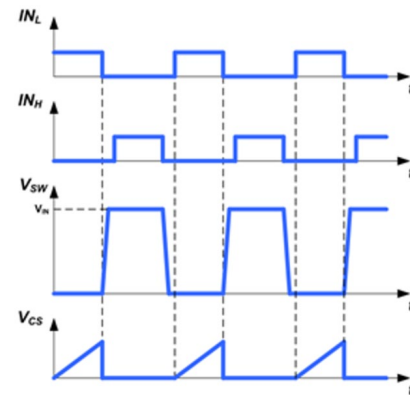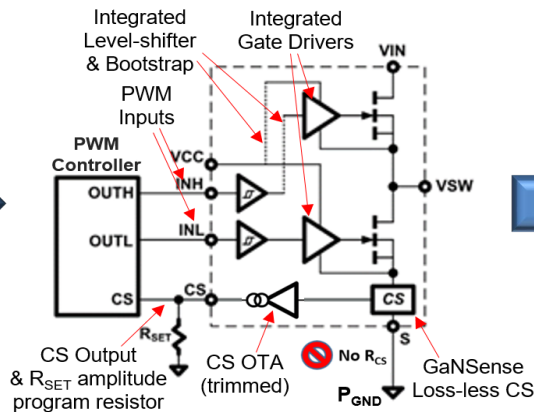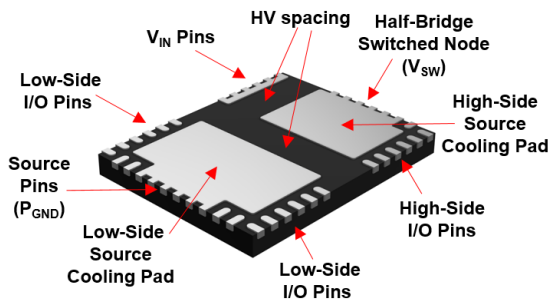
# NV6269C = Highest Integration, Lowest RDSON, Largest Cooling Pads & Simple Circuit Block



## NV6269C

- ✓ QFN 8x10 package
- ✓ Large cooling pads
- ✓ Low-side I/O pins
- ✓ High-side I/O pins
- ✓ 650V functional isolation

## Fully-Integrated GaNSense Half-Bridge IC


- ✓ Wide range VCC
- ✓ PWM inputs
- ✓ Level-shifting
- ✓ Gate drivers
- ✓ Bootstrap
- ✓ 2x 70m GaN power FETs
- ✓ Loss-less GaNSense with CS output

## Simple Half-Bridge Circuit Block

- ✓ 2x Low-side wide range PWM inputs
- ✓ 650V GaN half-bridge switched node output
- ✓ Programmable CS output
- ✓ Extra protection circuits (OCP/OTP)

# GaN Sense Half-Bridge IC = Smallest PCB Area, Fewest Components, No Ringing, No Glitching!



## NV6269C GaNSense Half-Bridge IC

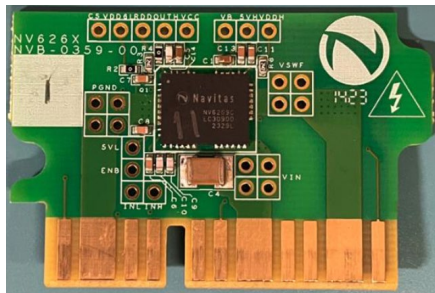

- ✓ 13 components
- ✓ 122mm<sup>2</sup> footprint
- ✓ Int. level shifters
- ✓ Int. bootstrap
- ✓ Int. gate drivers
- ✓ No exposed gates

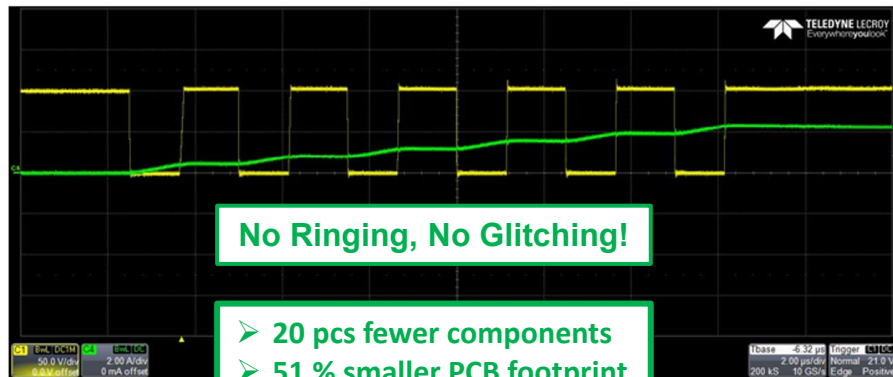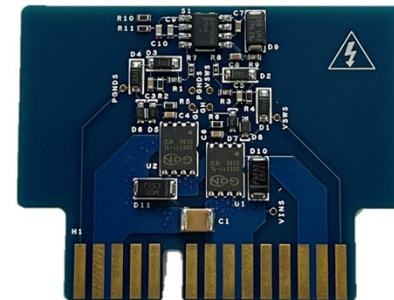
## Discrete GaN Half-Bridge

- ✗ 33 components
- ✗ 250mm<sup>2</sup> footprint
- ✗ 1x ext. HB driver HVIC
- ✗ 1x ext. HV bootstrap
- ✗ 2x HV bypass diodes
- ✗ 2x gate drive circuits
- ✗ Exposed gates




No Ringing, No Glitching!

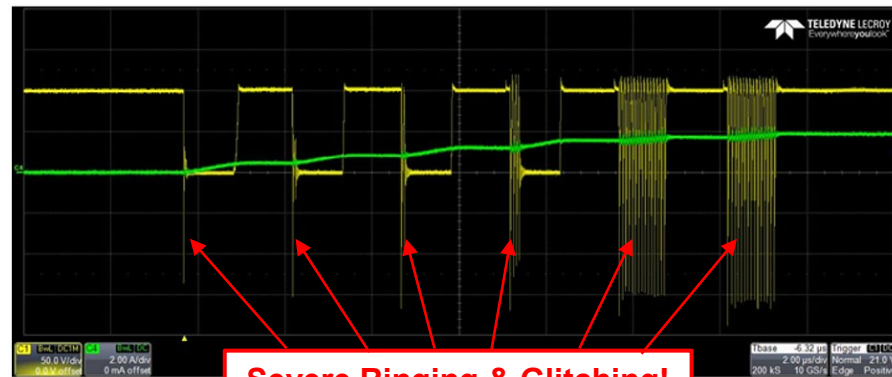- 20 pcs fewer components
- 51 % smaller PCB footprint
- No exposed gates
- Clean, reliable switching!




Severe Ringing & Glitching!

# 240W-1C TTP + AHB + GaNSense = 150 cc

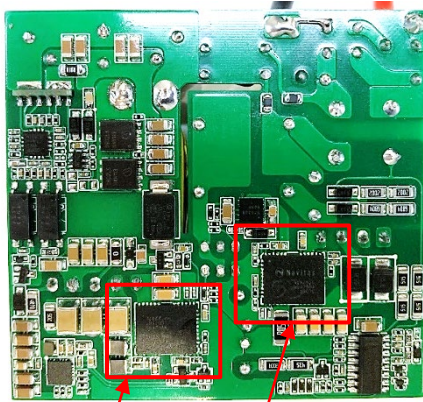


NV6269C  
(AHB)

NV6269C  
(TTP)

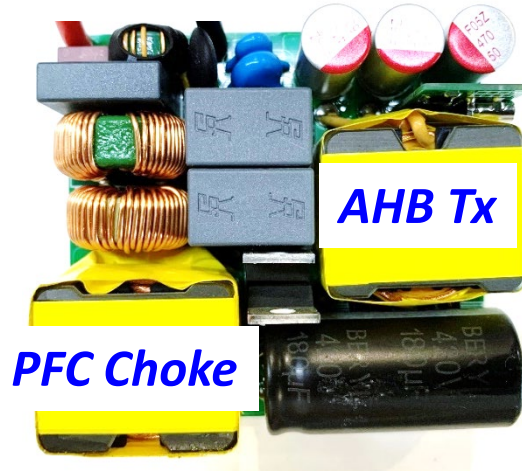

PFC Choke

AHB Tx


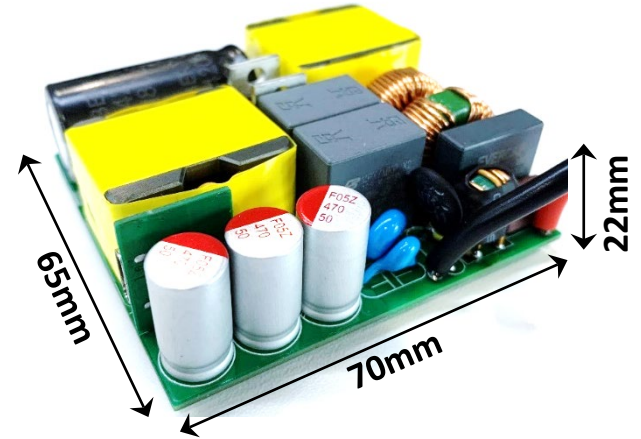


- Efficiency: 96 % (@90Vac/36V/6.7A)
- PCBA: 70 x 65 x 22 mm<sup>3</sup> = 100 cc
- Cased: 76 x 71 x 28 mm<sup>3</sup> = 150 cc
- +4% to +5.5% efficiency benefit vs existing designs!
- 29% to 52% smaller size vs existing designs!





# TTP Waveforms = Clean & Sinusoidal

115Vac/60Hz  
@ 240W

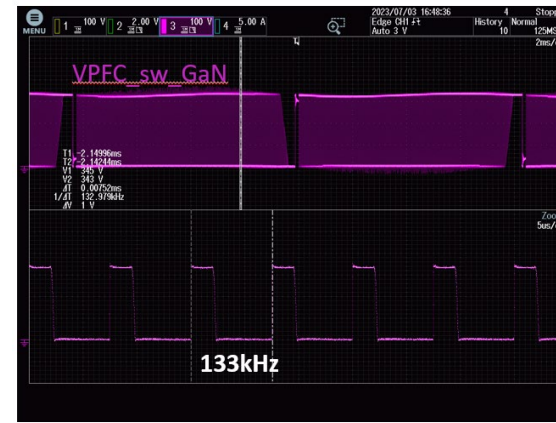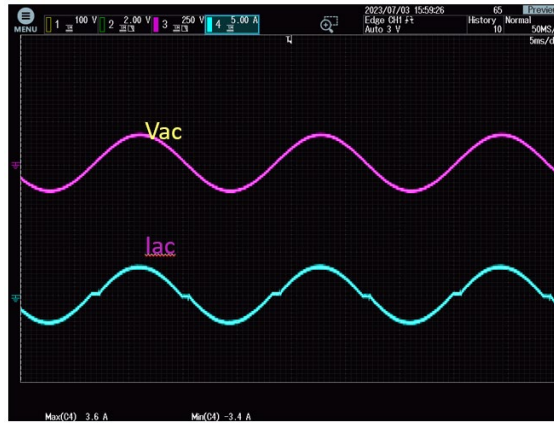

230Vac/60Hz  
@ 240W

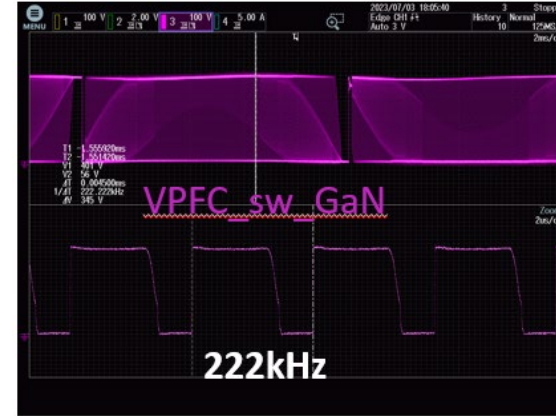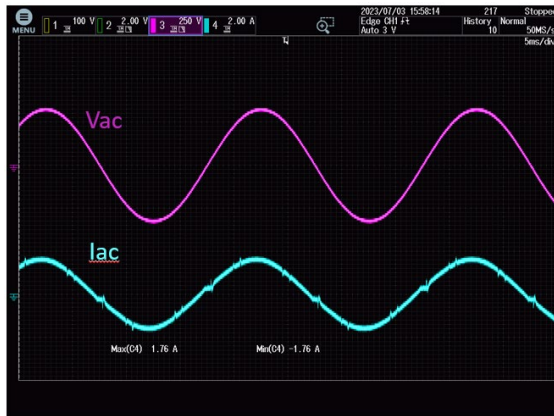


# AHB ZVS Waveforms = Smooth & Clean







## 115Vac/36V/6.7A



## 230Vac/36V/6.7A

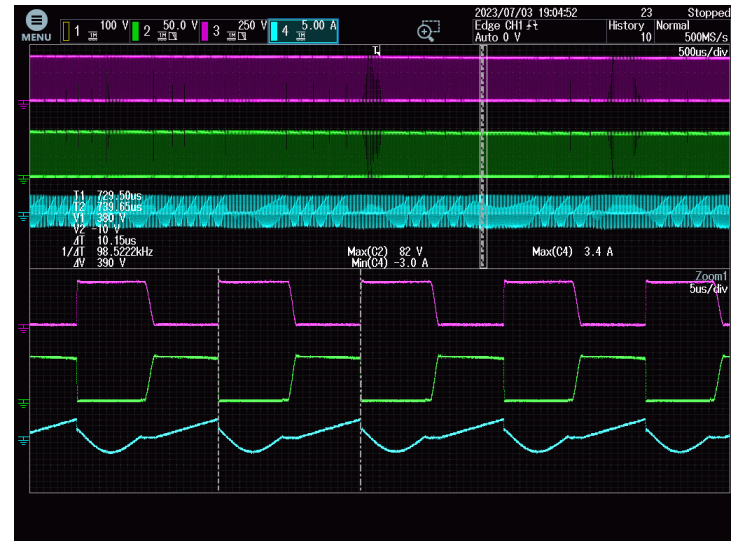


# Peak Efficiency > 97%

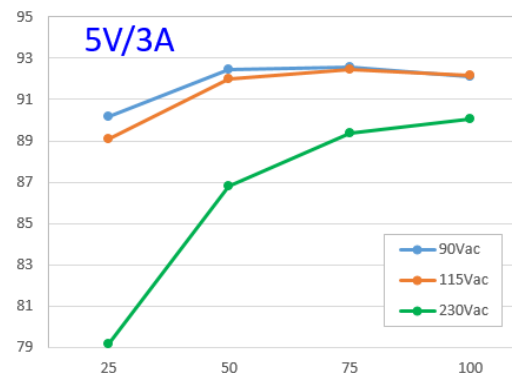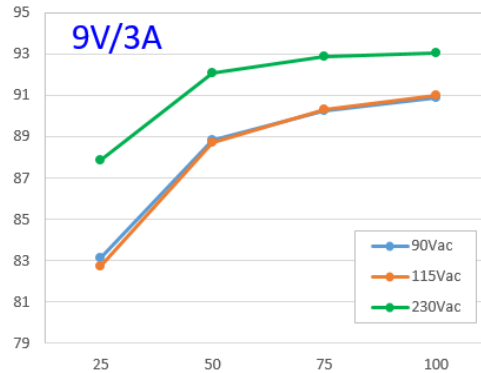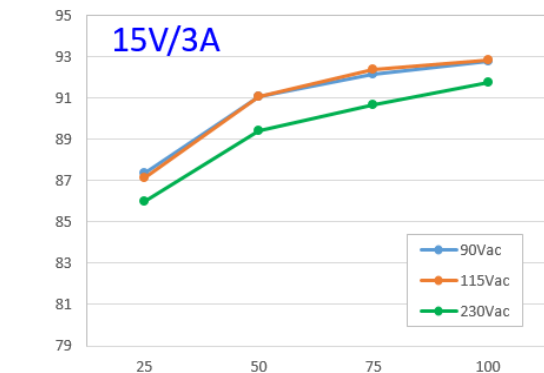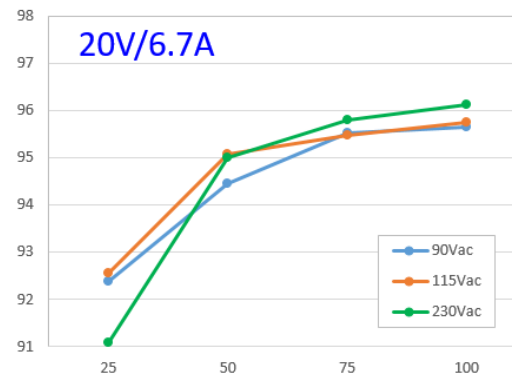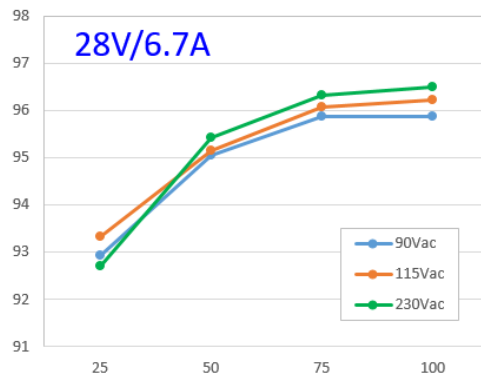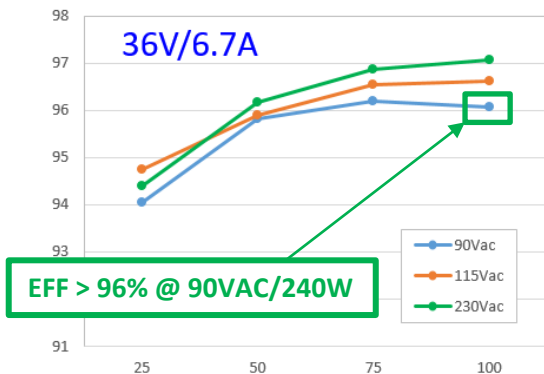


	115Vac	230Vac
<b>Pin @Standby (5V/0A)</b>	<b>64mW</b>	<b>142mW</b>


# Lower Losses = Lower Thermals!

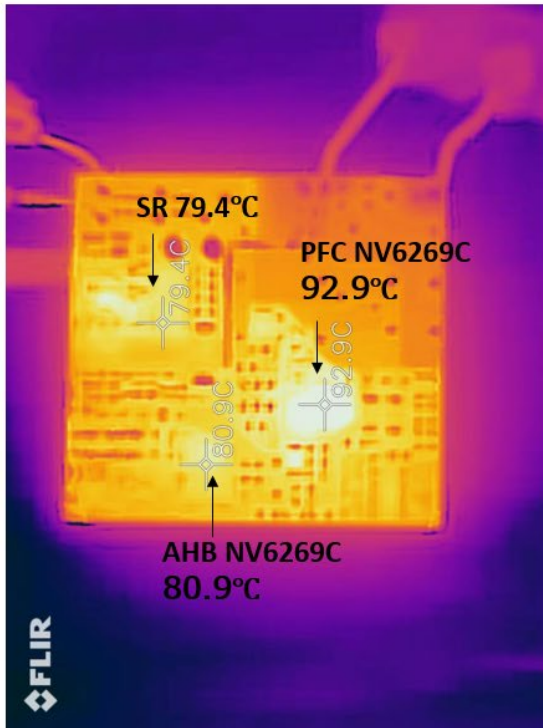

90Vac

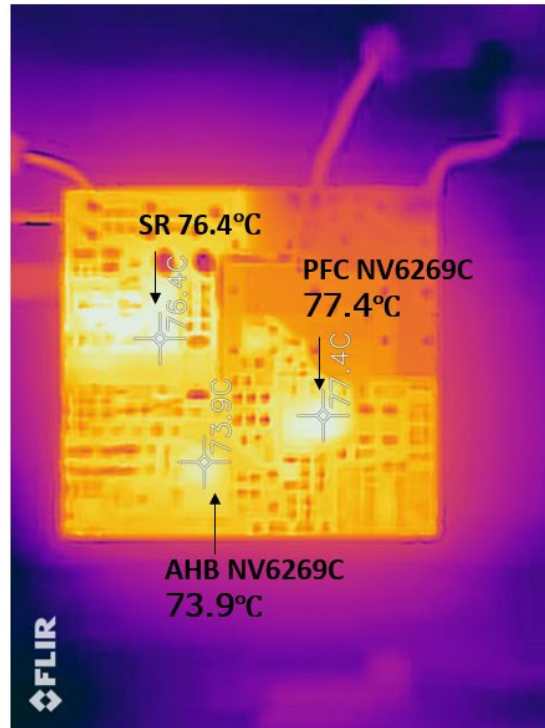

115Vac

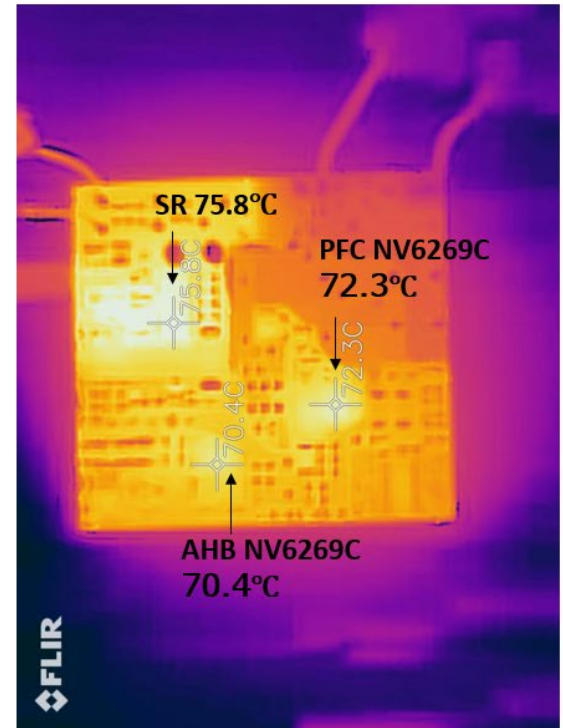



230Vac

# ZVS = Low EMI!

---

115Vac

230Vac

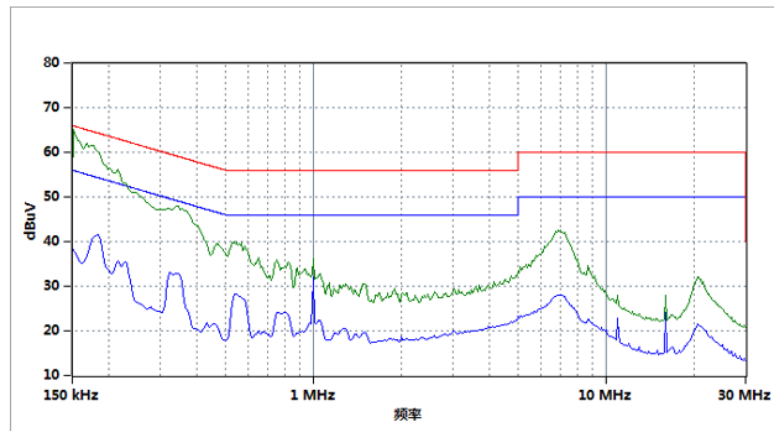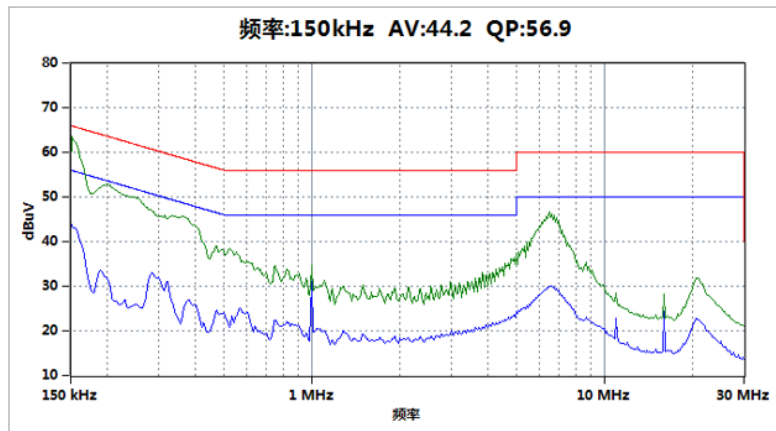

# Conclusions

---

- ✓ Existing 240W GaN chargers still have room for improvement (0.77 – 1.1 W/cc, 90.5% - 92% efficiency)
- ✓ Use Totem-Pole + AHB for highest efficiency, high frequency, ZVS, & smallest size
- ✓ NV6269C is an excellent GaN half-bridge building block IC, easy to use, small footprint, & reliable switching
- ✓ 240W-1C charger design using Totem-Pole + AHB + GaN Half-Bridge IC demonstrates 96% efficiency, 150cc size, & low EMI
- ✓ +4% to +5.5% higher efficiency vs existing designs!
- ✓ 29% to 52% smaller size vs existing designs!



# EVBs & Design Files Available!




240W 变压器绕线工艺:

客户	产品名称	日期
客户名称	客户名称	日期
客户材料	客户材料	客户材料
客户材料	客户材料	客户材料

序号	板头	长度	层数	漆包线	抽值、铁芯圈数规格	绕线方式
1	START	START	START	START	START	START

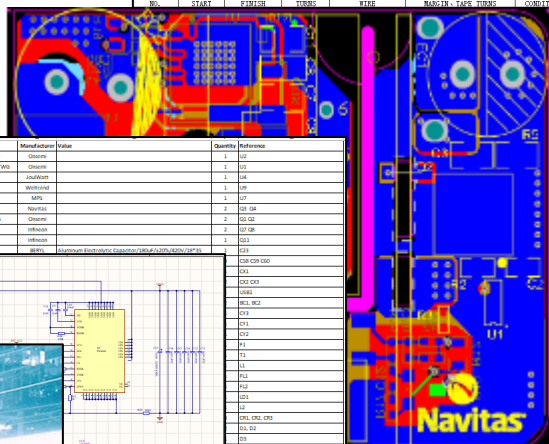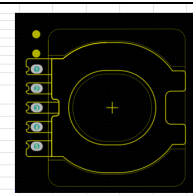

ID	Description	Component	Manufacturer	Value	Quantity	Reference
1	PFC Controller	UC2838B	ONSEMI		1	U1
2	Driver IC	MP1584MPW	ONSEMI		1	U2
3	AHB Controller	AV1234	ONSEMI		1	U3
4	USB PFC Controller	MP1584	ONSEMI		1	U4
5	SR Controller	MP1584	ONSEMI		1	U5
6	SR Controller	MP1584	ONSEMI		1	U6
7	PFC Controller	UC2838B	ONSEMI		1	U7
8	SR Controller	MP1584	ONSEMI		1	U8
9	SR Controller	MP1584	ONSEMI		1	U9
10	SR Controller	MP1584	ONSEMI		1	U10

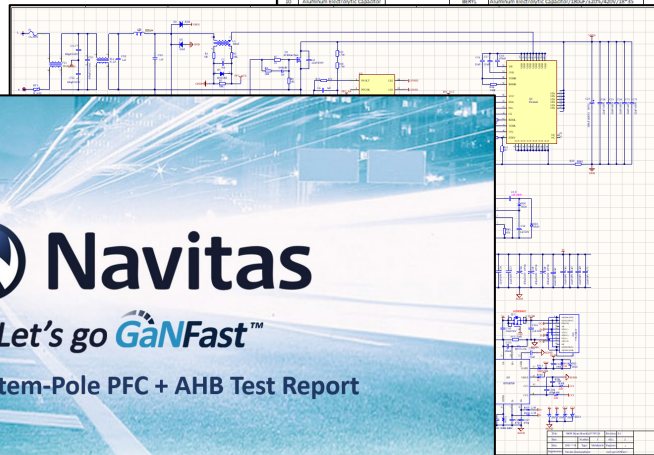

**Navitas**  
Let's go GaNFast™  
240W Totem-Pole PFC + AHB Test Report