



## GaN Power ICs at 1 MHz+: Topologies, Technologies and Performance

PSMA Industry Session, Semiconductors


Dan Kinzer, CTO/COO

[dan.kinzer@navitassemi.com](mailto:dan.kinzer@navitassemi.com)

March 29, 2017

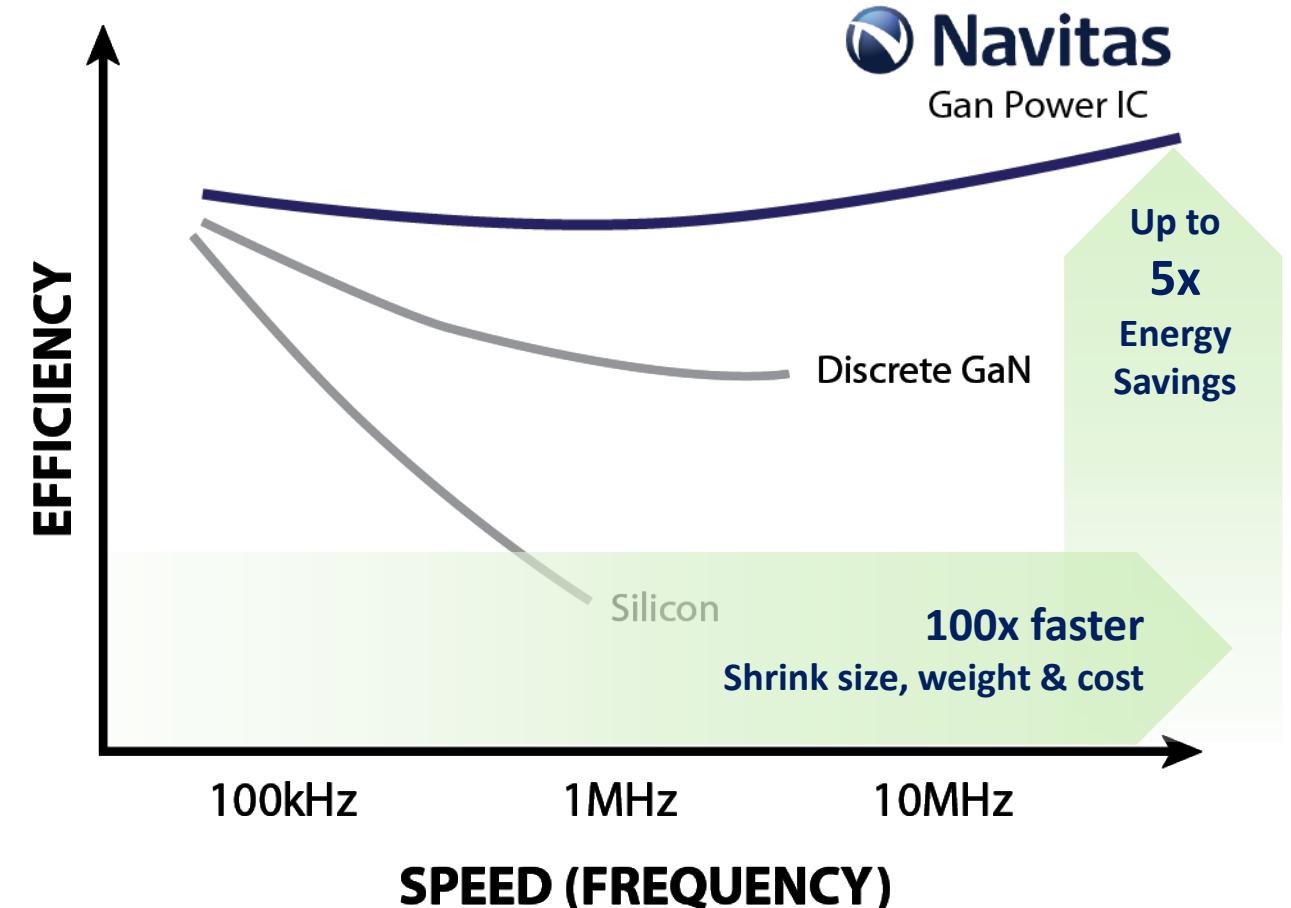
# Power Electronics: *Speed & Efficiency are Key*

- Speed enables *small size, low-cost* and *faster charging*
- Efficiency enables *energy savings*
- With Silicon or Discrete GaN power devices, you can get one **or** the other
- With GaN power ICs, you get **both at the same time** with unequaled **Speed & Efficiency**




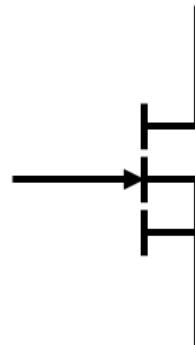
# World's First AllGaN™ Power ICs

**Fastest, most efficient  
GaN Power FETs**




- >10x faster than silicon
- >5x faster than cascoded GaN
- Proprietary design
- 5+ pending or issued patents

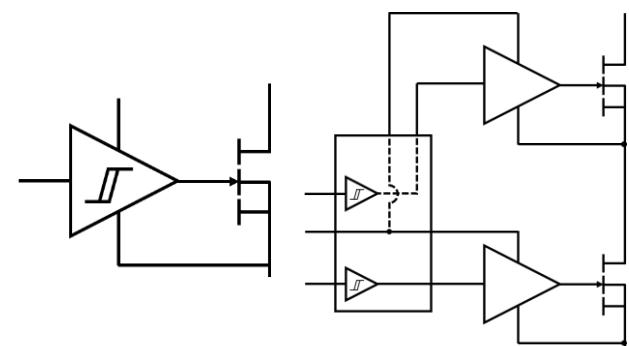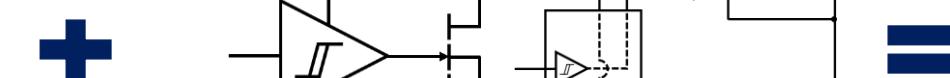*iDrive* First & Fastest  
Integrated GaN Gate Drivers



- >2x faster than any other gate driver
- Proprietary design
- 15+ pending or issued patents

**World's First  
AllGaN™ Power IC**



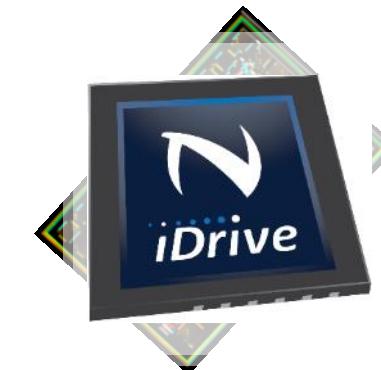


**Up to 40MHz switching, 5x higher density & 20% lower system cost**


# 27 MHz, 40 MHz...
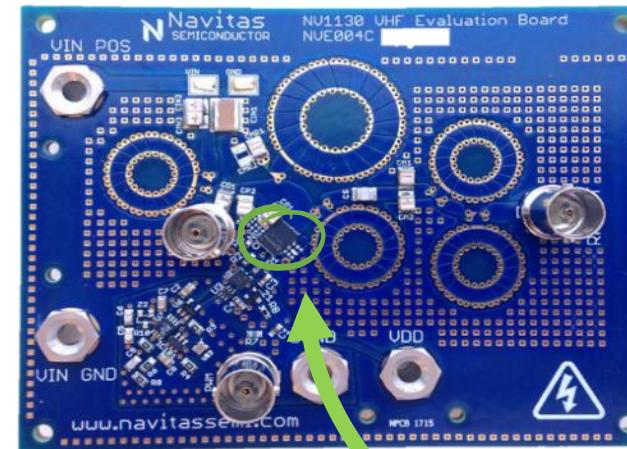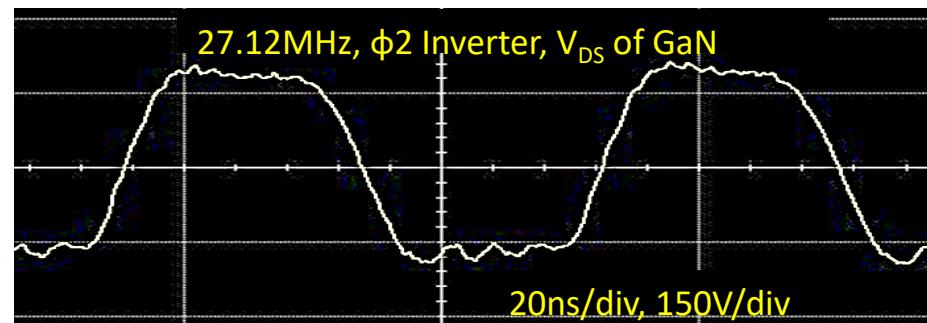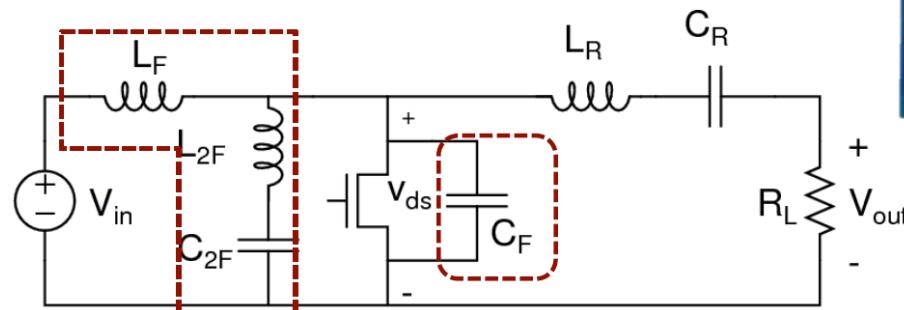
## Class Phi-2 DC/AC converter

- 50% less loss than RF Si
- 16x smaller package
- Air-core inductors
- Minimal FET loss
- Negligible gate drive loss




Power Loss Breakdown (Active Components)

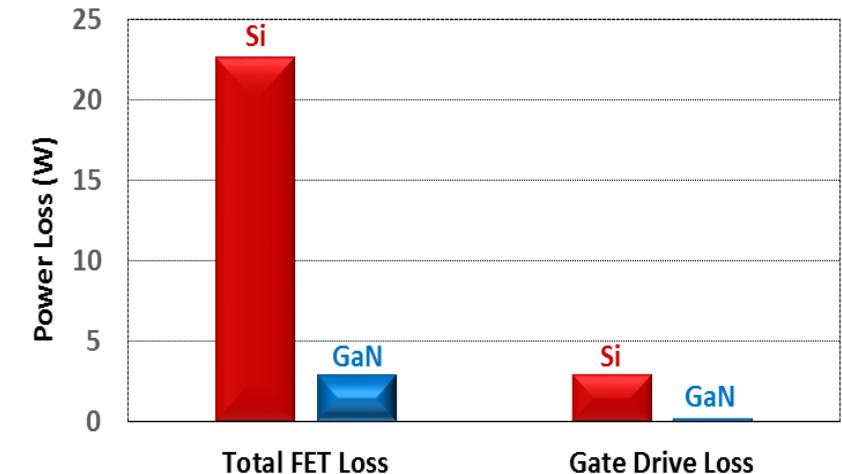

Technology	V	Pack (mm)	F <sub>SW</sub> (MHz)	Eff. (%)	Power (W)
RF Si (ARF521) 	500	M174 22x22	27.12	91%	150
Navitas	650	QFN 5x6	27.12	96%	150
			40.00	93%	115
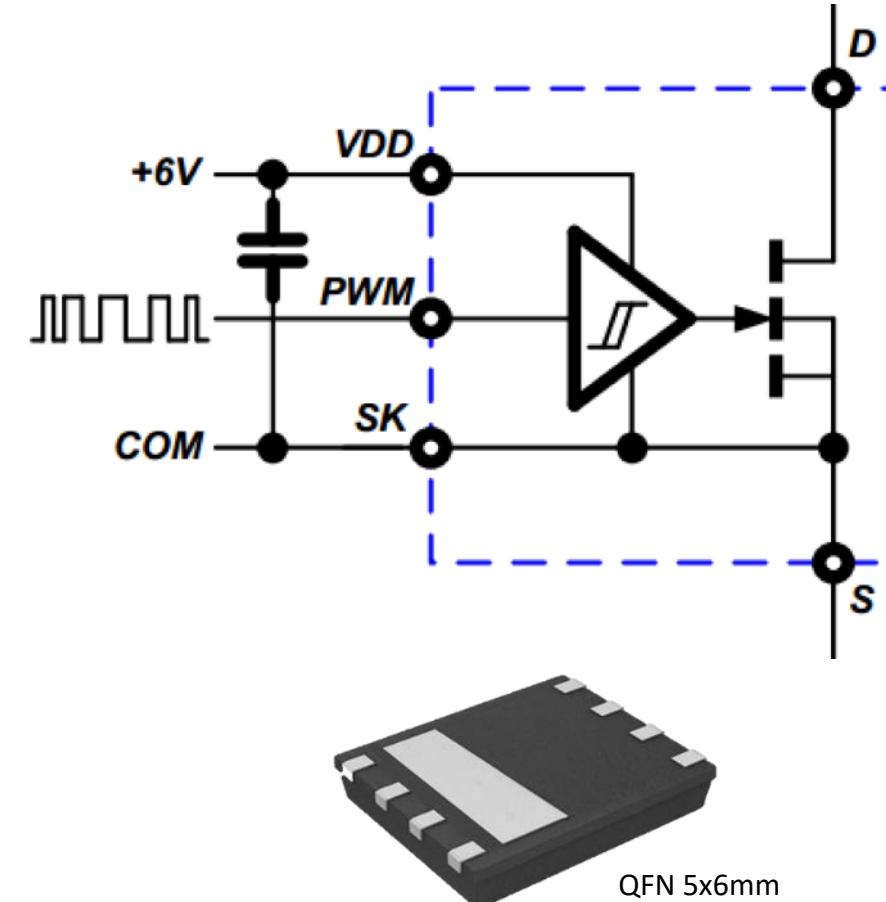
# Navitas GaN Power IC

- Monolithic integration
- 20X lower drive loss than silicon
- Driver impedance matched to power device
- Shorter prop delay than silicon (10ns)
- Zero inductance turn-off loop
- Digital input (hysteretic)
- Rail-rail drive output
- Layout insensitive






# Speed & Integration → Eliminate Turn-off Losses

## External drivers

- Just 1-2 nH of gate loop inductance can cause unintended turn-on
- Gate resistors reduce spikes but create additional losses

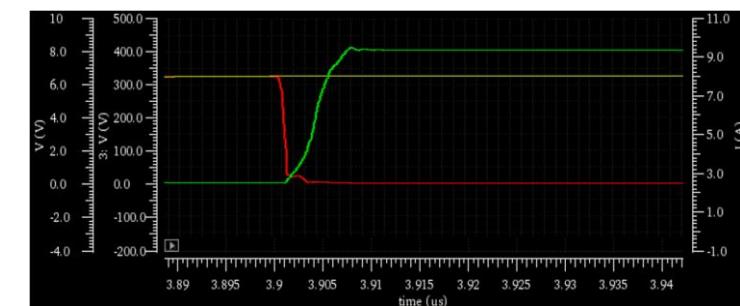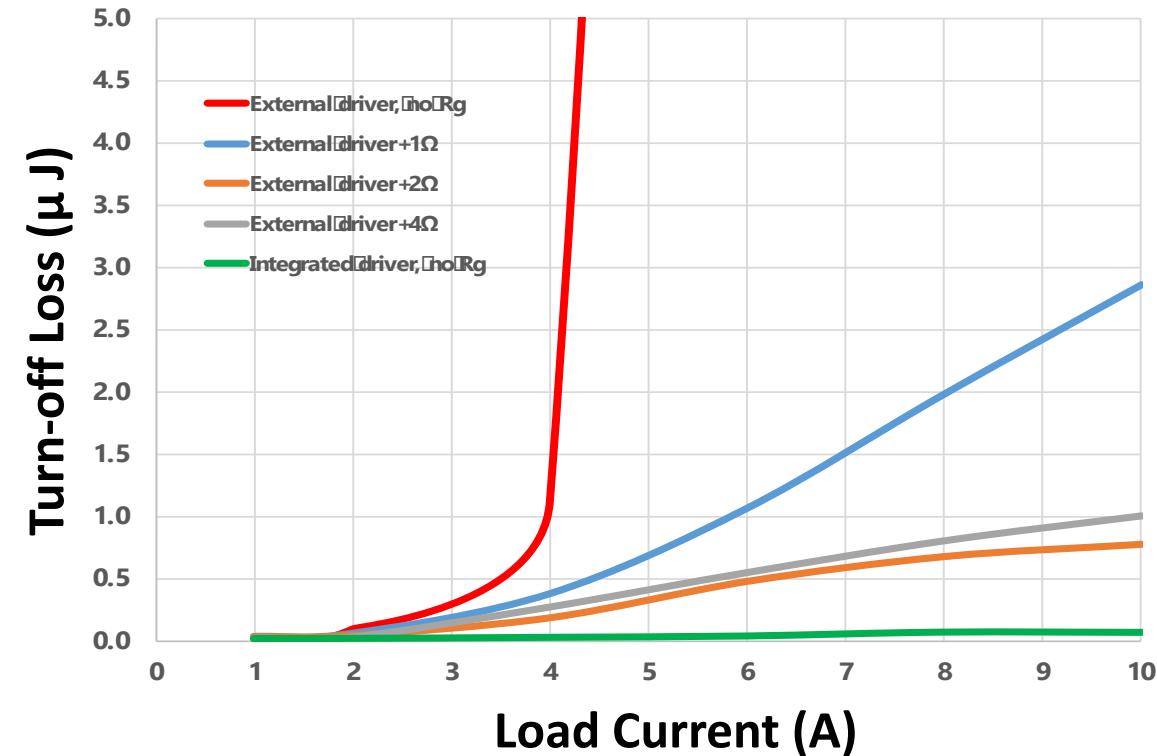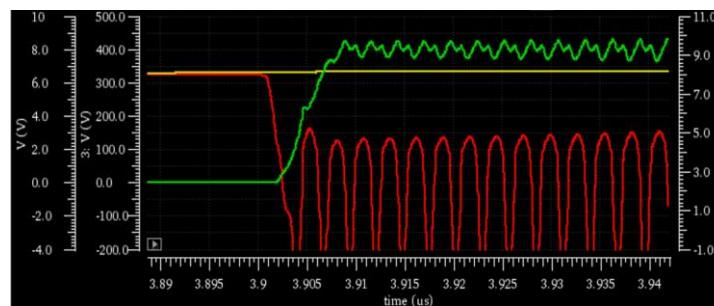
## Integrated GaN drivers (iDrive™)

- Eliminate the problem
- Negligible turn-off losses


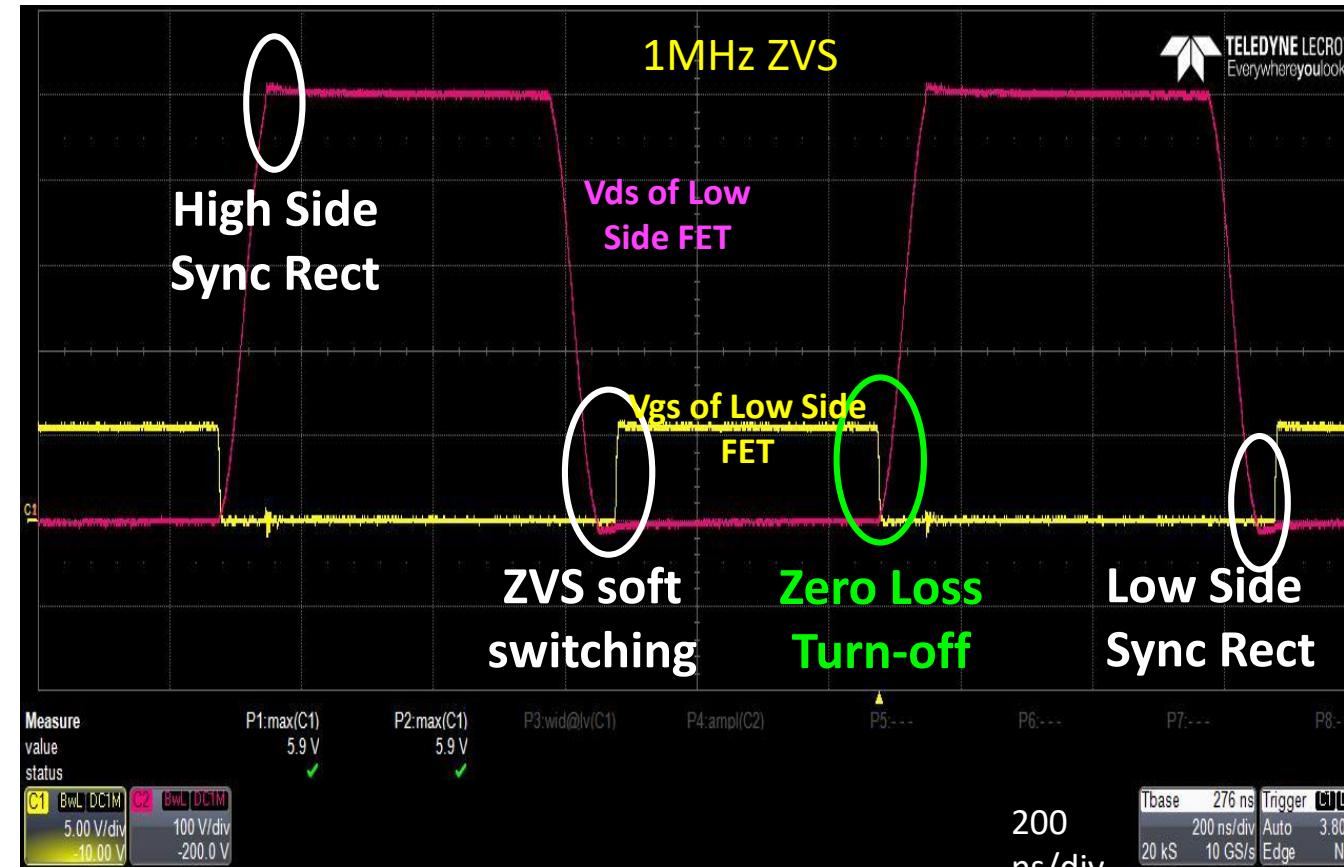
# GaN Power IC – Fast & Efficient

- No overshoots, No spikes, No oscillations , S-curve' transitions,
- Zero Loss Turn-on (Soft switching) Zero Loss Turn-off (Integrated Gate Drive)



# Wireless Power ... Accelerated

Existing Silicon-based multi-stage wireless power



AC-DC Adapter  
88% Efficiency

DC-DC  
94% Efficiency

Power Amplifier  
93% Efficiency

Wireless Transfer  
90% Efficiency




Single-Stage Amplifier  
90% Efficiency

- 650V GaN Power ICs
- 3-stages integrated in 1-stage
- 6.78MHz Operation
- High-Efficiency


- **Multi-stage Efficiency: 77%**
- **GaN-enabled single stage: 90%**
- **20% lower system cost**
- **3x faster charging**

# AC-RF Single Stage, Efficient & Cost-effective
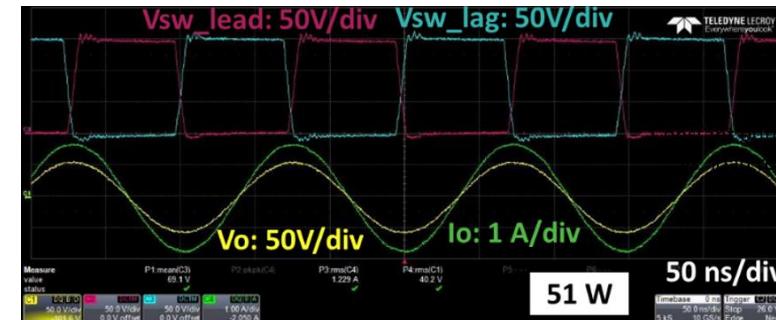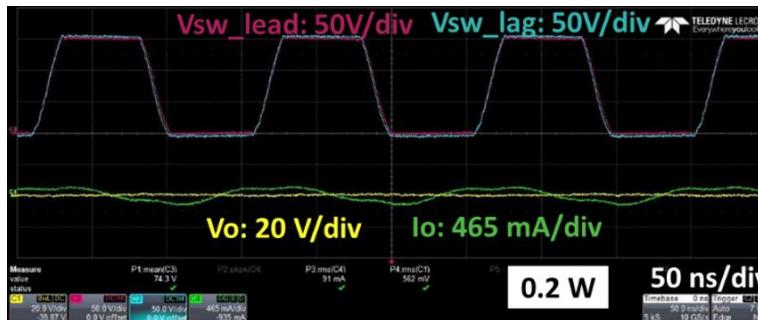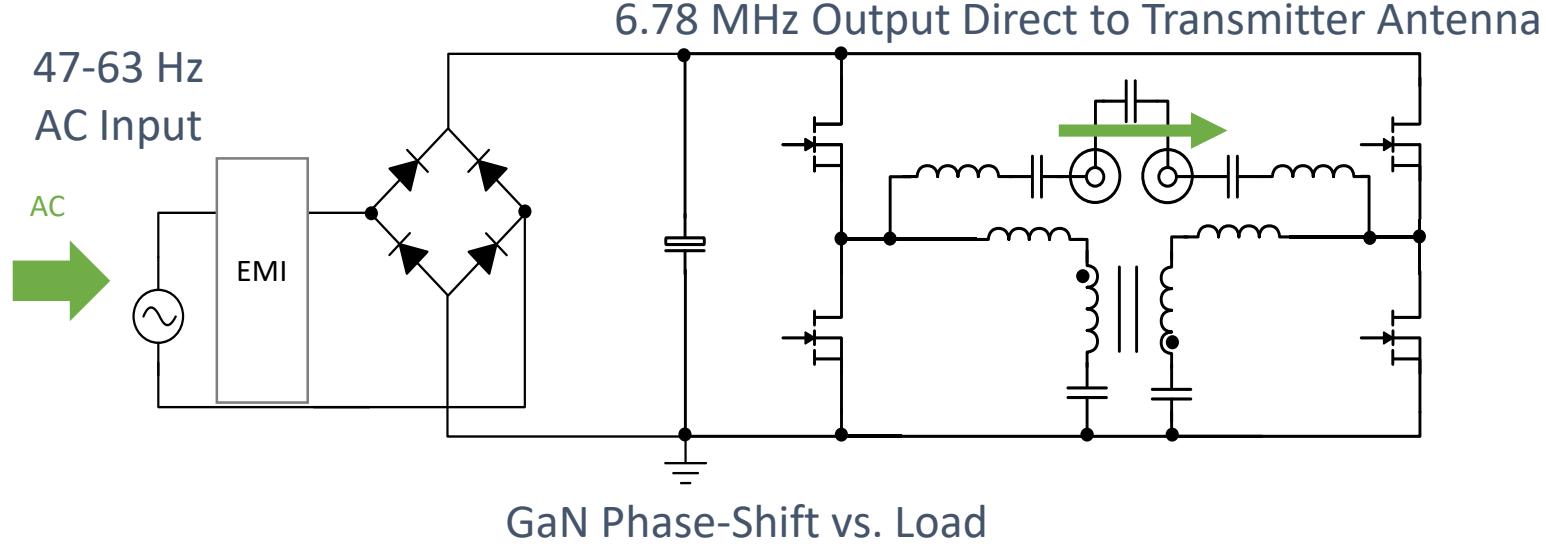
# 400V Phase-shifted Full Bridge with ZVS Coupled Inductors




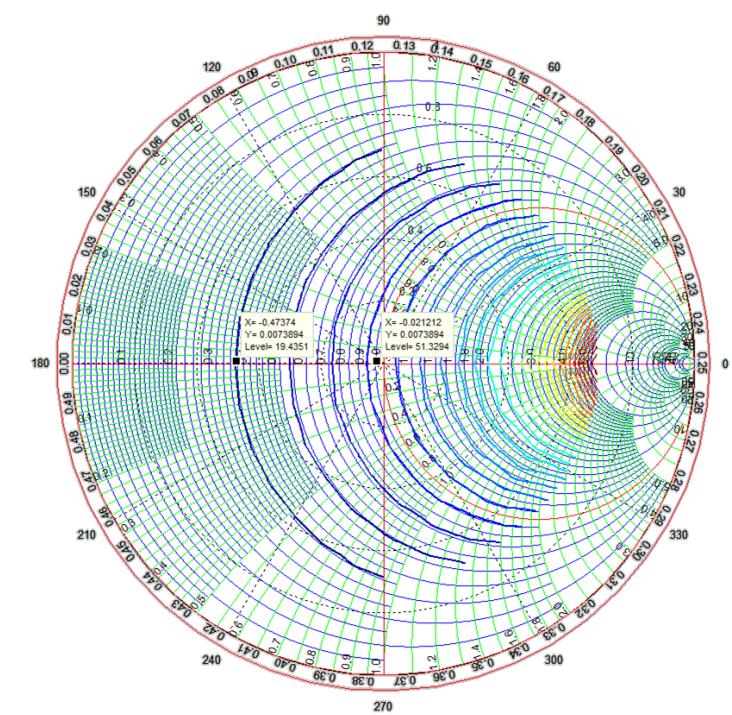Meets Key System Requirements:  
constant output current  
vs. load reactance


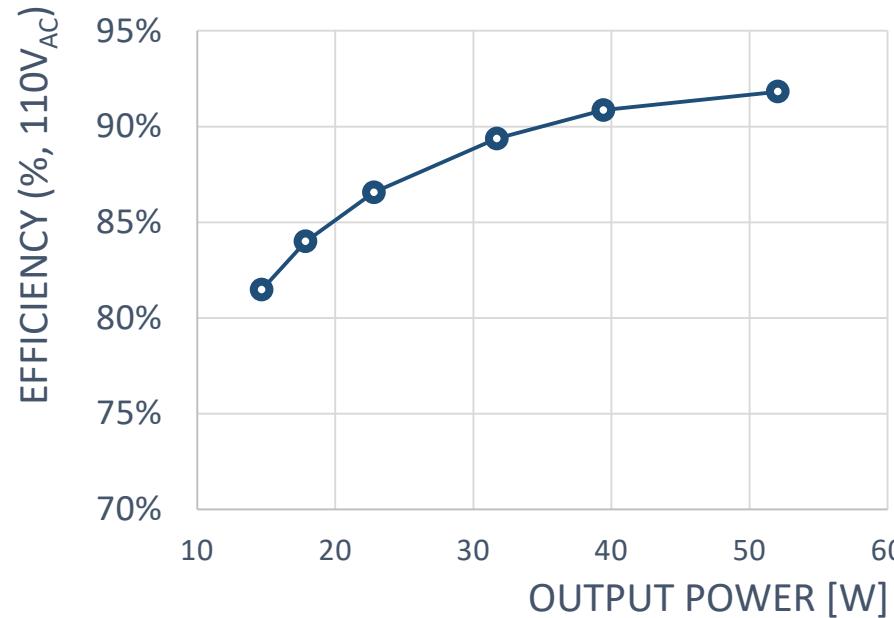
# Cool AllGaN, No Chance for Silicon


Efficiency from AC line to Transmitter Coil






50W Prototype Board:

- a) Significant potential for further integration (control & GaN Power IC)
- b) Thermal performance (50W):  
Max GaN Power IC  $T_{CASE} = 53^\circ\text{C}$

Device Speed

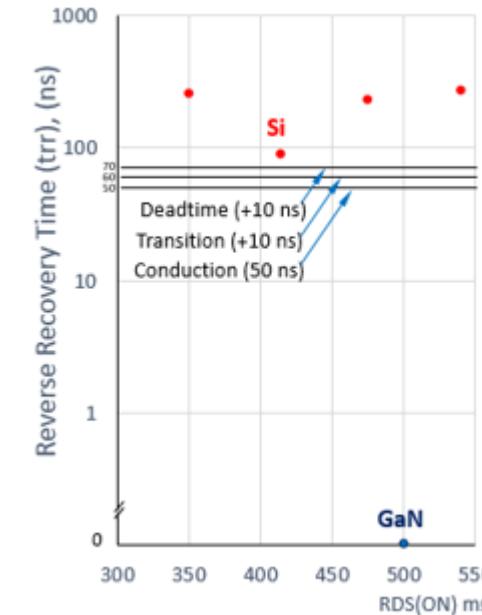

ZVS Current-Induced Loss

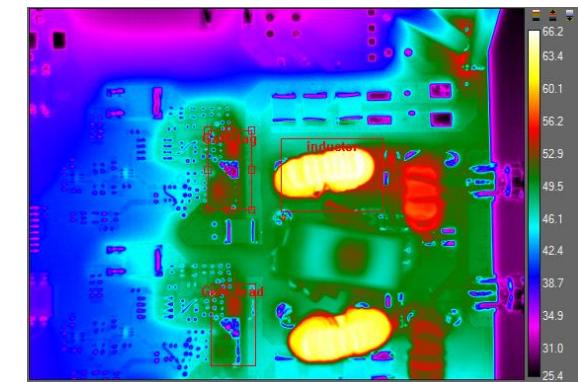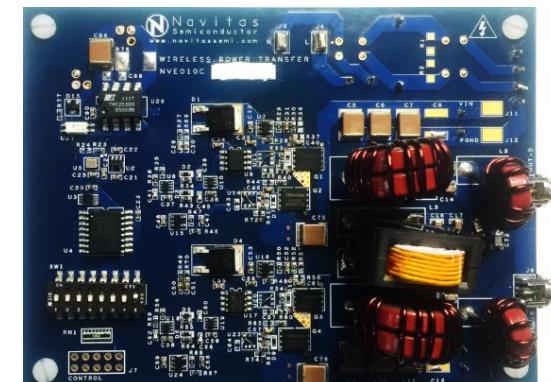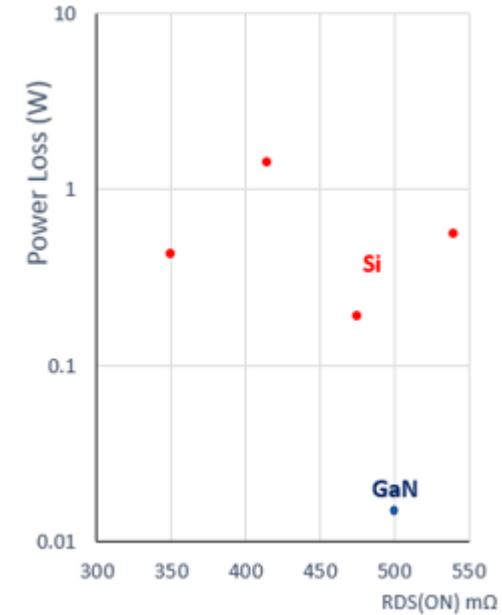


# The Road Ahead (as per APEC 2016...)





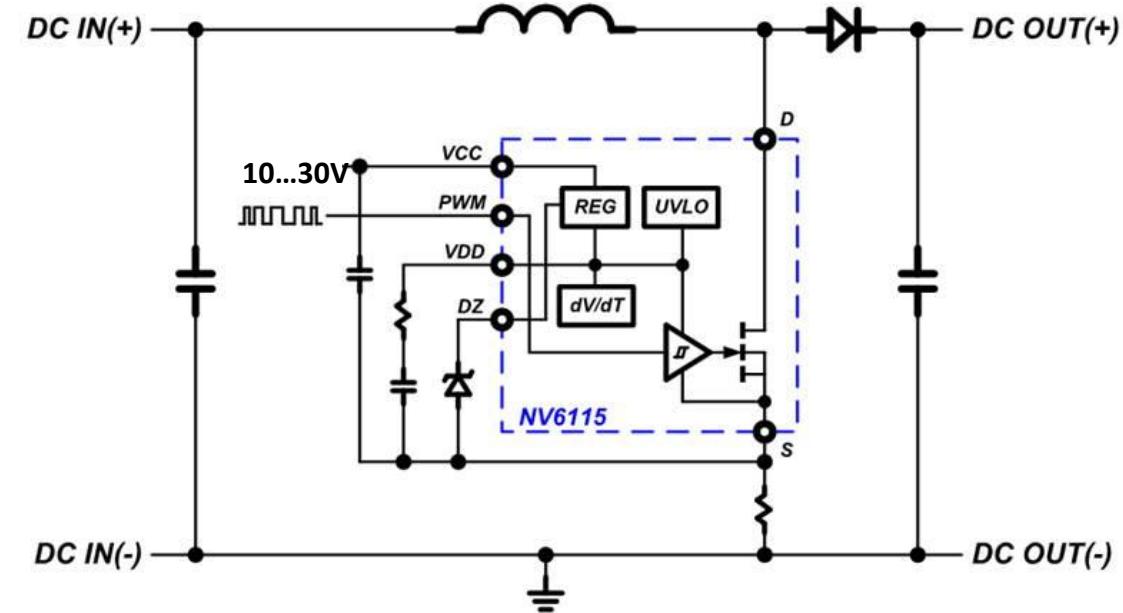
# GaN Power IC: Hi-Speed FET, Drivers & More

- Proprietary AllGaN™ technology
- Monolithic integration of GaN FET, GaN Driver, GaN Logic
- 650 V eMode
- 20x lower drive loss than silicon (<35 mW at 1 MHz)
- Driver impedance matched to power device
- Very fast (prop delay and turn-on/off of 10-20 ns)
- Zero inductance turn-off loop
- High dV/dt immunity (200 V/ns) with control
- Digital input
- Complete layout flexibility




QFN 5x6mm

# 150W AC-19V, ~300 kHz

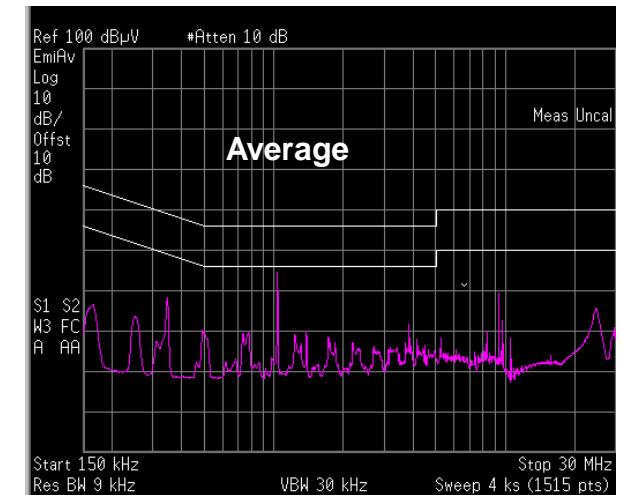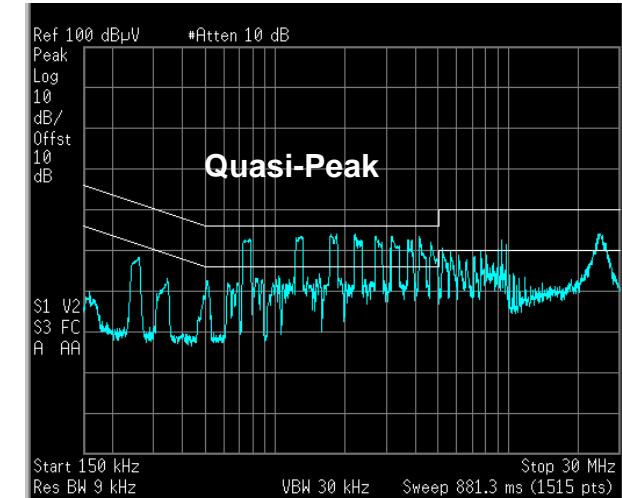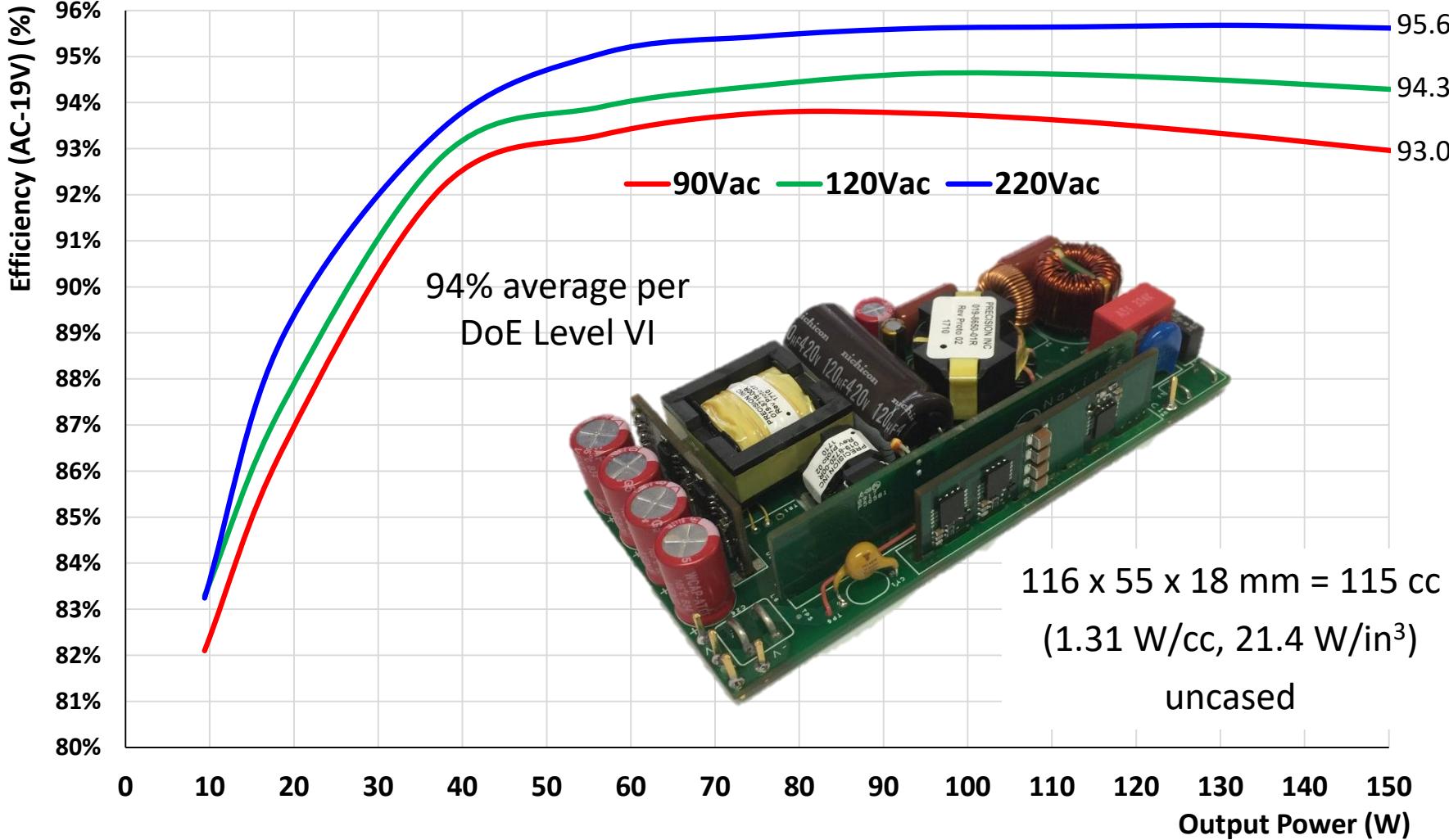


# 150W: Running Cool

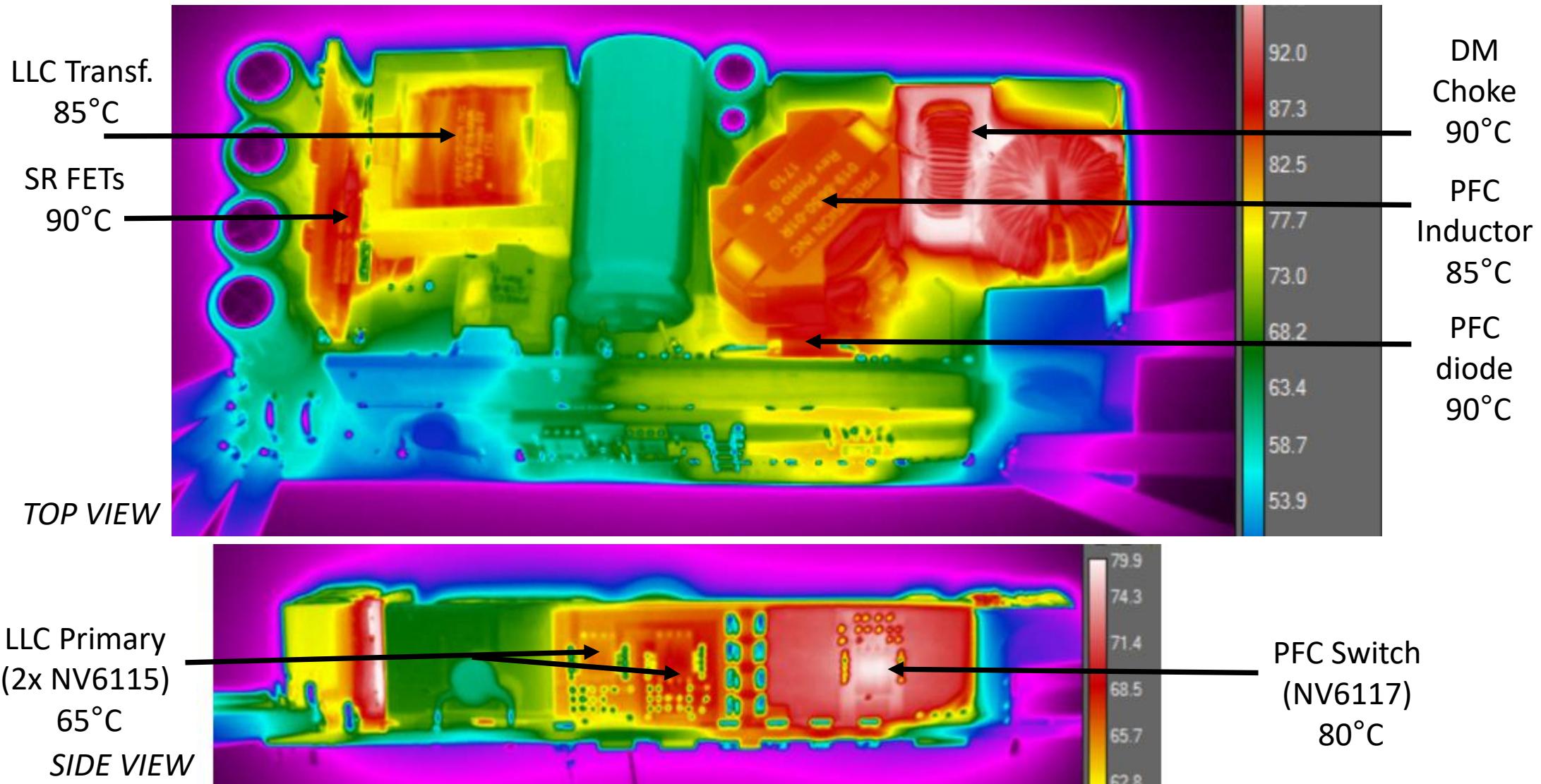


# AllGaN 2017: MHz 150W Totem-pole + LLC

PFC

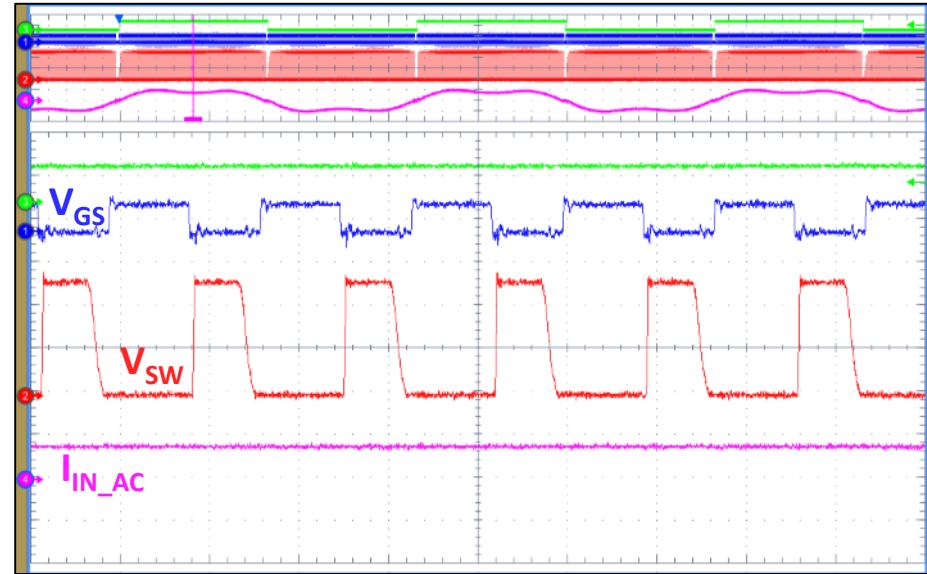


LLC

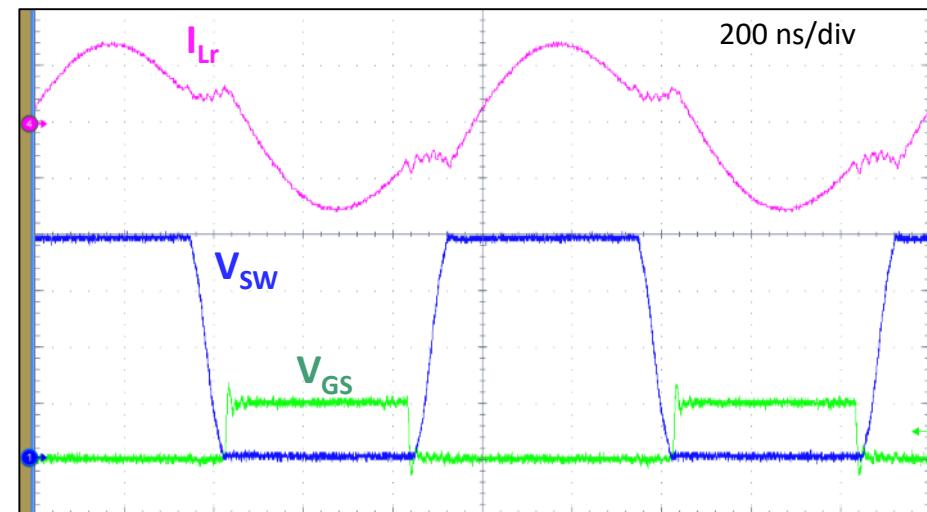


GaN-based  
Power Density  
= 35 W/in<sup>3</sup>

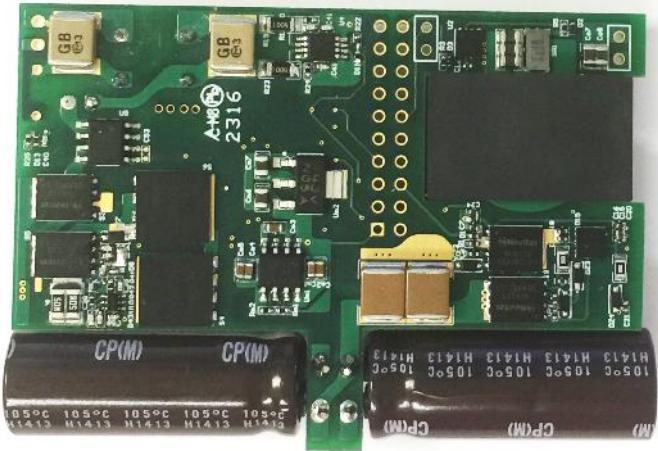
(Best commercial benchmark  
= 12W/in<sup>3</sup>)




**GaN based**

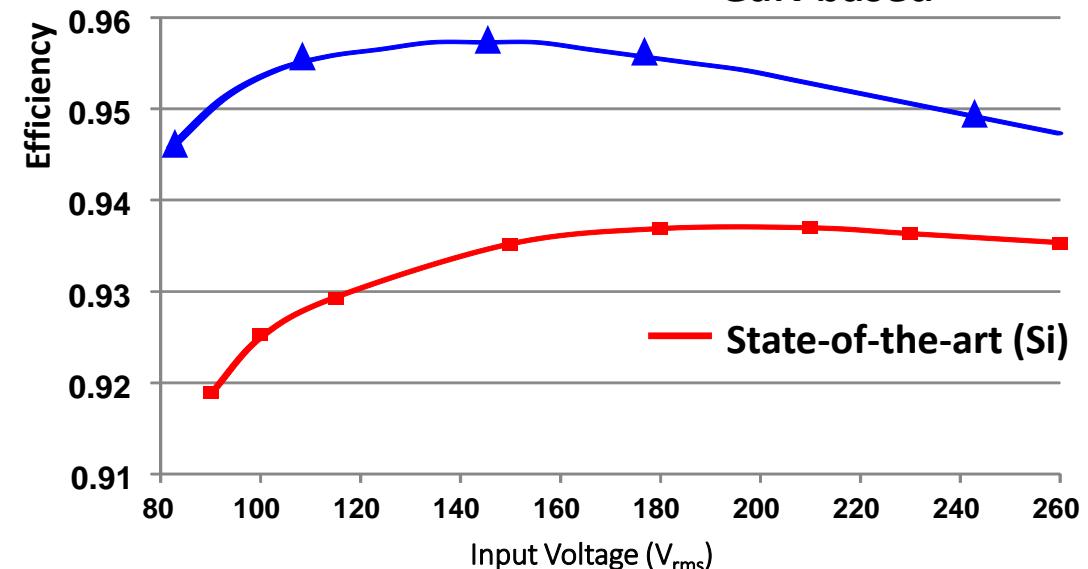


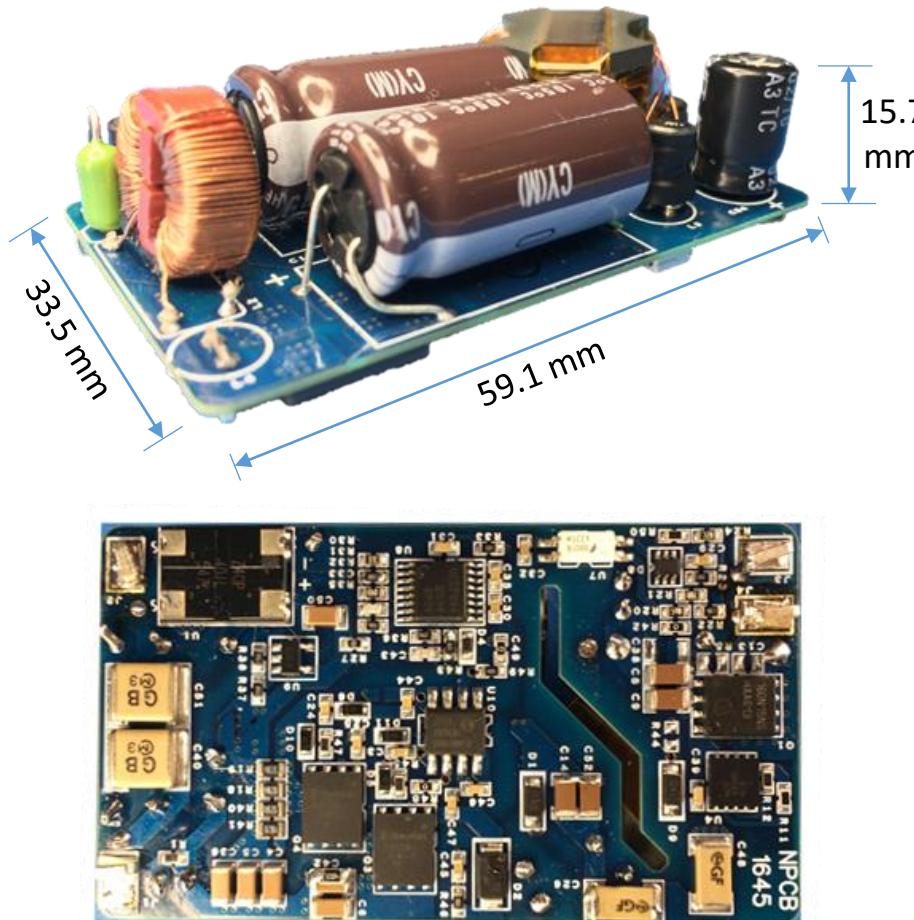
# 45W Active Clamp Flyback & AllGaN Power ICs



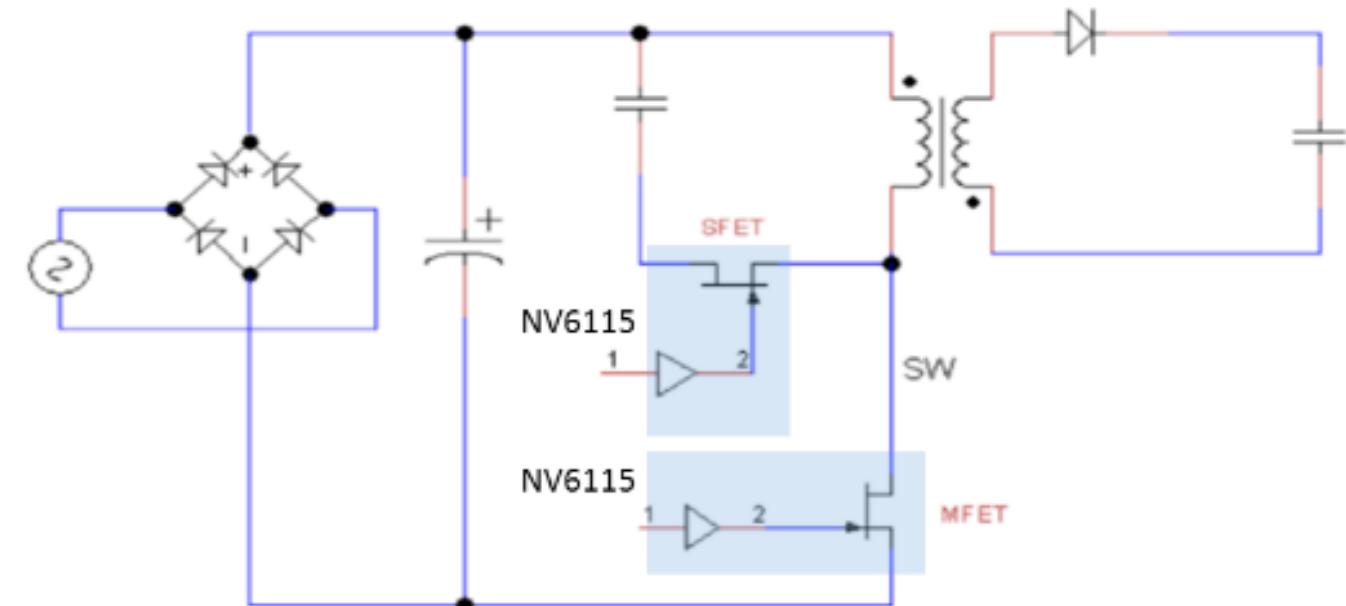- 94.5% efficient at 220 V (94.2% at 120 V<sub>AC</sub>, 93.1% at 90 V<sub>AC</sub>)
  - 23.7 W/in<sup>3</sup> density (uncased)
  - 15.7 mm profile



# 45W CrCM ACF Operation

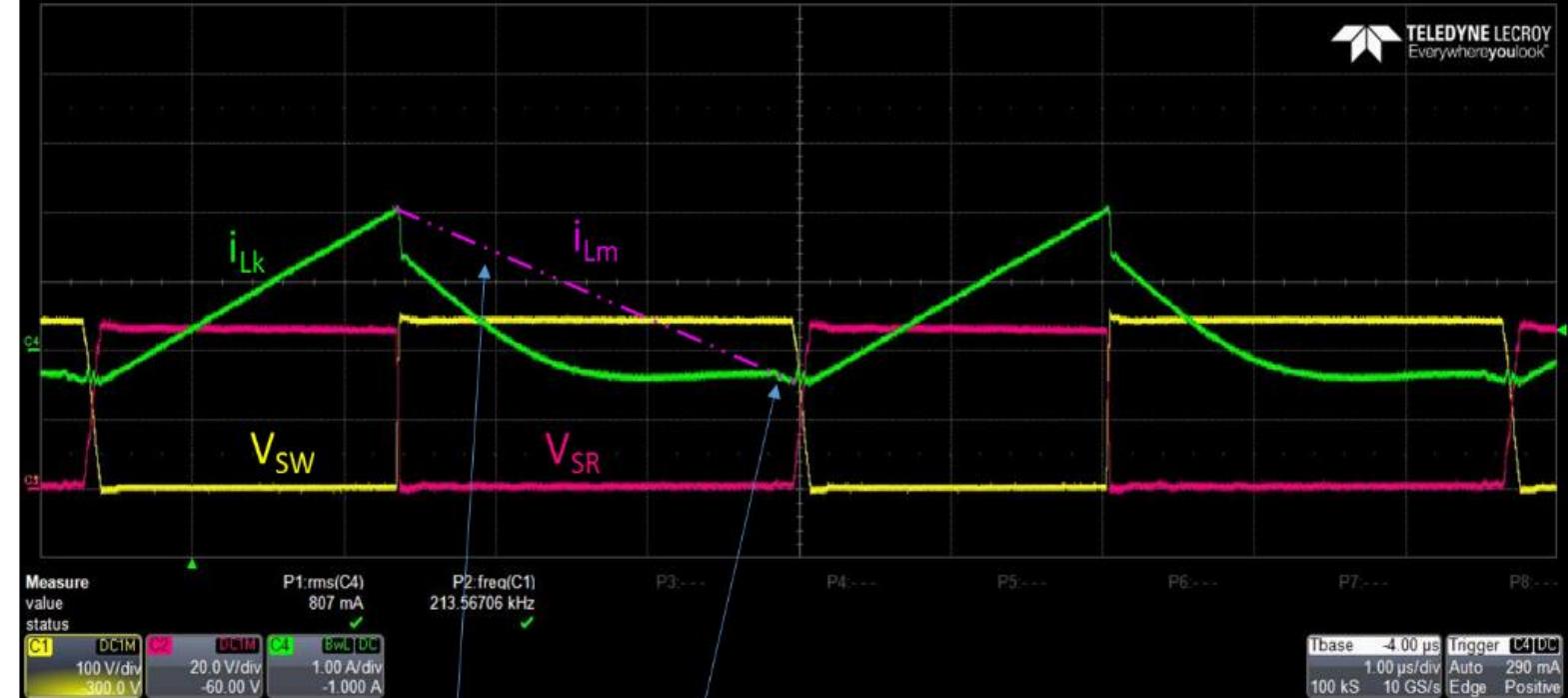
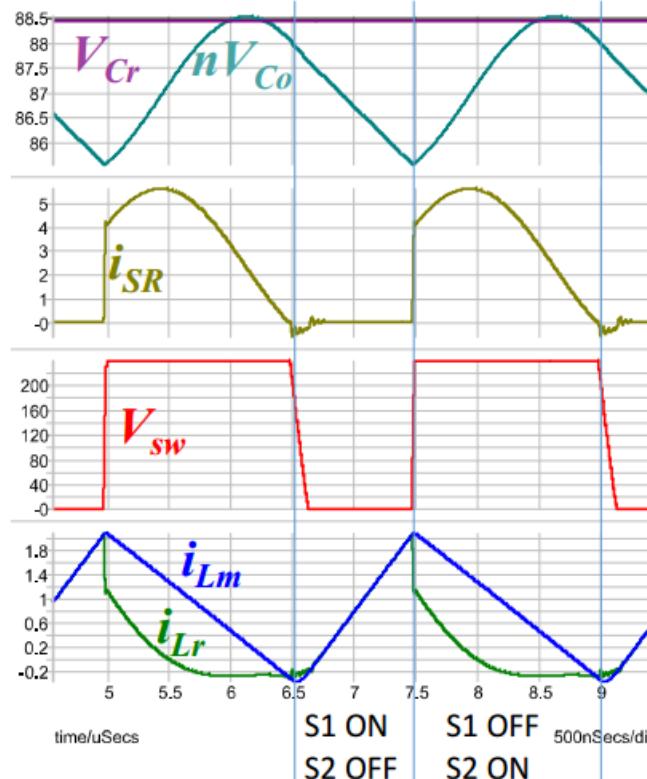


Magnetizing current (drawing)

Inductor current merges with magnetizing current, achieves SR ZCS turn-off

- Switch-node voltage ( $V_{SW}$ ), SR FET voltage ( $V_{SR}$ ), leakage current ( $i_{LK}$ ) and magnetizing current ( $i_{Lm}$ )
- 120V<sub>AC</sub>, 0.2A load,  $F_{SW} = 210\text{kHz}$ , Circulating Current minimized using Secondary Resonance
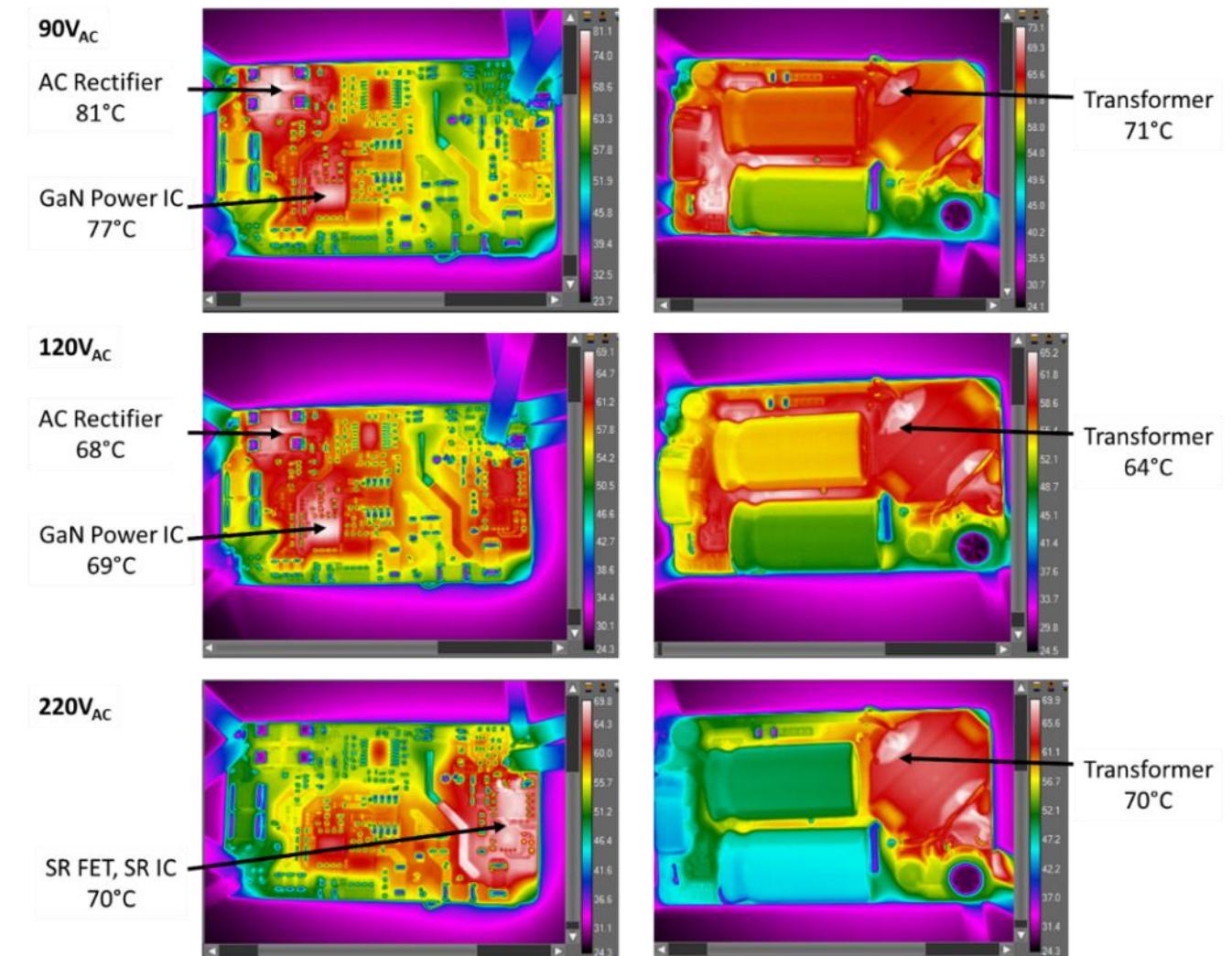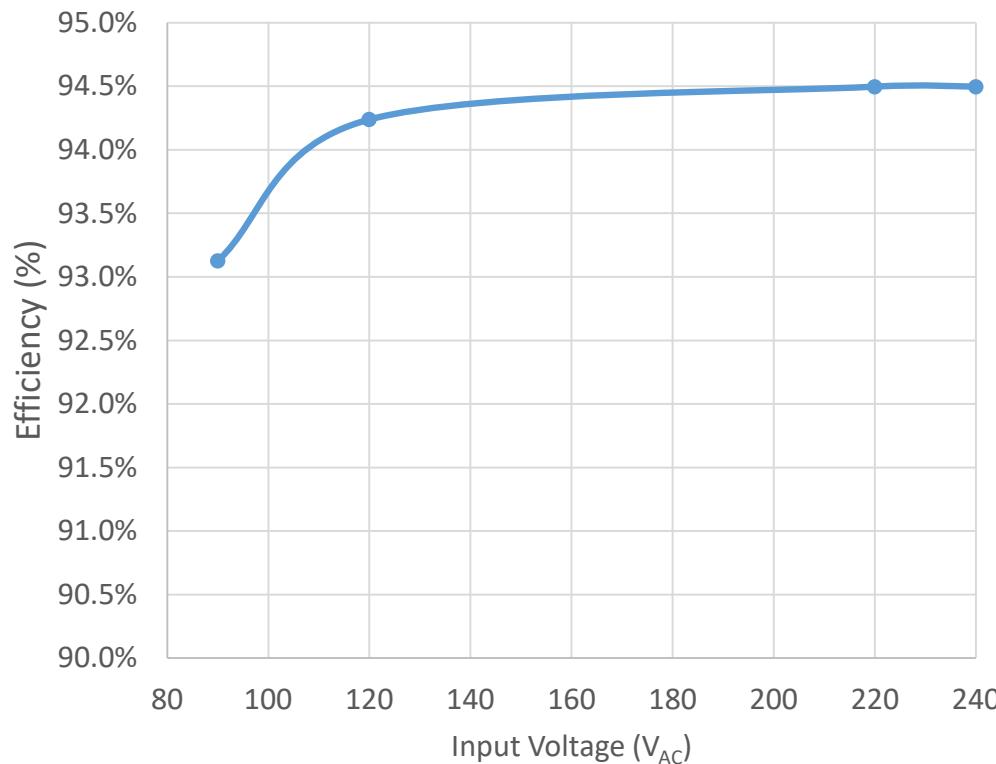
# 45 W ACF: High Efficiency, Cool Temperatures



# 45W → 65W ACF


Just 13% longer for 44% more power

$$45W = 59.1 \times 33.5 \times 15.7 \text{ mm} = 24 \text{ W/in}^3 \text{ (uncased)}$$

2x NV6115 (160mΩ)




45W

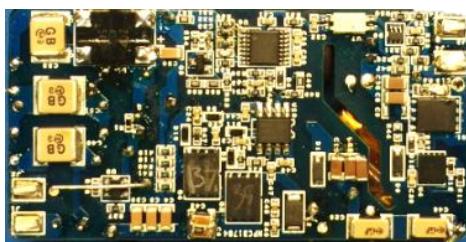


65W

$$65W = 66.7 \times 33.5 \times 15.7 \text{ mm} = 30 \text{ W/in}^3 \text{ (uncased)}$$


1x NV6115 (160mΩ) + 1x NV6117 (110mΩ)

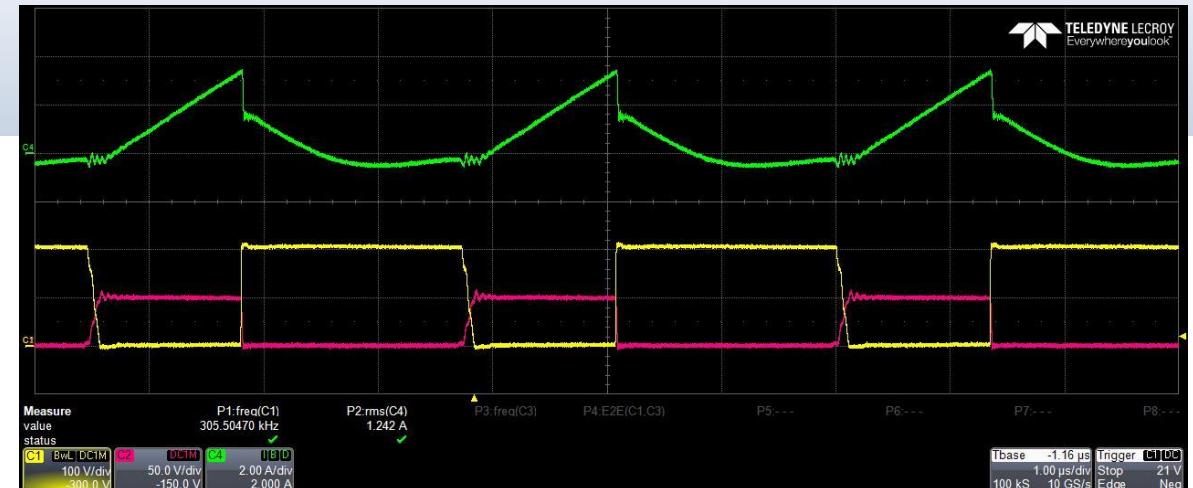

ACF switching waveforms, 300 kHz

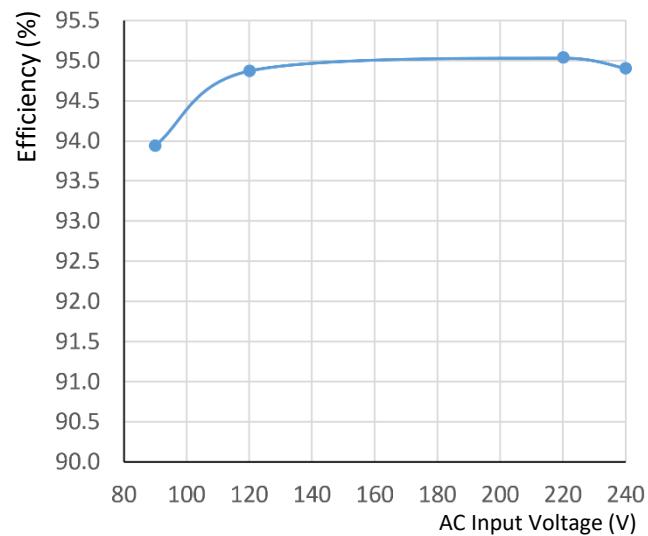


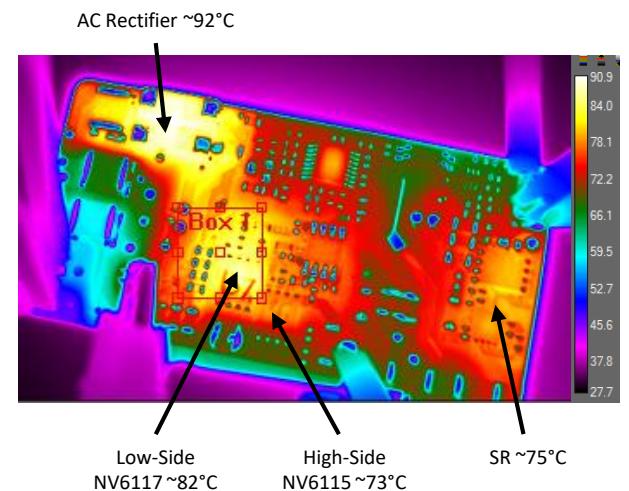65W Efficiency (*excluding EMI*) vs. AC line  
(25°C ambient, no airflow, full load)




65W Thermal Performance  
(90VAC, 25°C ambient, no airflow, full load)


# 650V Half-Bridge AllGaN™ Power IC

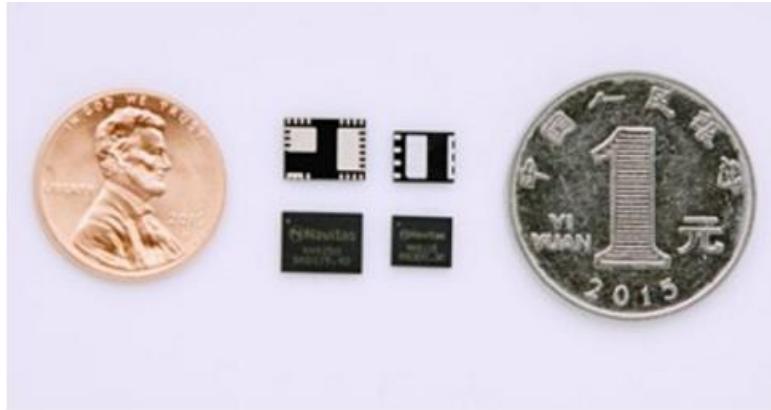

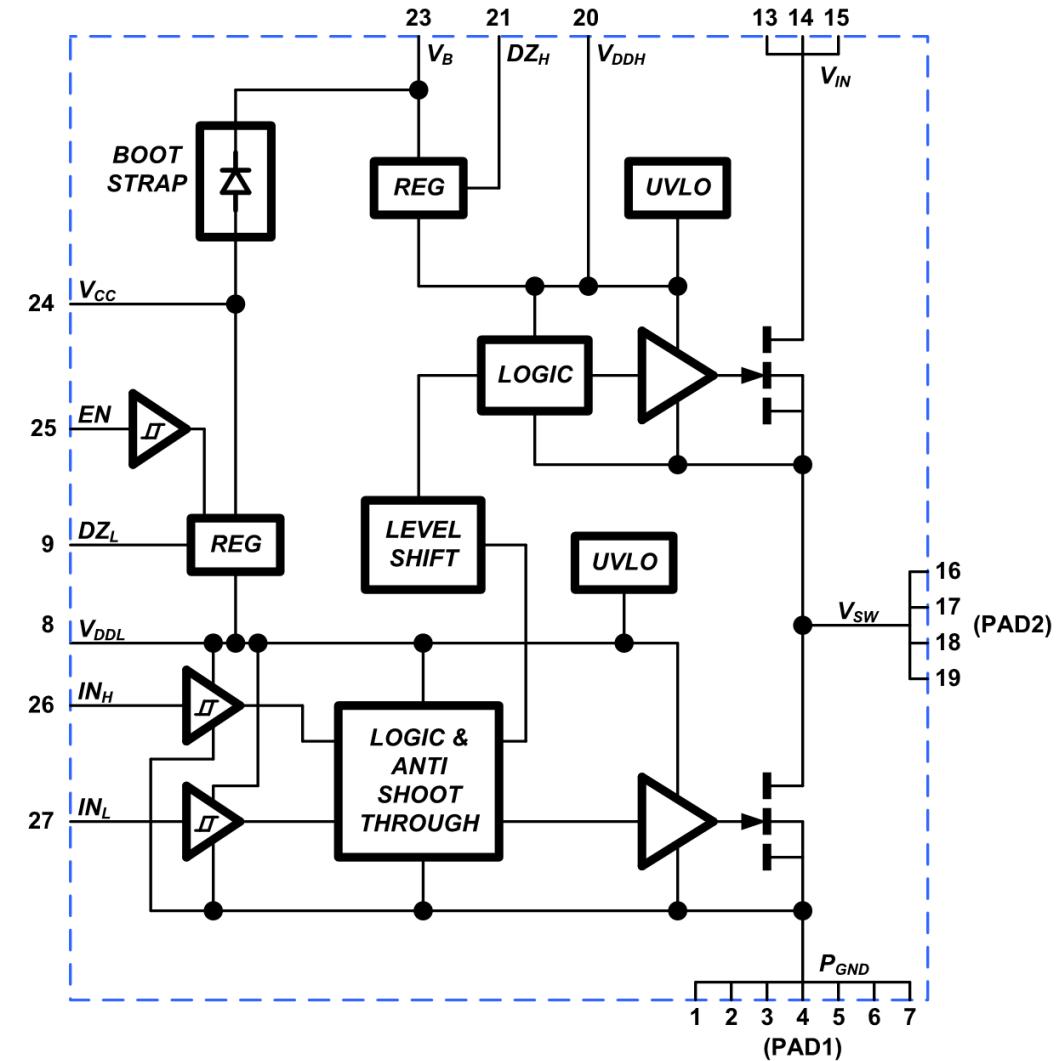
- Proprietary AllGaN™ technology
- Monolithic integration of 650V eMode GaN FET, driver, logic
- Internal level-shift, bootstrap
- Ground-referenced, digital input
- High dV/dt immunity (200 V/ns)
- Zero inductance turn-off loops
- ESD, UVLO, shoot-through protection
- Flexible topologies: Active Clamp Flyback, Half-Bridge, LLC, etc.



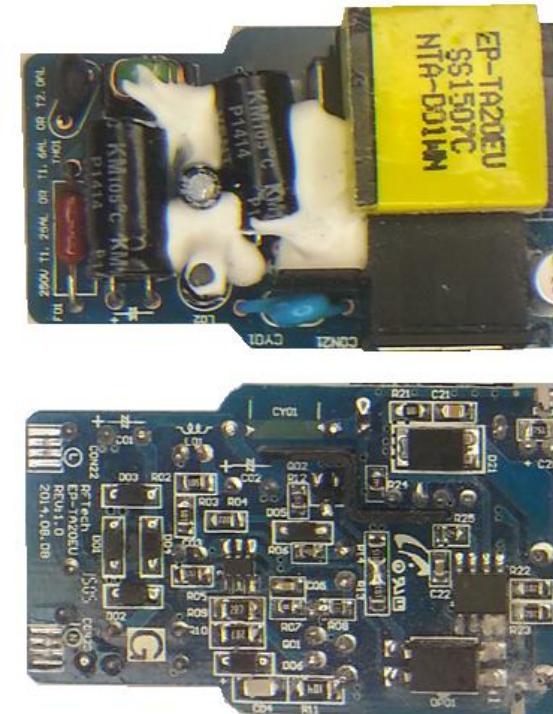
# 66% Higher Power with Half-Bridge GaN Power IC



a) Original 15 W AC charger case


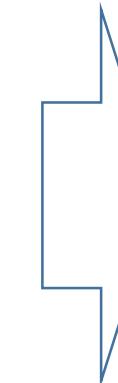


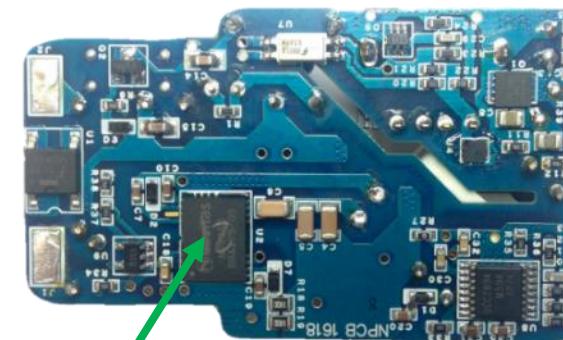b) Original 15 W, Si-based QR Flyback, ~100 kHz




c) Upgraded 25 W, Half-Bridge GaN Power IC ACF, ~400 kHz

# 25W Cool Thermals (12.5V, 2A)

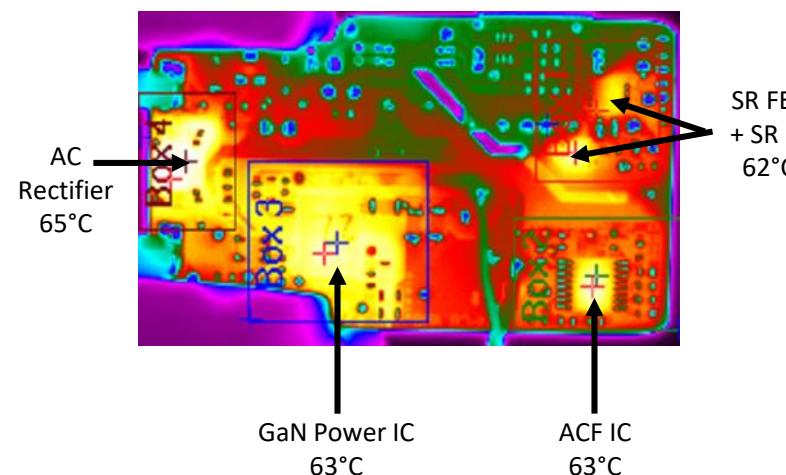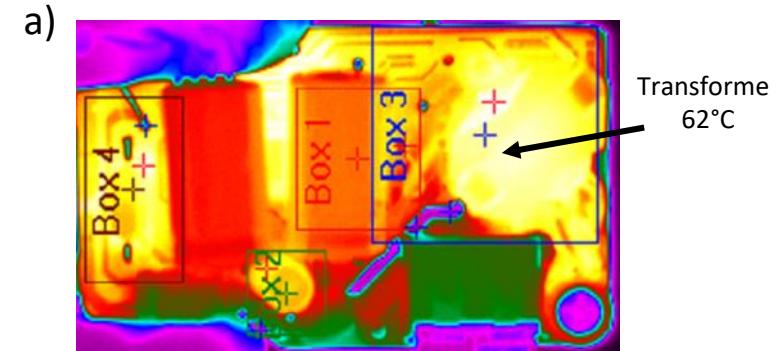

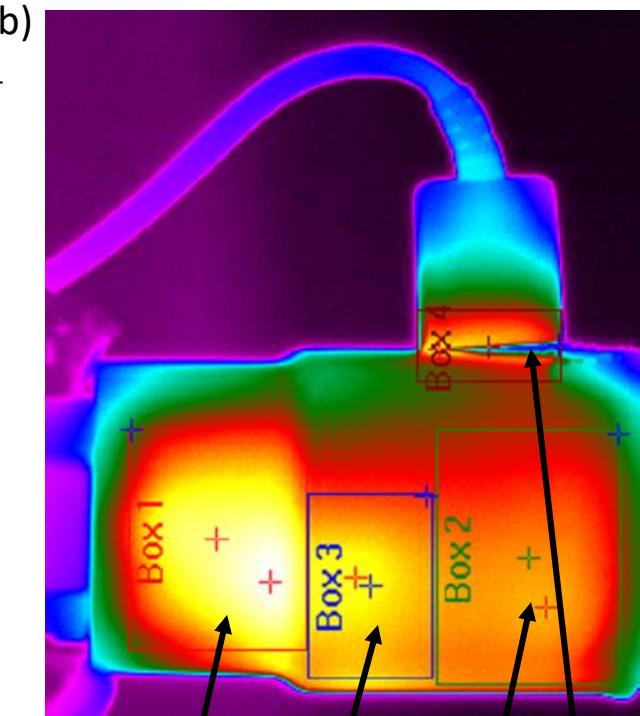
a) No case, 25°C ambient, full load, 90 V<sub>AC</sub> input, no heatsinking.




b) Cased, 25°C ambient, full load, 90 V<sub>AC</sub> input, no heatsinking.
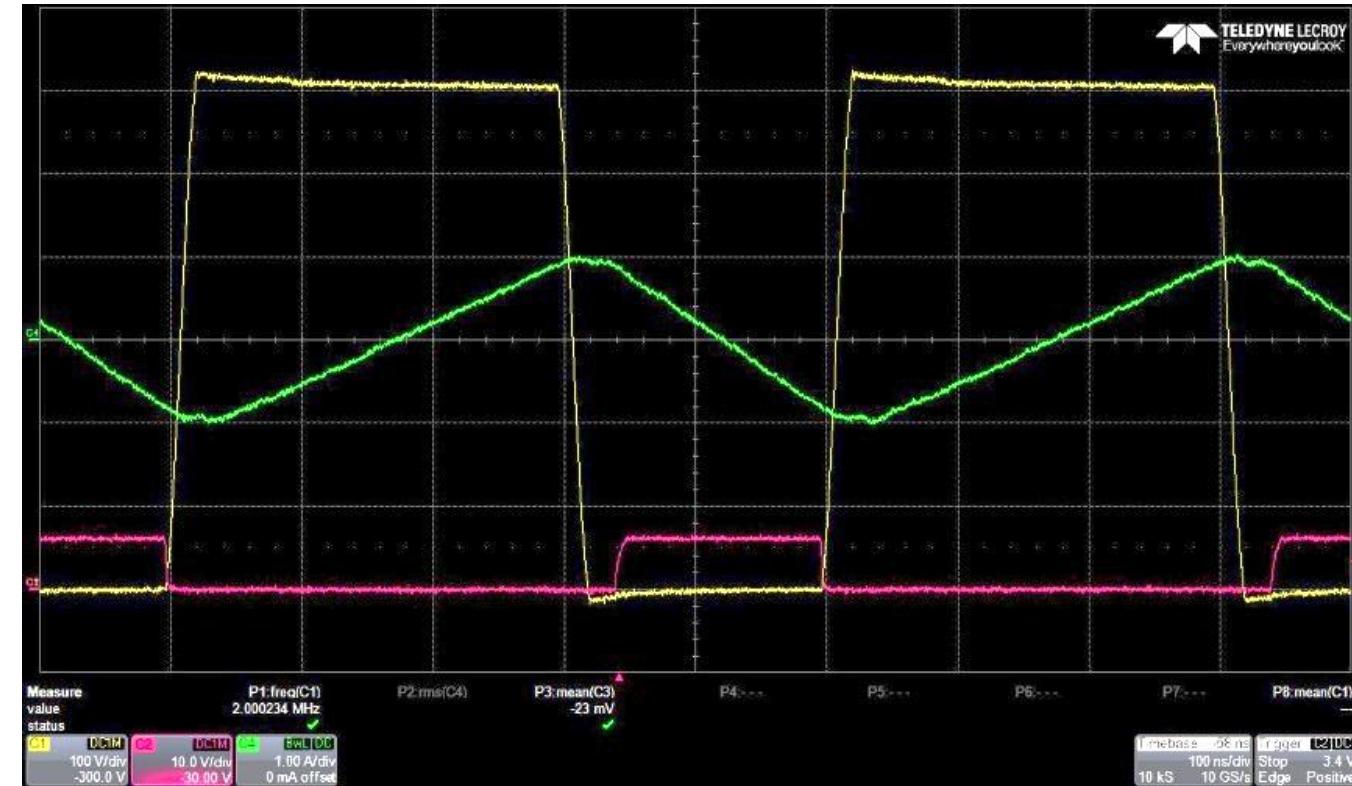
# Clean 600V ZVS switching at 2 MHz

- Demonstration board with half bridge AllGaN™ Power IC driving an LC resonant load
- Nearly perfect, loss-free half bridge switching up to 650V with a single part
- Only 5V PWM logic signals are needed
- No diode recovery losses
- No turn-on losses
- Nearly zero turn-off losses



# 1 MHz, 25 W ACF – Next Step

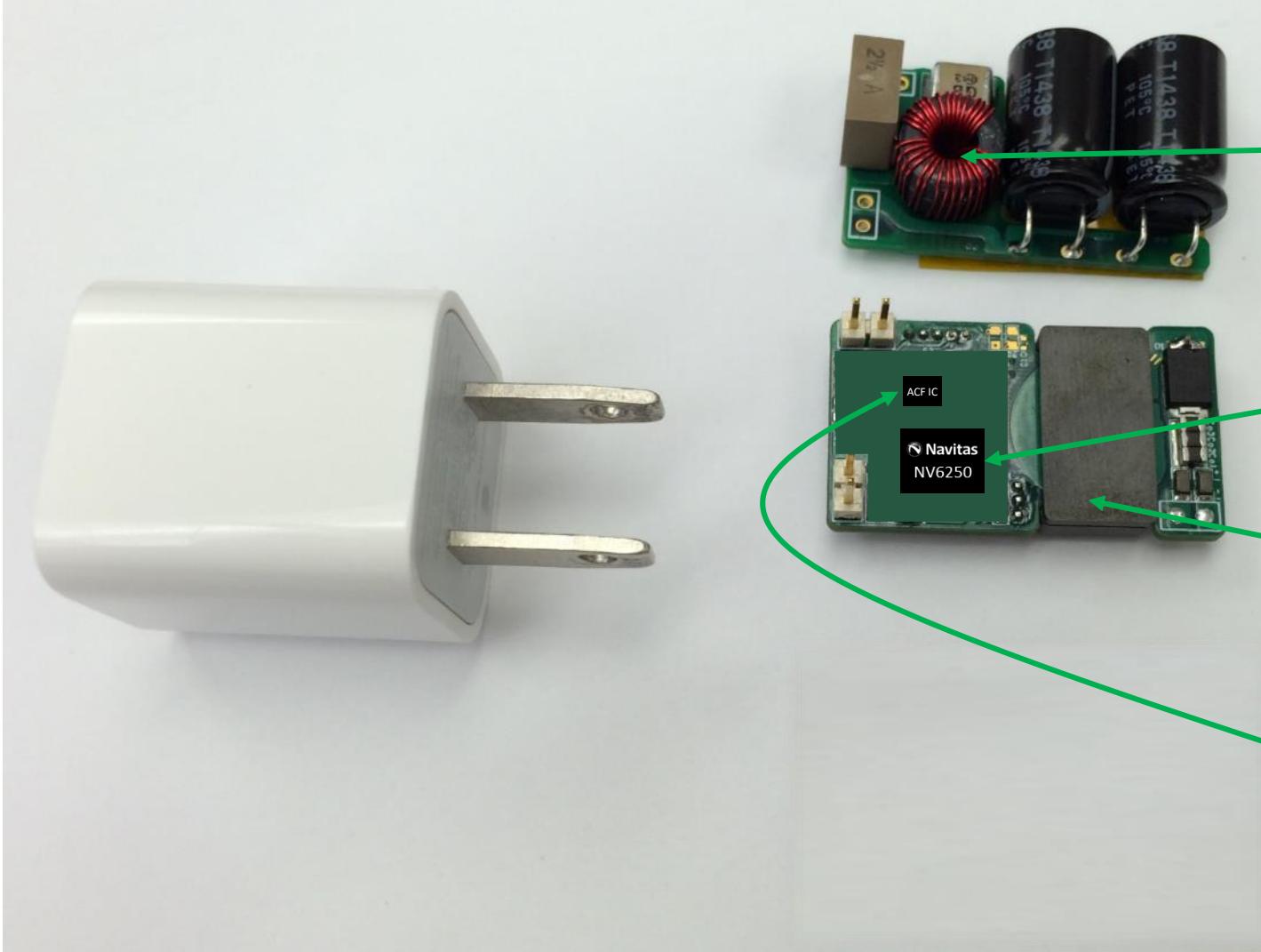


- Single-stage EMI
- 1x Navitas Half-Bridge GaN Power IC
- Planar transformer
- ACF IC




# MHz+ 25 W ACF Prototype Performance

$F_{sw}=1.5\text{MHz}$

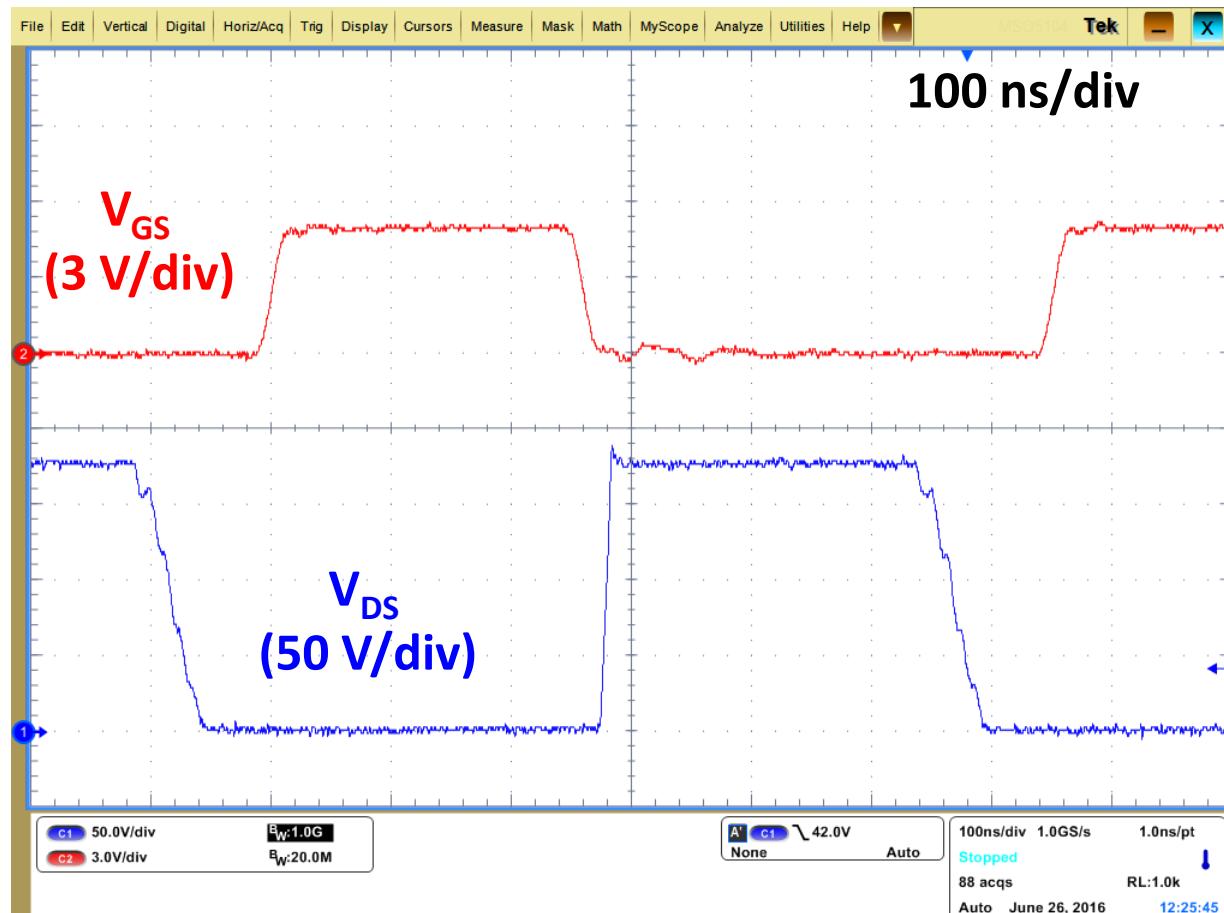



Efficiency vs. Load

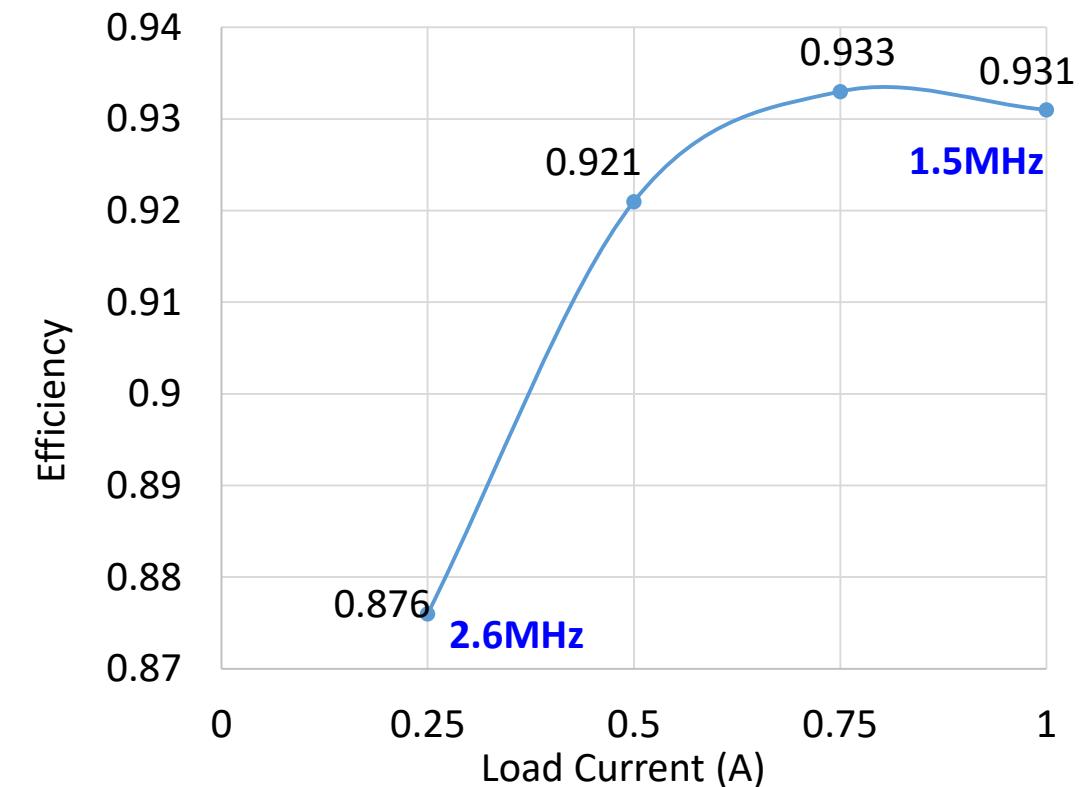

\* Exclude bridge and EMI filter loss


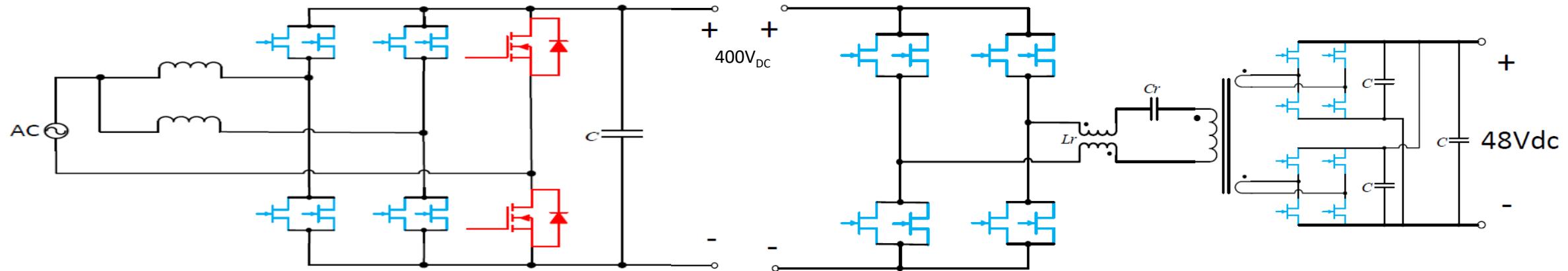
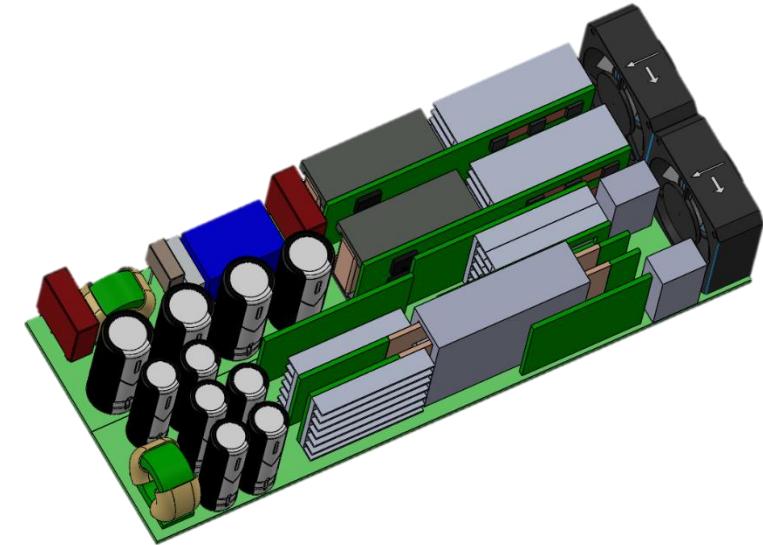
# 1 MHz, 3.2 kW Server Supply – 65 W/in<sup>3</sup>

- 220 V<sub>AC</sub> (47-63 Hz) to 48 V, 3.2 kW
  - Target > 97.5% efficiency (<80W loss)
  - >99% efficiency demonstrated on PFC alpha version
- Multi-phase Totem-Pole CrCM
  - Variable frequency interleaving (500 kHz – 1.5 MHz)
- 2-phase full-bridge LLC with full-bridge SR
  - Fixed-frequency interleaved 1 MHz



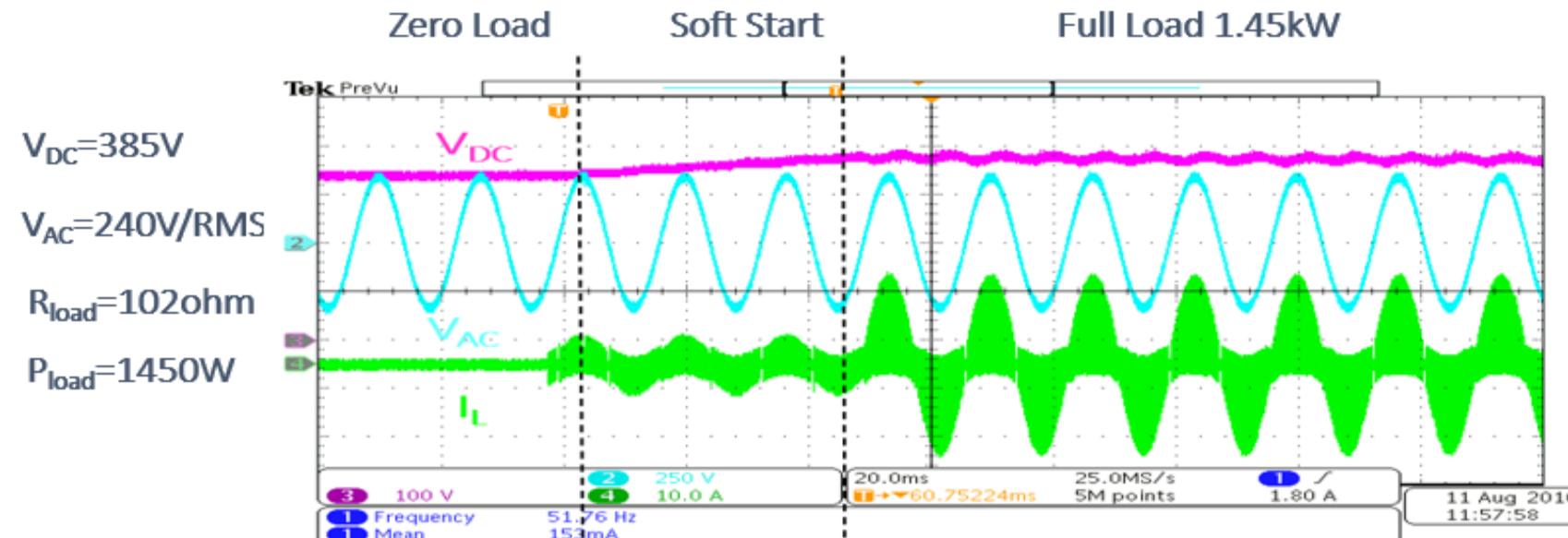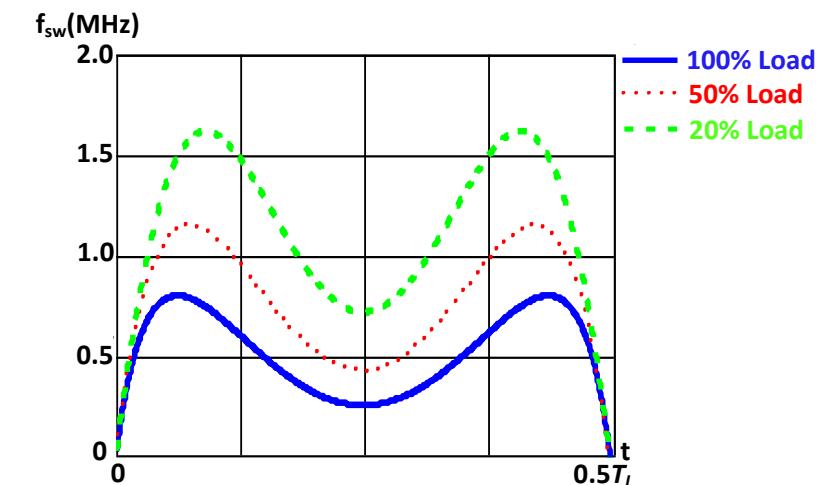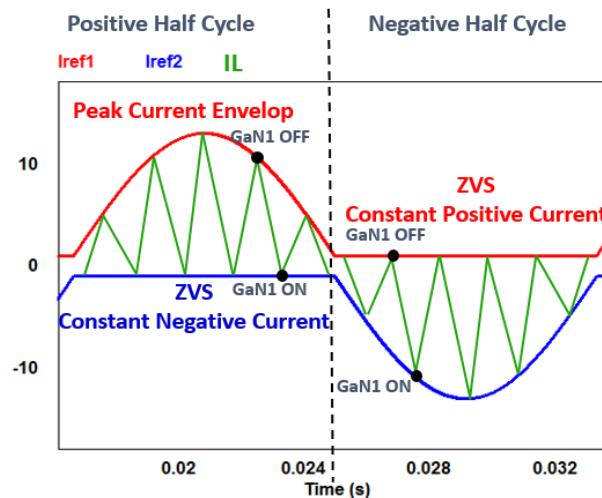
# Quasi-Square Wave PFC Full-range ZVS Operation


- Totem Pole Configuration
  - Current Mode Control
  - Constant ZVS current point
  - Alpha version waveforms


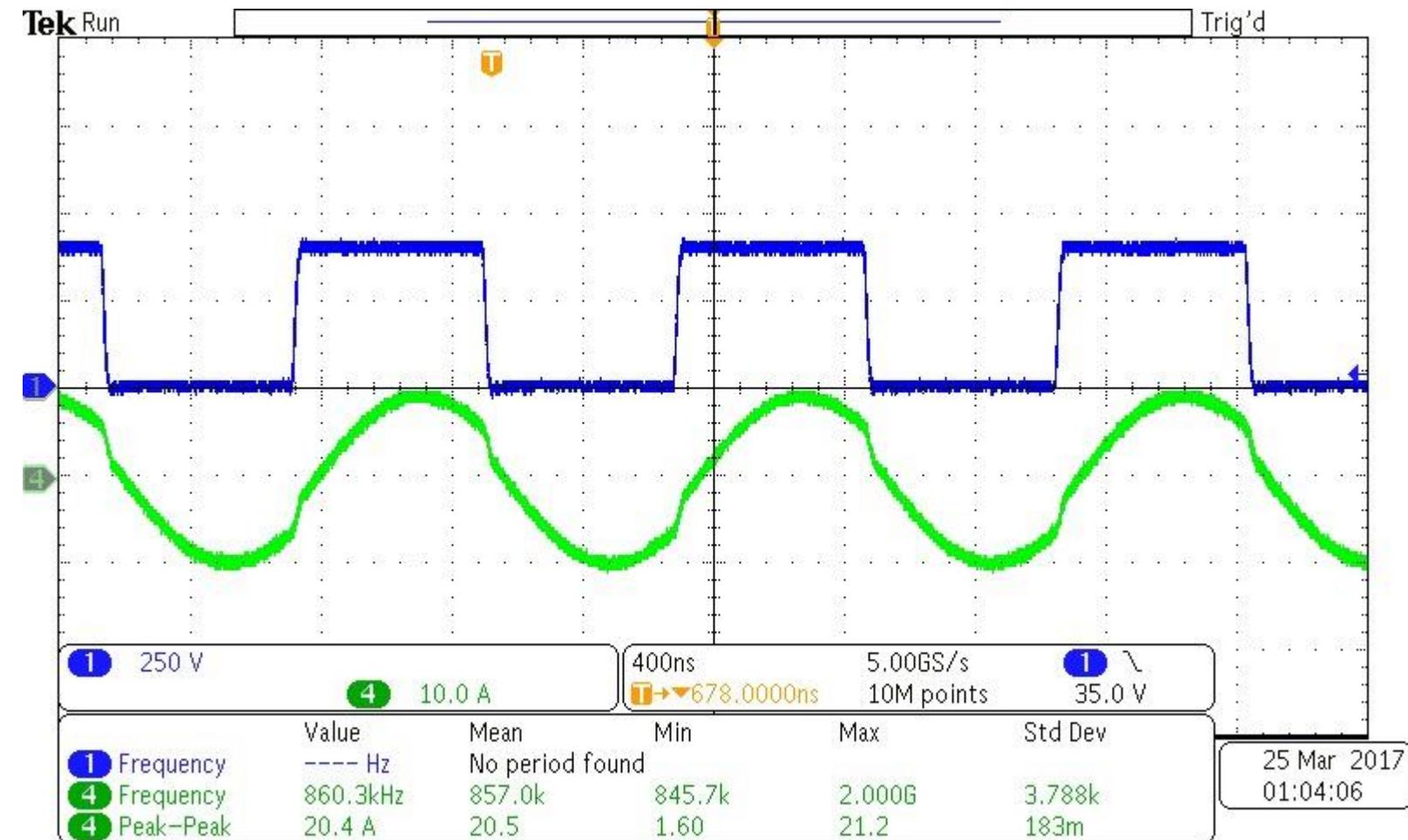
# Preliminary LLC Waveforms at 400V, 2.4kW



# 1 MHz, 3.2 kW – 100% GaN

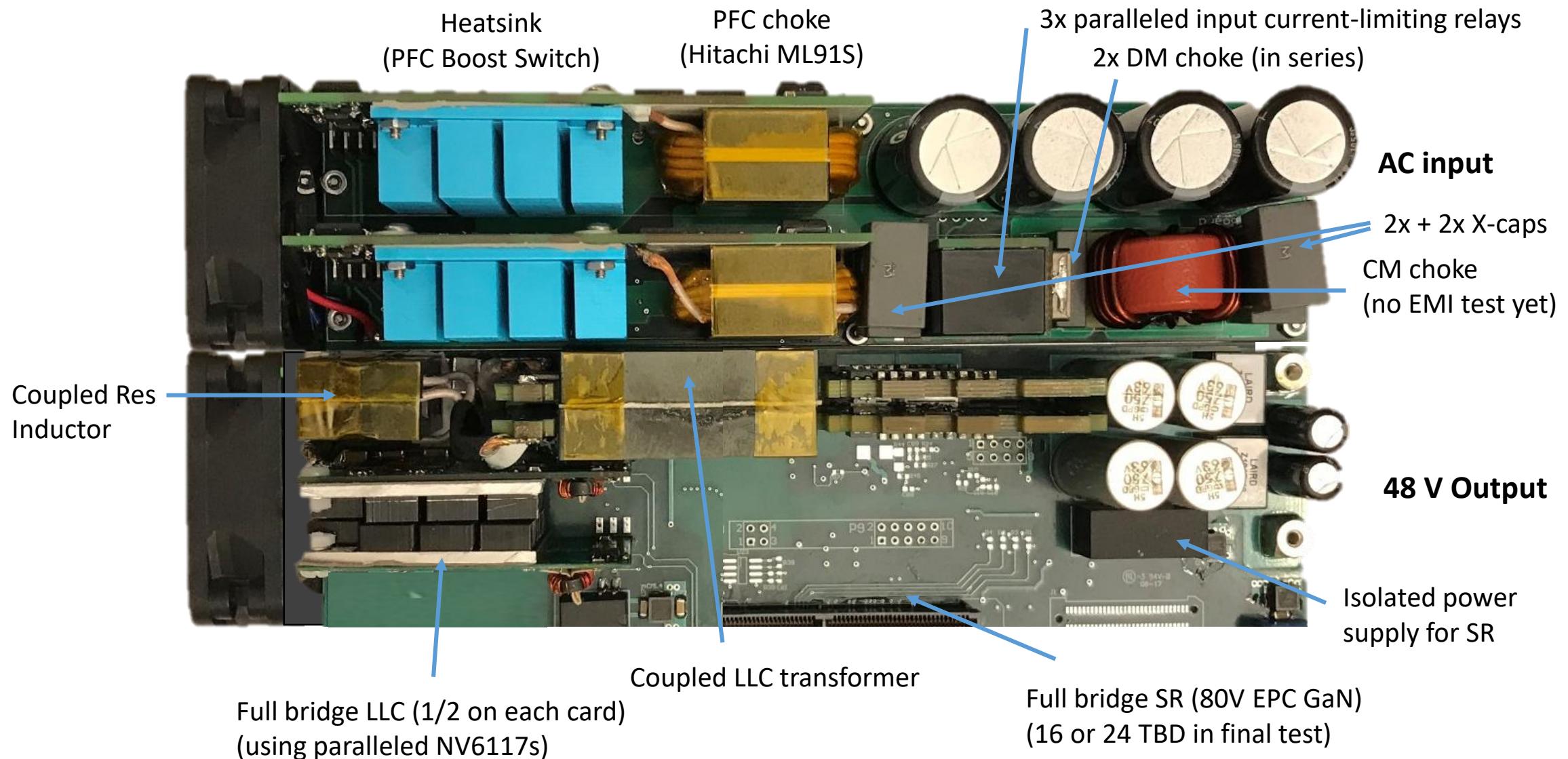

# We Have Arrived!

- GaN Power ICs are now delivering these desired features and more
- System designers are taking a major step forward to deliver more power with less loss in smaller form factors than ever before
- It's time to go "GaN Fast"





# GaN Power ICs at 1 MHz+: Topologies, Technologies and Performance

PSMA Industry Session, Semiconductors

Dan Kinzer, CTO/COO, [dan.kinzer@navitassemi.com](mailto:dan.kinzer@navitassemi.com)

March 2017