



Power Accelerated

GaN Power IC Enable Next Generation Power Adaptor Design

Peter Huang, Director, FAE & Technical Marketing

peter.huang@navitassemi.com


2018前瞻電源設計與功率元件技術論壇 Jan -30th

Navitas Semiconductor Inc.


- World's first & only GaN power IC company
- Founded January 2014
- HQ in El Segundo, CA, USA
- World-class team
- World-class manufacturing partners
- www.navitassemi.com




navitas
noun | en·er·gy

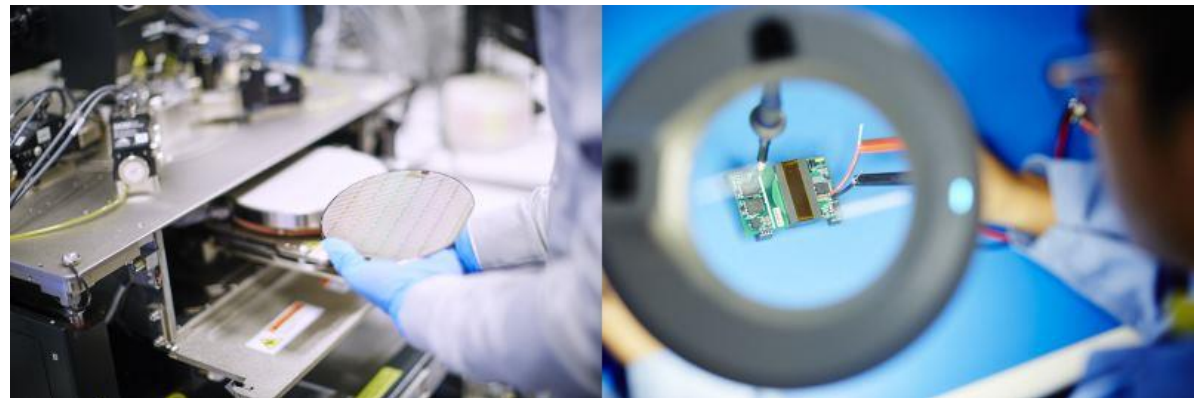

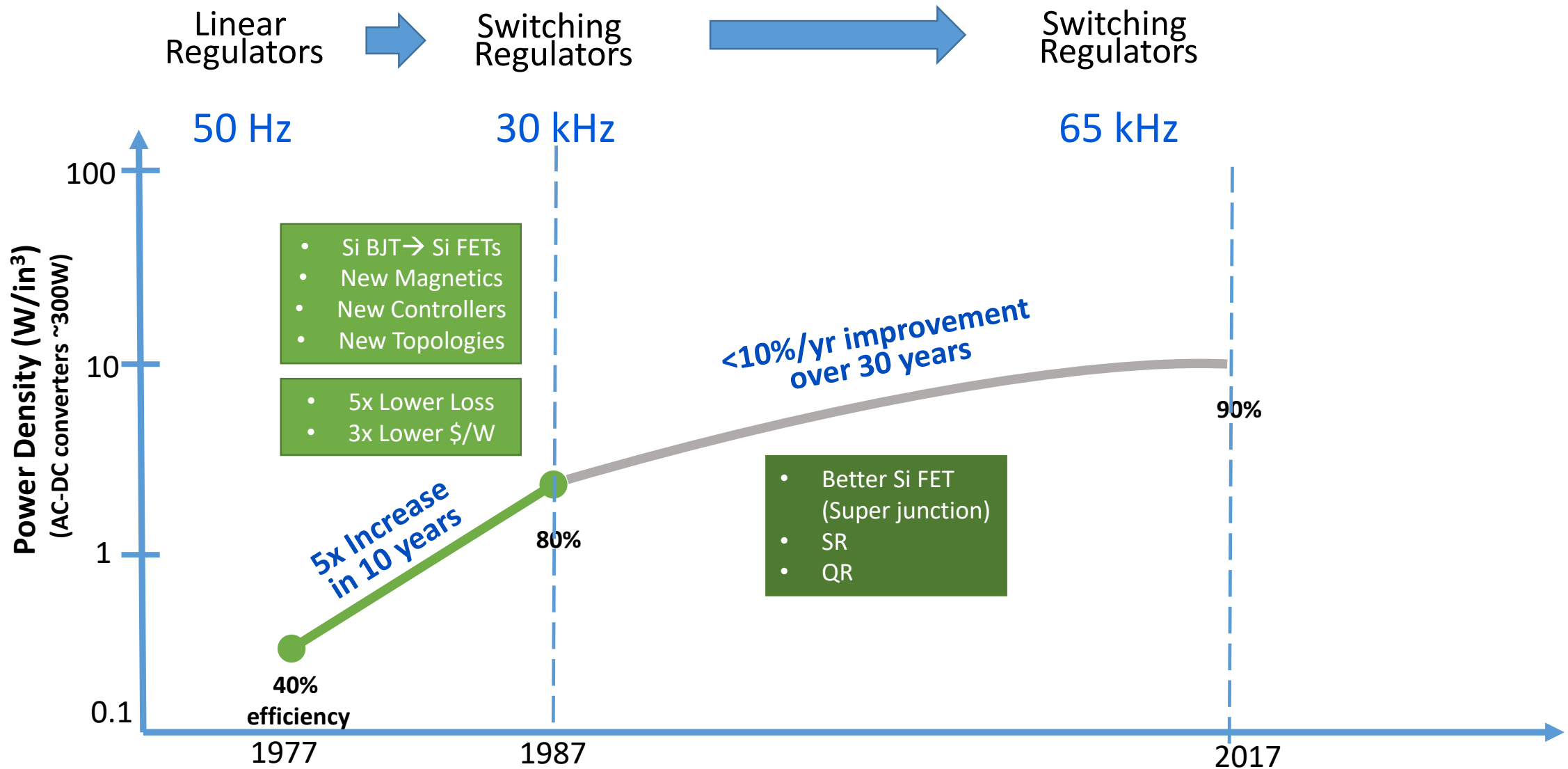The First Revolution in Power Electronics






Today's Power Revolution

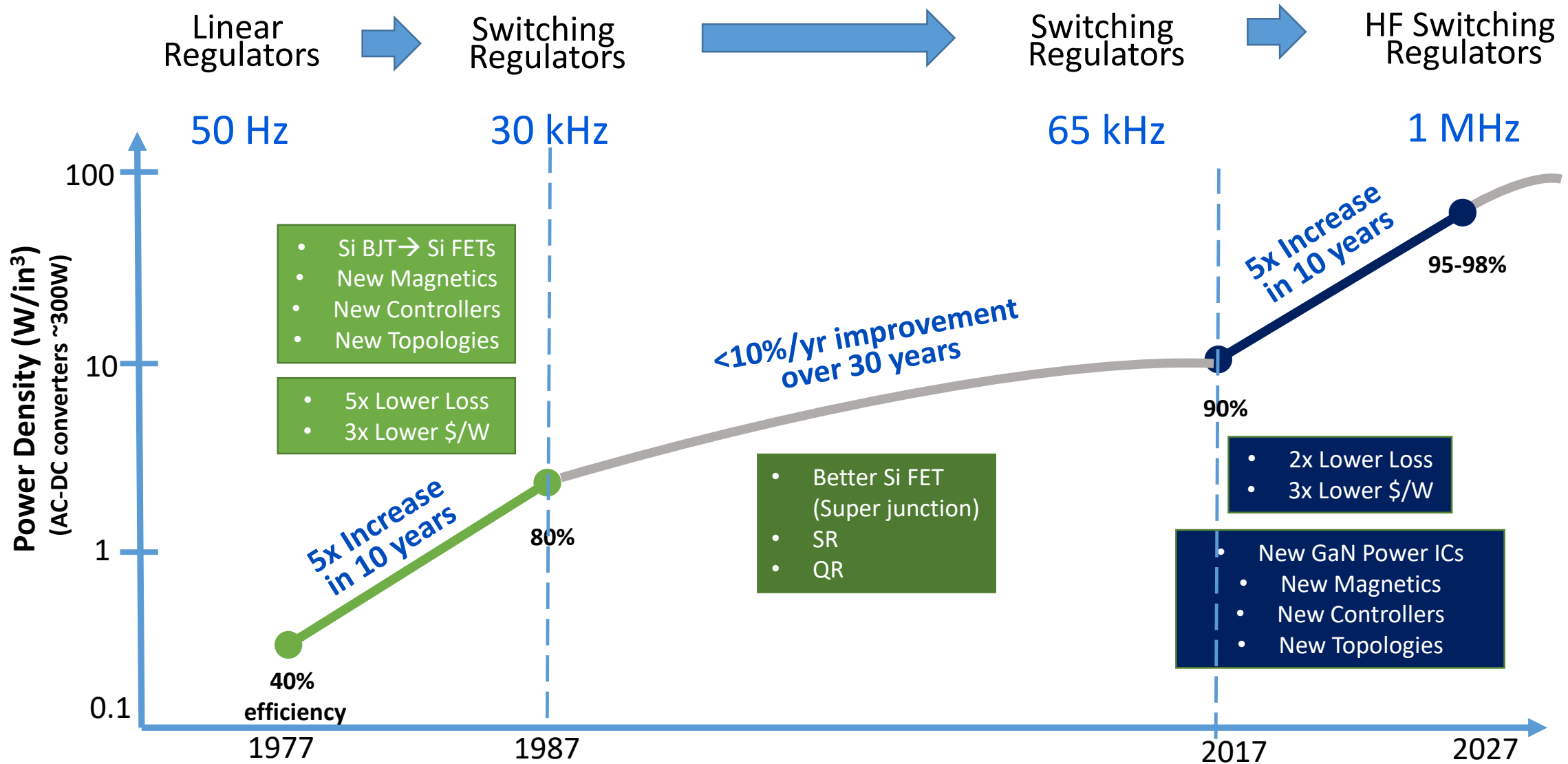


Key Factors for Next Generation Power Adaptor

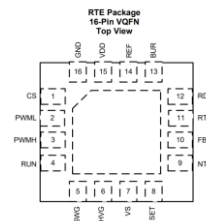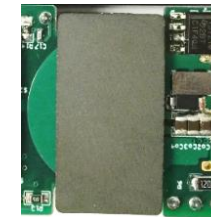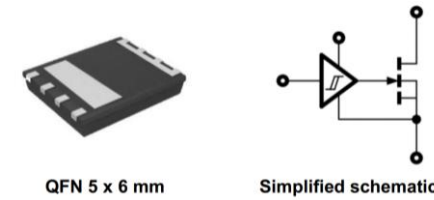- **HF Power Switch**
 - GaN Power IC, GaN FET, SiC FET
- **HF Magnetics**
 - 300kHz~2MHz
- **HF Controllers**
 - ASIC ACF (up to 2MHz)
 - ASIC TP PFC (up to 2MHz)
 - ASIC LLC (up to 2MHz)



HF Magnetics

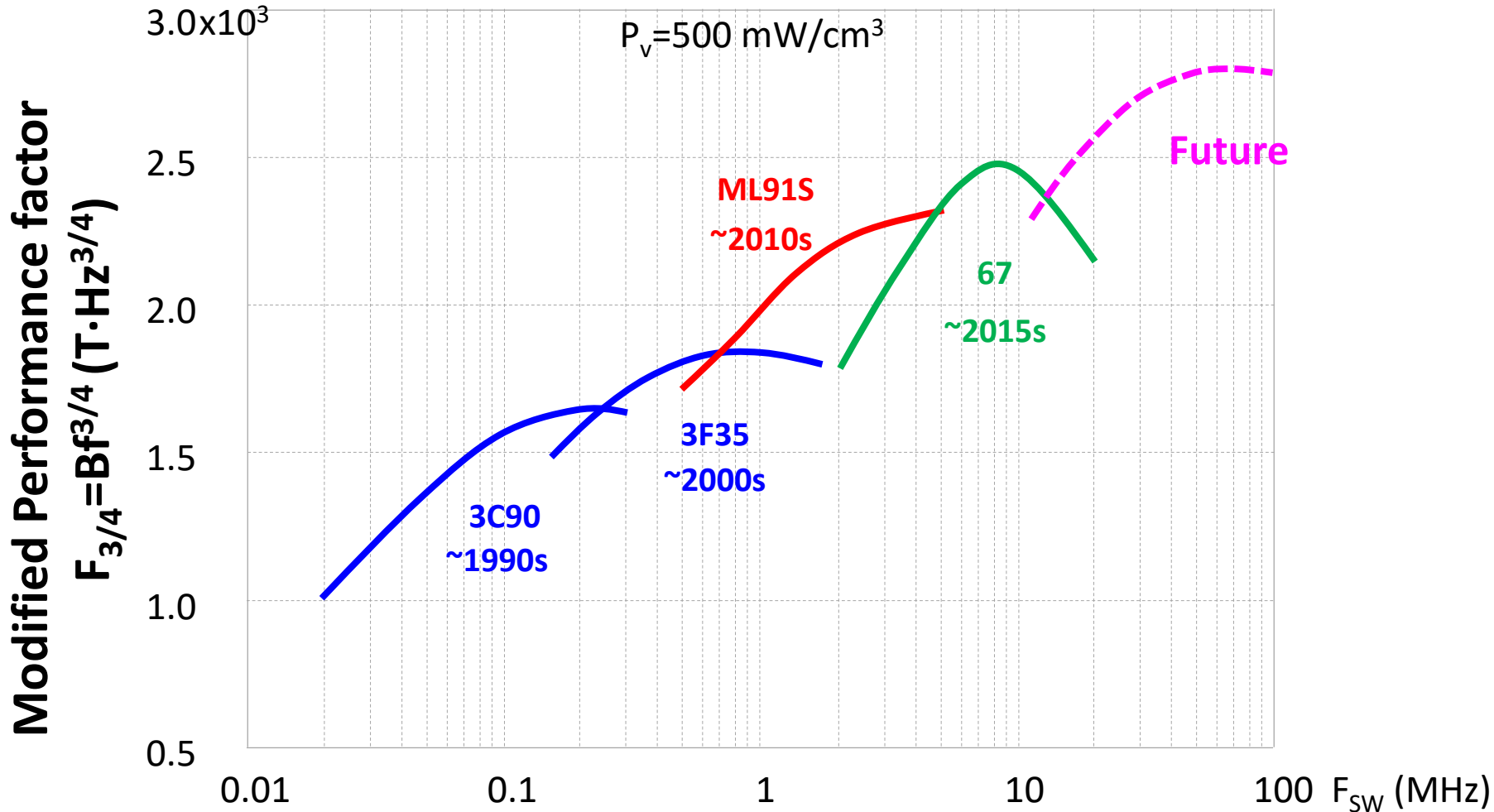


Y. Han, G. Cheung, A. Li, C. R. Sullivan and D. J. Perreault, "Evaluation of Magnetic Materials for Very High Frequency Power Applications," in *IEEE Transactions on Power Electronics*, vol. 27, no. 1, pp. 425-435, Jan. 2012.

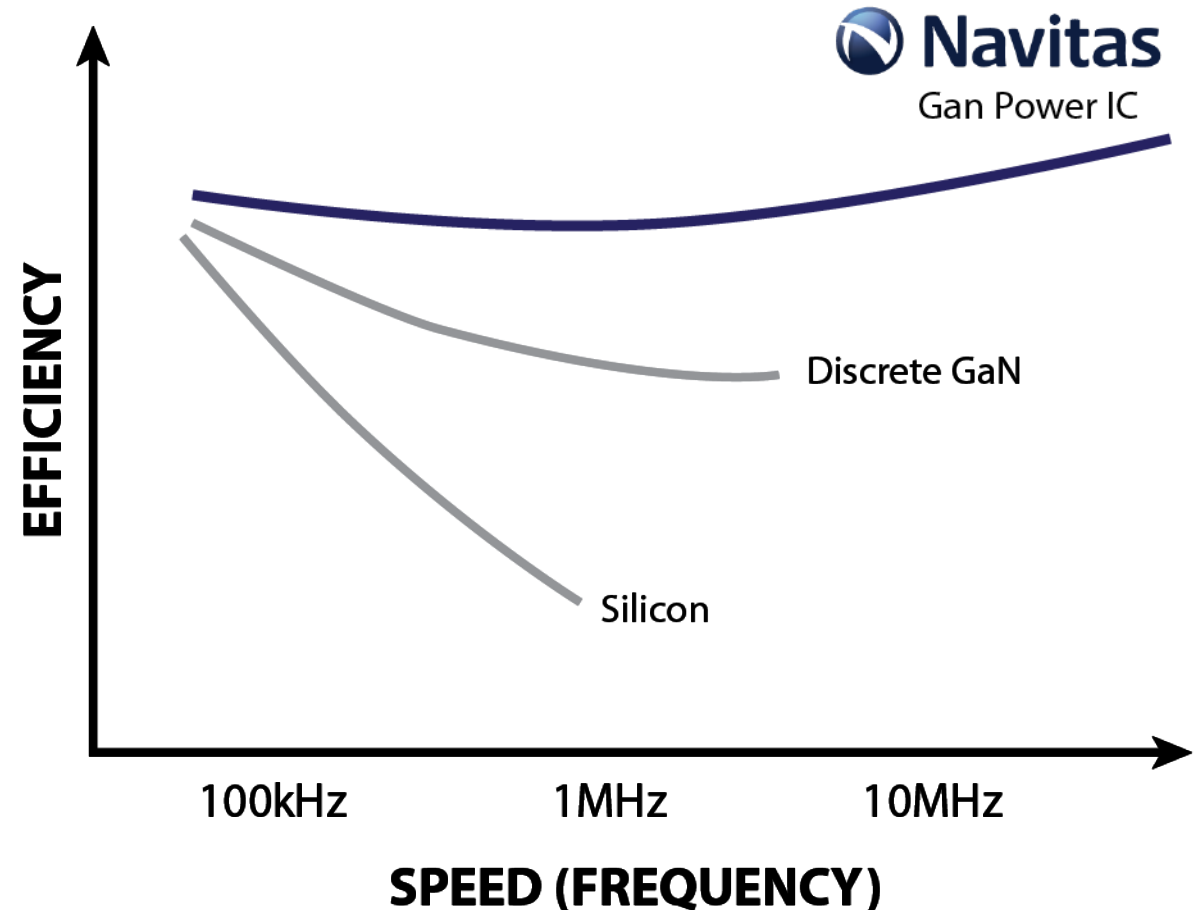A. J. Hanson, J. A. Belk, S. Lim, C. R. Sullivan and D. J. Perreault, "Measurements and Performance Factor Comparisons of Magnetic Materials at High Frequency," in *IEEE Transactions on Power Electronics*, vol. 31, no. 11, pp. 7909-7925, Nov. 2016.

HF Power Switch: Navitas GaN Power IC

- **Speed** enables *small size*, *low-cost* and *faster charging*
- **Efficiency** enables *energy savings*
- With Silicon or Discrete GaN power devices, you can get one **or** the other
- With GaN power ICs, you get **both at the same time**, unequaled **Speed & Efficiency**



Hard-Switch → Soft-Switch with eMode GaN

Primary Switch Power Loss:

$$P_{FET} = P_{COND} * k + P_{DIODE} + P_{T-ON} + P_{T-OFF} + P_{DR} + P_{QRR} + P_{QOSS}$$

Minimized Reduced

开关频率有关损耗

- k-factor >1 due to increased circulating current, duty cycle loss (deadtime)
- P_{T-On} = 0 (soft-switch)
- P_{DR} ↓ 10X (GaN P_{DR} negligible up to 2Mhz)
- P_{QRR} = 0 (NO Reverse recovery)
- P_{DIODE} ↓ 2X (reverse conduction loss reduced due to short deadtime)
- P_{Qoss} ↓ 10X (GaN Coss charging/discharging loss negligible up to 2Mhz)
- P_{T-OFF} = Reduced (limited by I-V crossover loss due to drive loop impedance)

eMode GaN 消除的损耗

Hard-Switch → Soft-Switch with Navitas GaN Power IC

Primary Switch Power Loss:

$$P_{FET} = P_{COND} \overset{\text{Minimized}}{* k} + \overset{\text{Reduced}}{P_{DIODE}} + \cancel{P_{T-ON}} + \cancel{P_{T-OFF}} + \cancel{P_{DR}} + \cancel{P_{QRR}} + \cancel{P_{QOSS}}$$

- k-factor >1 due to increased circulating current, duty cycle loss (deadtime)
- P_{T-ON} = 0 (soft-switch)
- P_{DR} ↓ 10X (GaN P_{DR} negligible up to 2Mhz)
- P_{QRR} = 0 (NO Reverse recovery)
- P_{DIODE} ↓ 2X (reverse conduction loss reduced due to short deadtime)
- P_{QOSS} ↓ 10X (GaN C_{oss} charging/discharging loss negligible up to 2Mhz)
- P_{T-OFF} = 0 (Due to driver Integration, No gate loop impedance)


Ideal Switching = No Switching Loss @ High F_{sw}

Navitas GaN ICs provide Ideal Switching

How?

HF Power Switch: World's First AllGaN™ Power ICs


Fastest, Most Efficient
GaN Power FETs

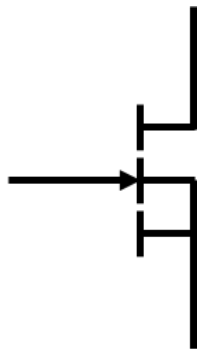

>20x faster than silicon
>5x faster than cascoded GaN
Proprietary design



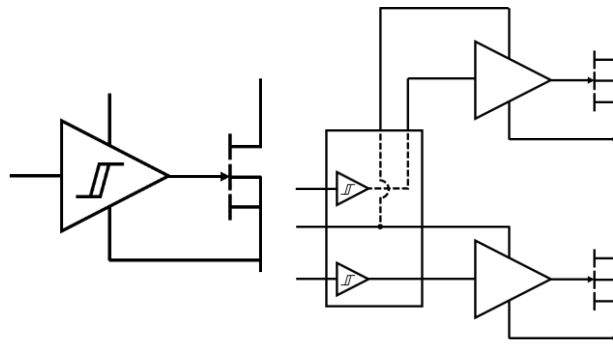
iDrive First & Fastest
Integrated GaN Gate Drivers



>3x faster than any other gate driver
Proprietary design
30+ patents granted/applied



World's First
AllGaN™ Power IC



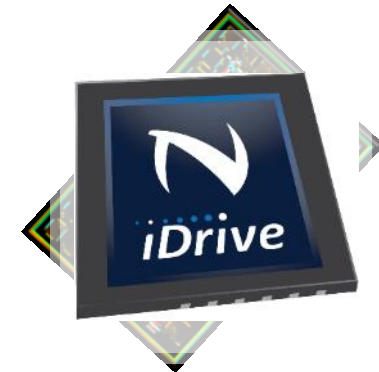


Up to 40MHz switching, 5x higher density & 20% lower system cost



AllGaN™: Monolithic GaN Power IC

- Monolithic integration at 650 V
 - GaN FET (range 110-560 mΩ)
 - GaN Driver (iDrive™)
 - GaN Logic
- “Digital In, Power Out”

NV6115 PFC Boost 应用线路

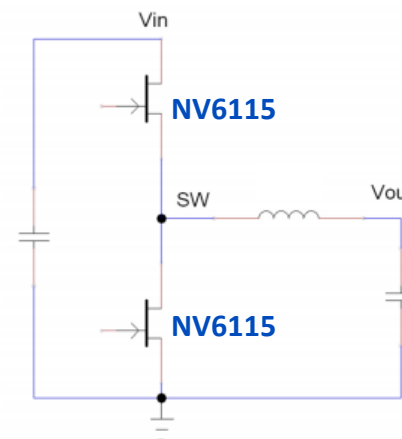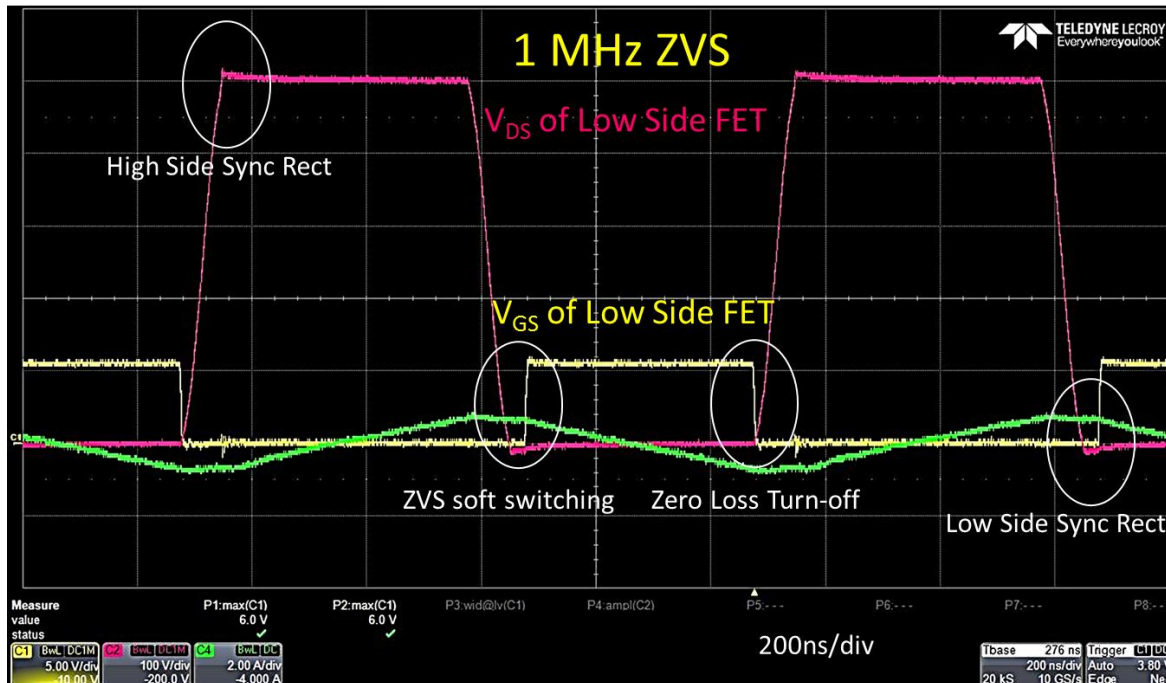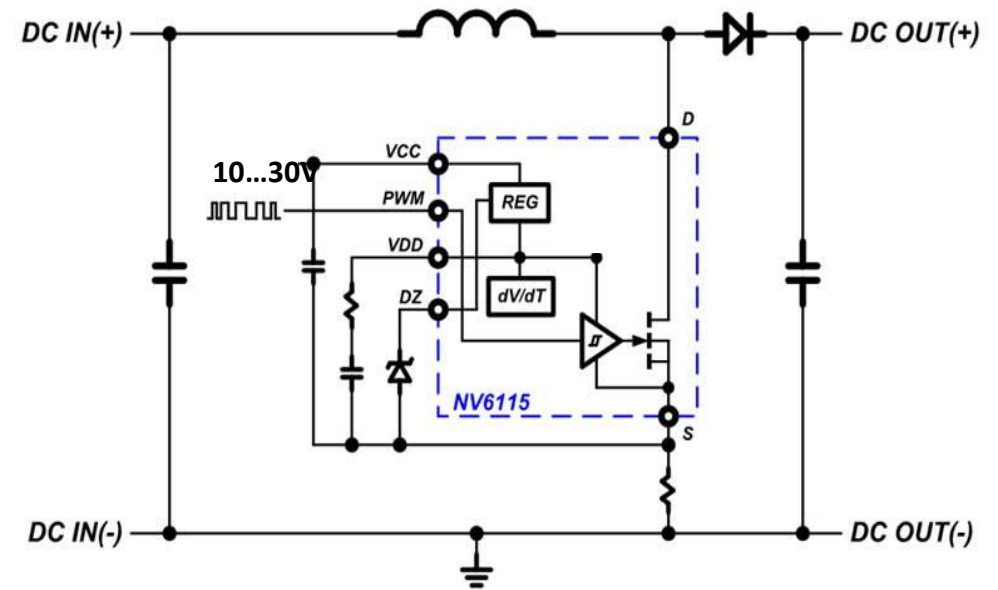

Integrated Drive → Simple & Robust

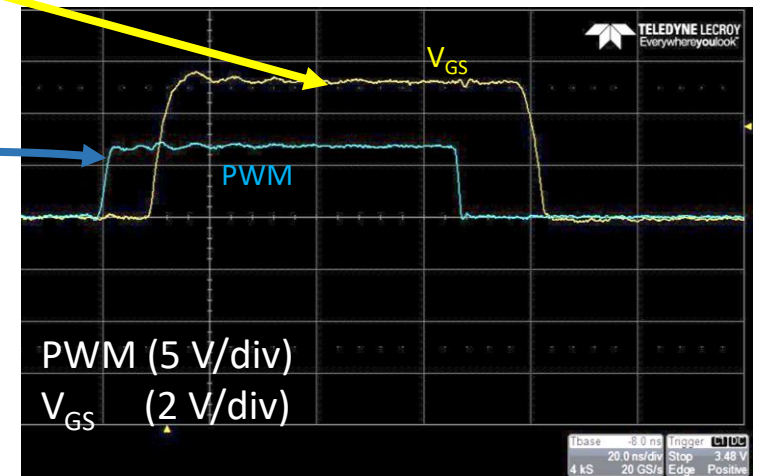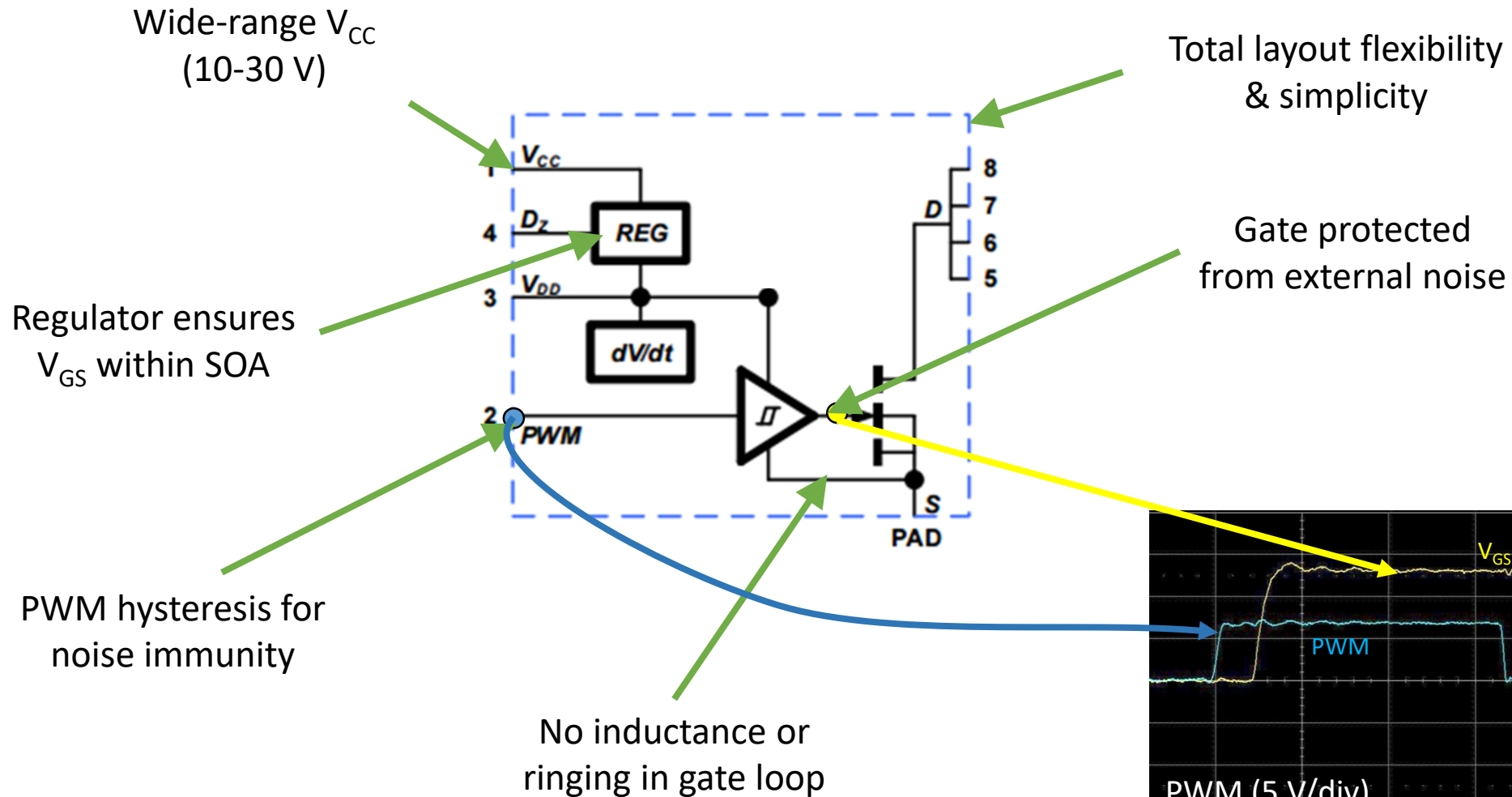


Clean, Controlled FET Gate

- **Discrete driver**


- Gate loop inductance creates overshoot (even with good layout)
- Reliability concern

- **iDrive™ GaN Power IC**

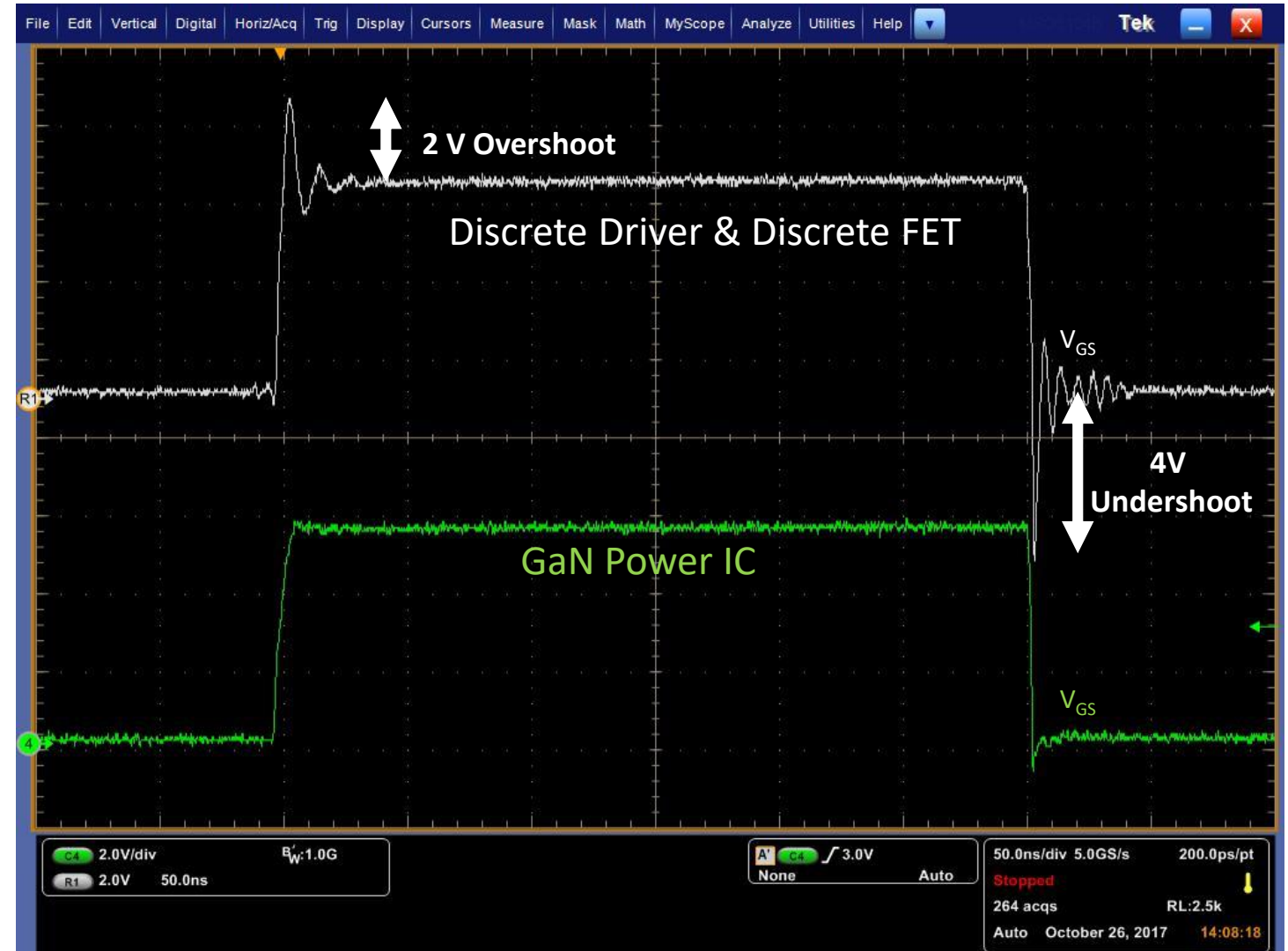
- No gate loop parasitic
- Clean and fast gate signal



Fast & Clean Hard Switching

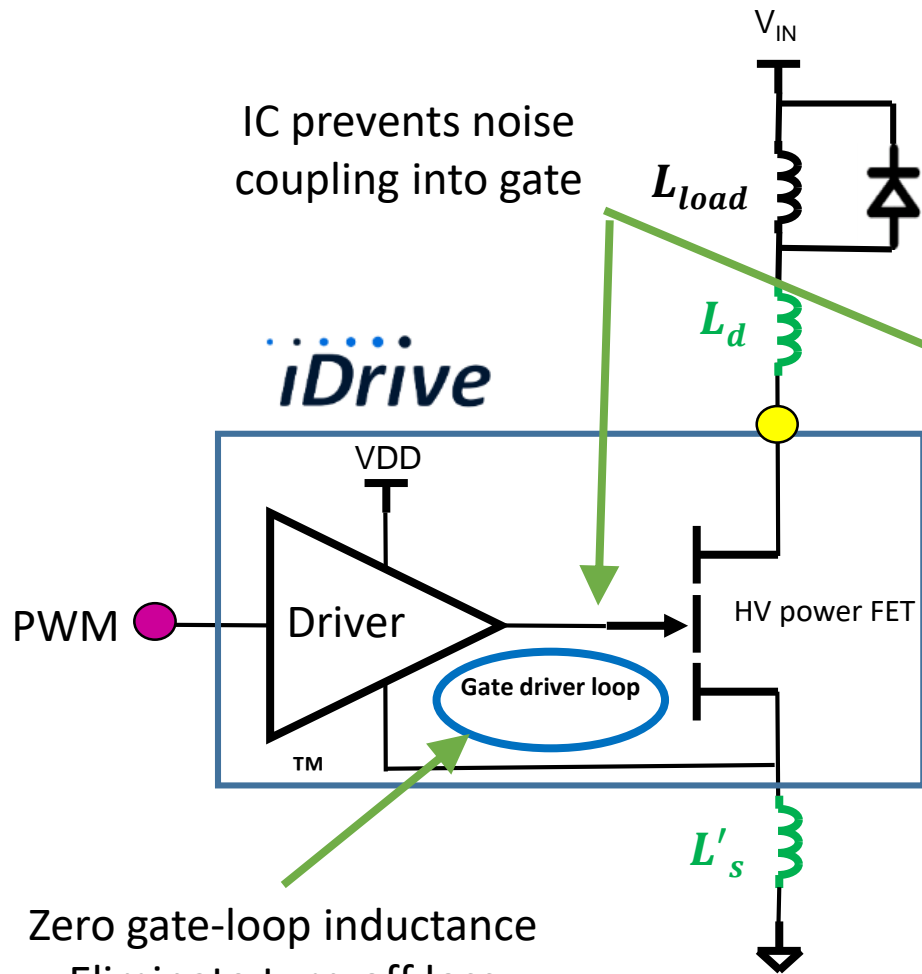

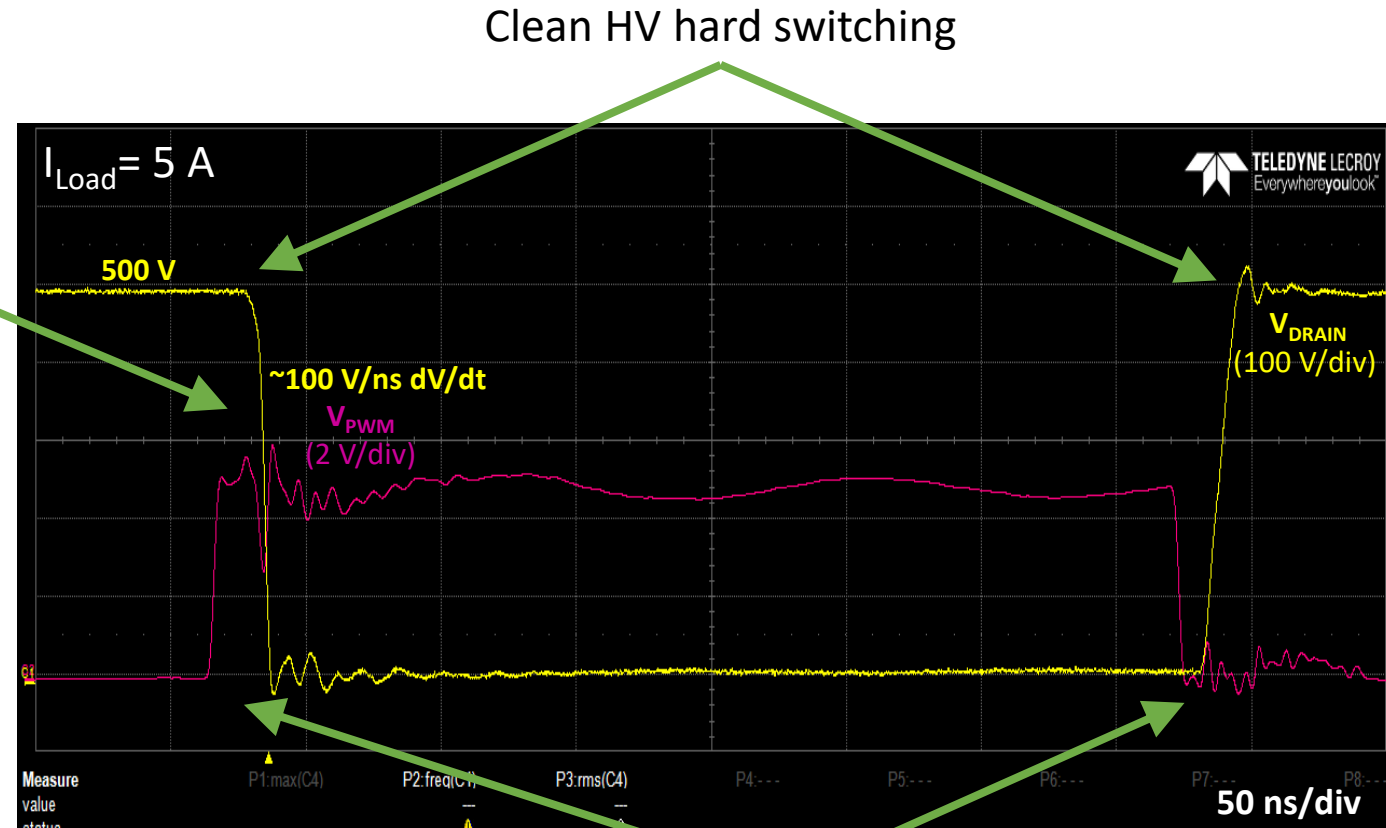
Zero gate-loop inductance
Eliminate turn-off loss



Prop delay 10-20 ns

Speed & Integration → Eliminate Turn-off Losses

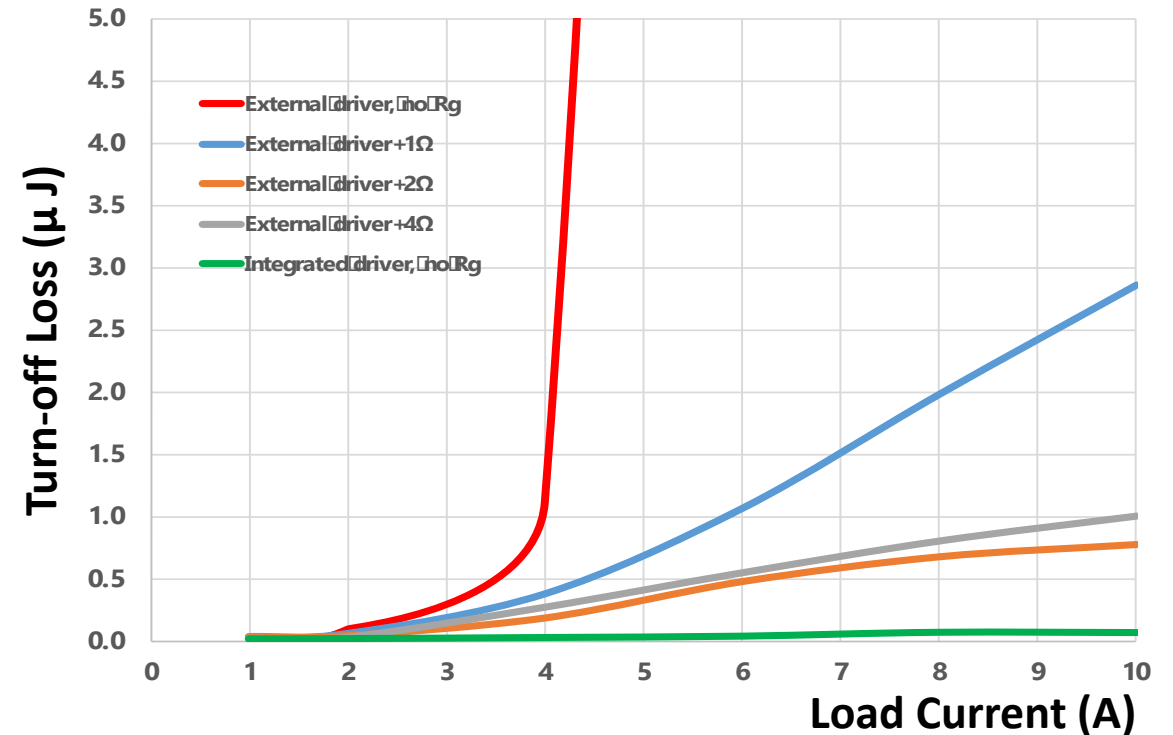
- **External drivers**
 - Just 1-2 nH of gate loop inductance can cause unintended turn-on
 - Gate resistors reduce spikes but create additional losses
- **Integrated GaN drivers (iDrive™)**
 - Eliminate the problem
 - Negligible turn-off losses
 - Removes unintended dV/dt turn-on



Discrete FET and drive, no R_G = out of control



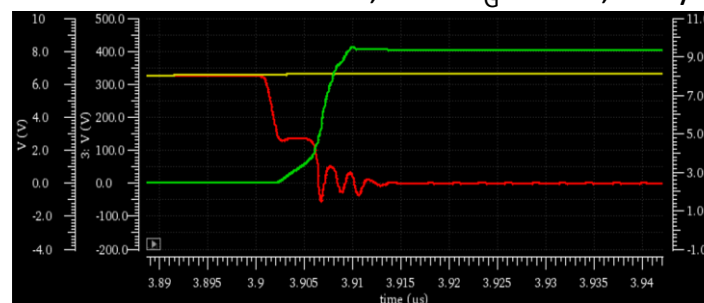Discrete FET and drive, with R_G = slow, lossy



Integrated FET and drive, no R_G = fast, efficient



Hard-Switch → Soft-Switch with Navitas GaN Power IC

Primary Switch Power Loss:





$$P_{FET} = P_{COND} \overset{\text{Minimized}}{*k} + \overset{\text{Reduced}}{P_{DIODE}} + \cancel{P_{T-ON}} + \cancel{P_{T-OFF}} + \cancel{P_{DR}} + \cancel{P_{QRR}} + \cancel{P_{QOSS}}$$

- k-factor >1 due to increased circulating current, duty cycle loss (deadtime)
- P_{T-ON} = 0 (soft-switch)
- P_{DR} ↓ 10X (GaN P_{DR} negligible up to 2Mhz)
- P_{QRR} = 0 (NO Reverse recovery)
- P_{DIODE} ↓ 2X (reverse conduction loss reduced due to short deadtime)
- P_{QOSS} ↓ 10X (GaN C_{oss} charging/discharging loss negligible up to 2Mhz)
- P_{T-OFF} = 0 (Due to driver Integration, No gate loop impedance)


High Power Density = More Integration

AllGaN™ Half-Bridge GaN Power IC

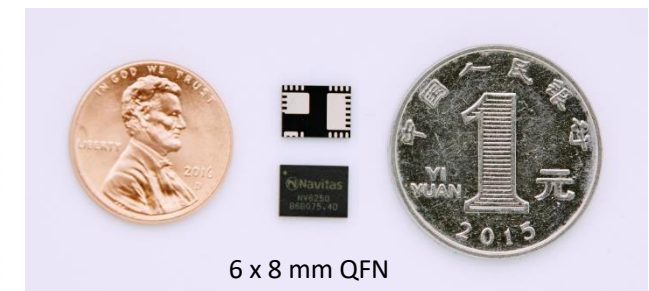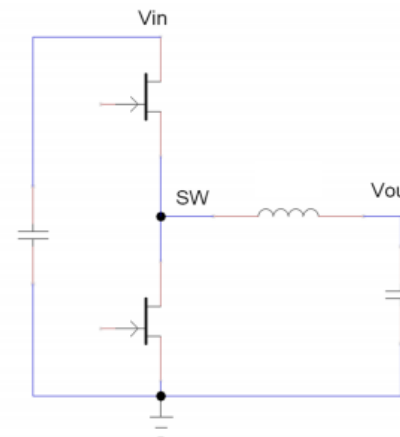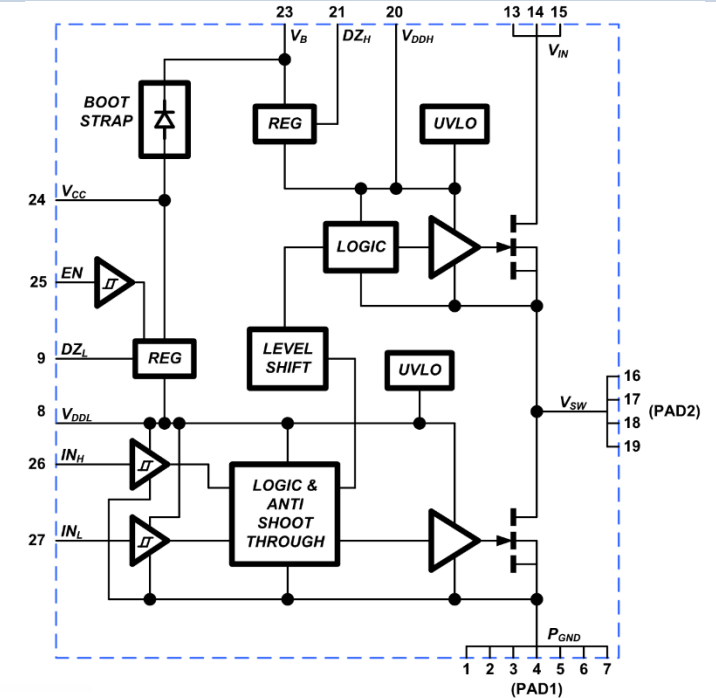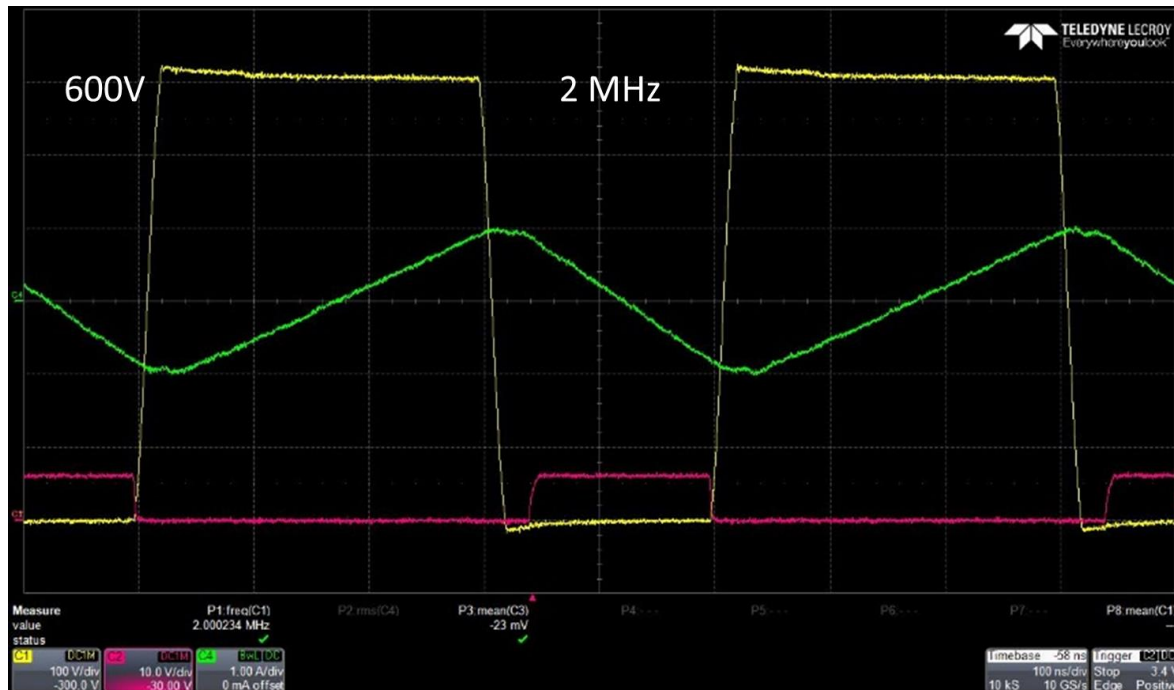- Monolithic integration at 650V
 - 2x GaN FETs (110-560 mΩ)
 - 2x GaN drivers (iDrive™)
 - GaN Logic (level-shift, bootstrap, UVLO, shoot-through, ESD)
- “Digital In, Power Out”



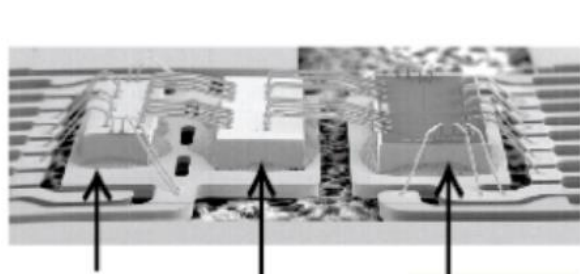GaN Level-Shift: Low Loss, High-Frequency




I/F
Chip
Si CMOS

On-chip
Transformer
SiO₂ / Polyimide



Gate Driver
Chip
Si CMOS



Bootstrap
Diode
Si / SiC

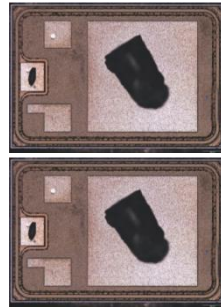

Half-Bridge
FETs
Si

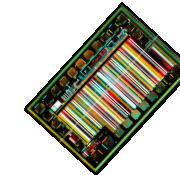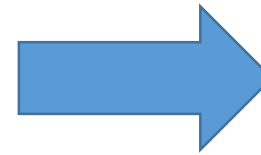

AllGaN™ Technology
Lateral 650V GaN-on-Si



Disparate Technologies

Hybrid isolator, discrete driver, discrete power, bootstrap diode

High Power Loss

- Driver loss, R_G loss
- Bootstrap diode Q_{RR} , V_F
- Pulsed high current level shifter power (?)



Monolithic Platform



Lateral GaN-on-Si, Half-Bridge GaN Power IC

Low Power Loss


- No gate driver loop parasitics, matched driver-FET capability, negligible loss vs. frequency
- Zero Q_{RR} , low V_{DS} in synchronous charging
- Very fast, low-power loss, MHz+

Complex Design → Easy-to-Use

Half-Bridge Discrete GaN

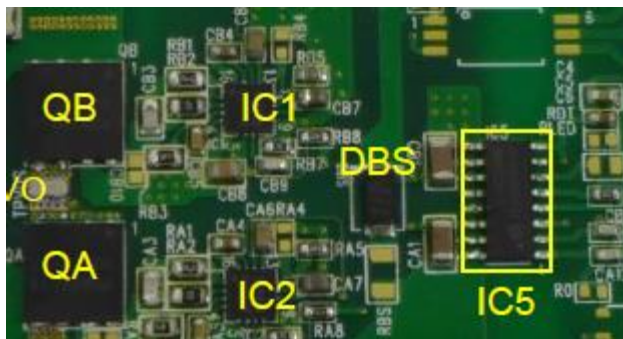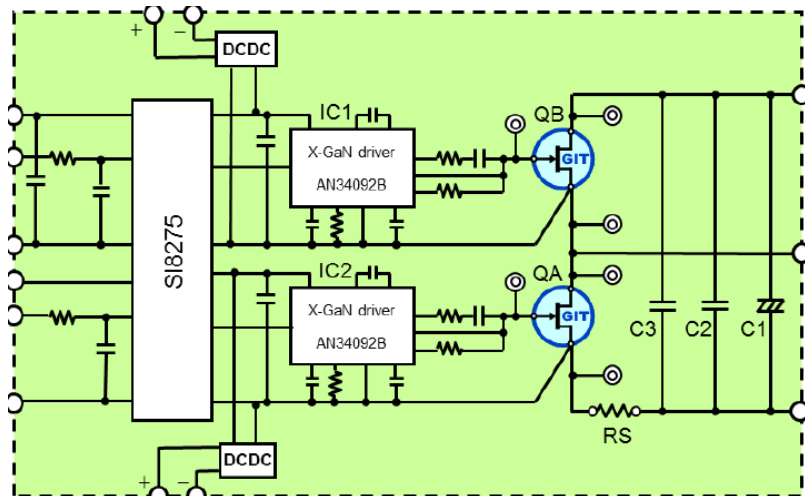


PCB Area: 24 x 42 ~ 1,000 mm²

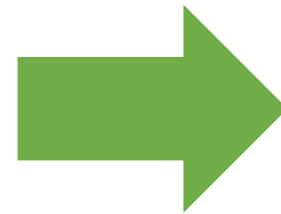

- ✓ 20x smaller PCB area
- ✓ Lower cost
- ✓ Robust & protected
- ✓ Simple
- ✓ Easy layout

Half-Bridge GaN Power IC


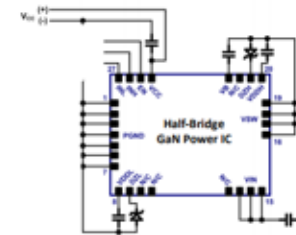


PCB Area: 6 x 8 = 48 mm²



HF Topology for Low Power Adaptor(<75W)

Active Clamp Flyback

QR vs ACF

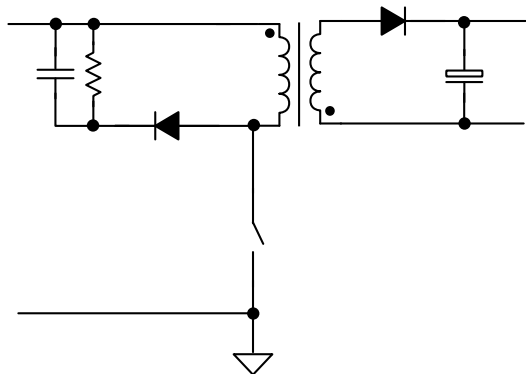
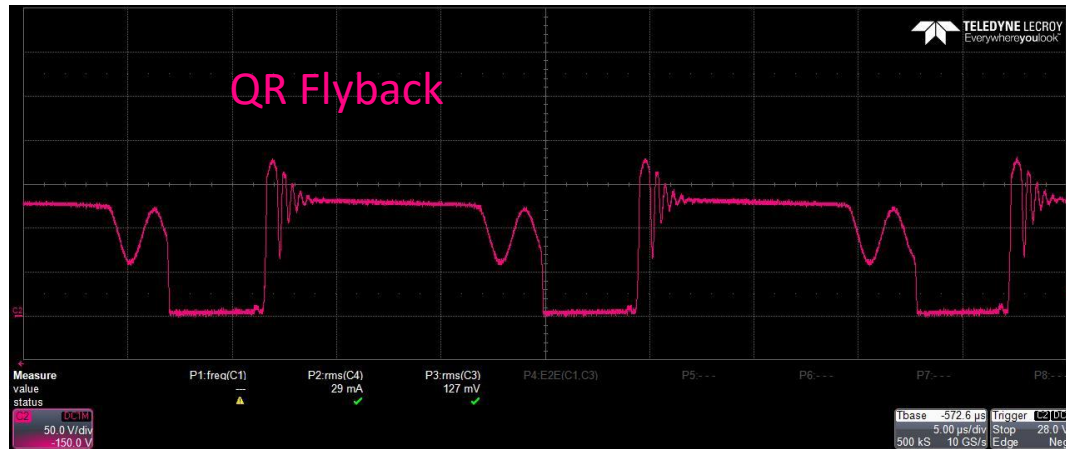


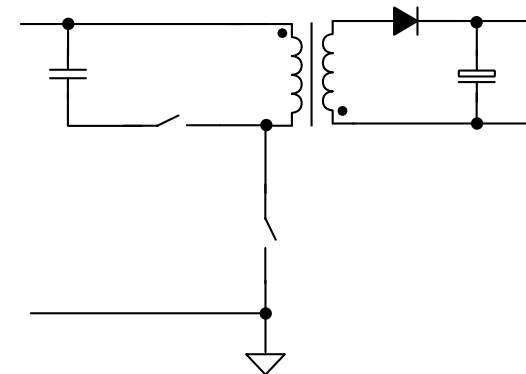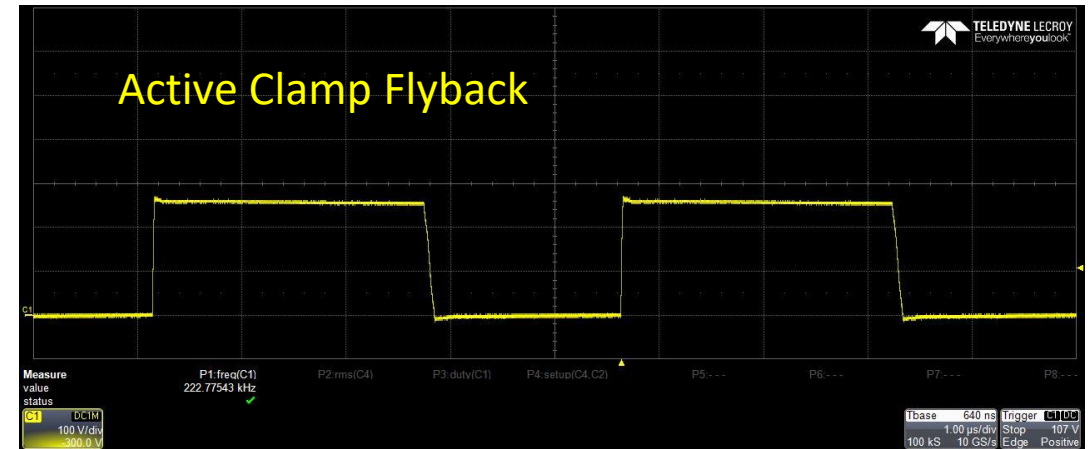- RCD loss(leakage loss)
- Hard switching loss(high Line)
- Switching loss increases with high fsw





- No RCD loss(leakage loss)
- ZVS over all AC line, all load conditions
- ZCS achieved
- ACF operates at > 1MHz

ACF Operation (S1 ON)

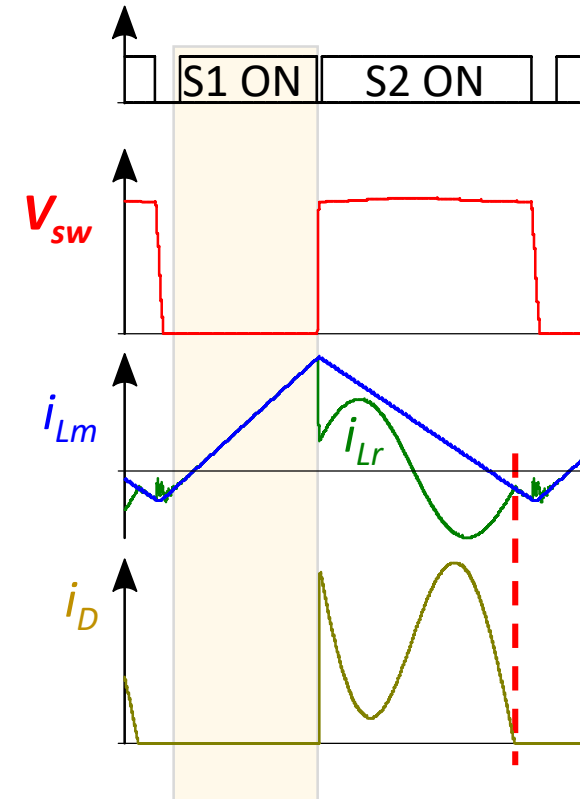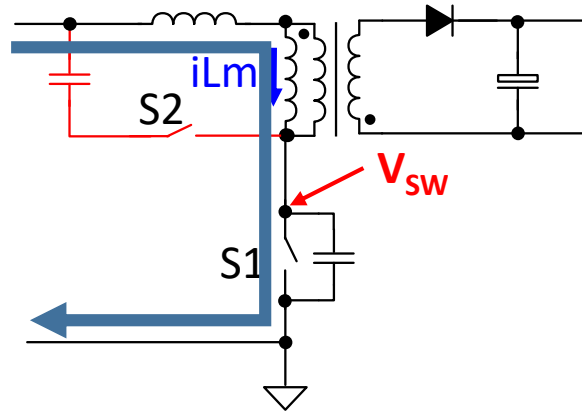


- S1 ON, linearly charging L_m , like a QR flyback

ACF Operation (S2 ON, S1 OFF)

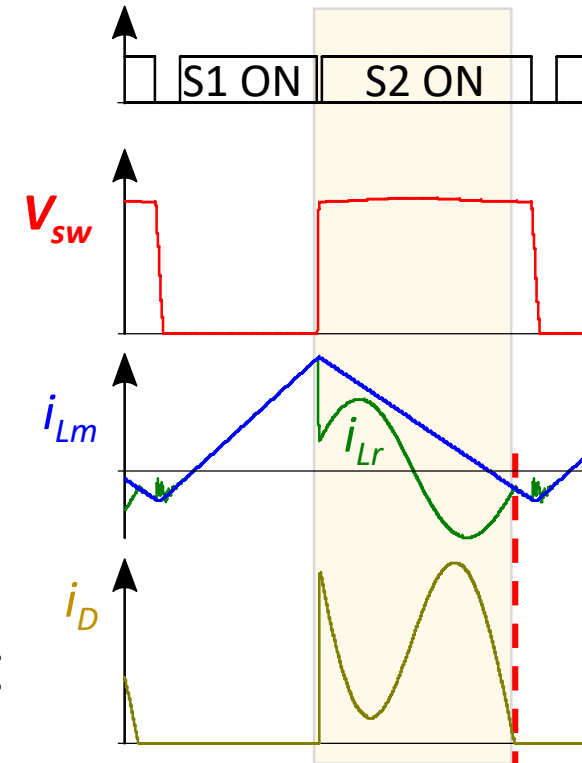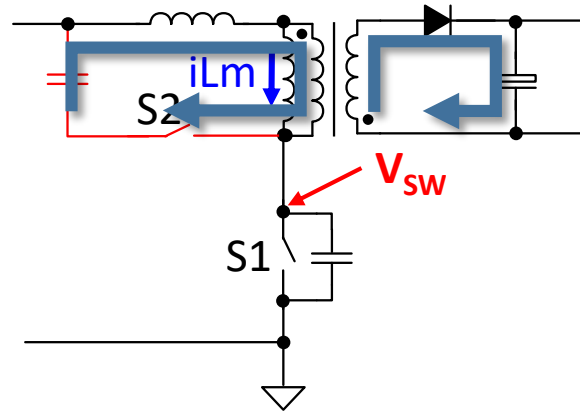


- S2 ON with ZVS, effective clamping since current can go both direction, no overshoot
- Leakage resonates with clamping capacitor
- Rectifier diode conducts and delivers power
- Interval ends when rectifier current drops to zero



ACF Operation (Building Negative L_m)

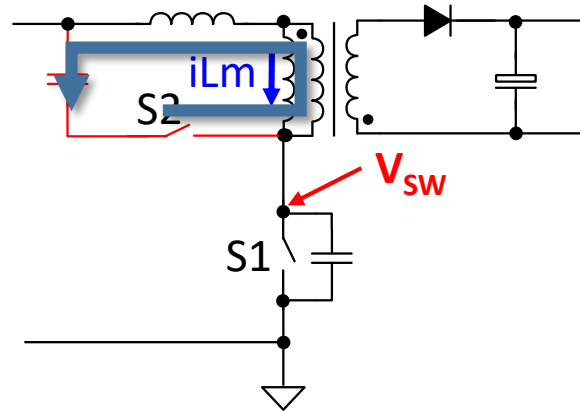

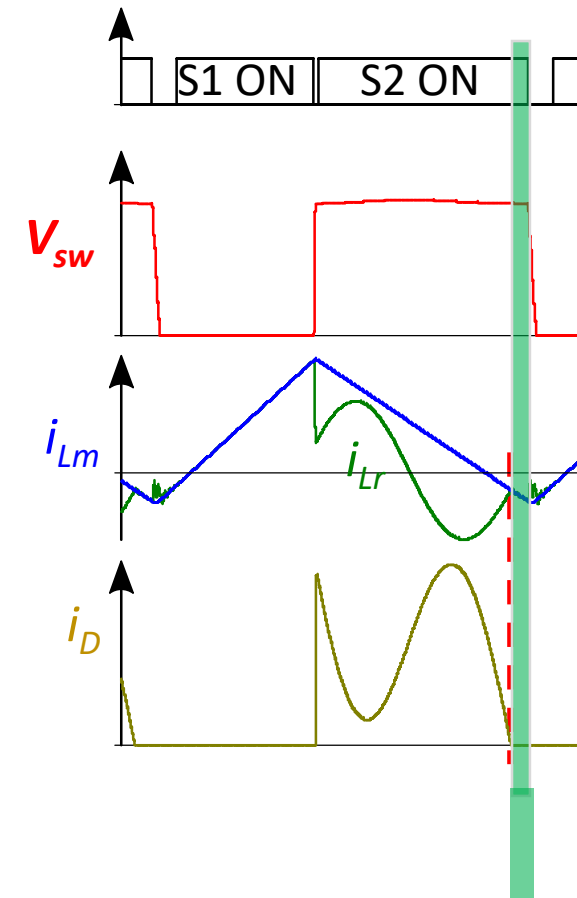- S2 current equals to magnetizing current
- Magnetizing current becomes negative





ACF Operation (S1 ZVS Transition)

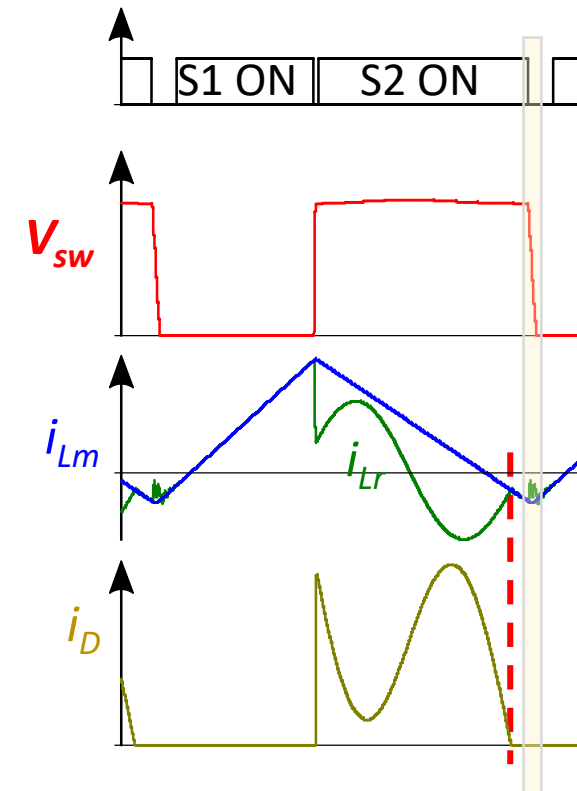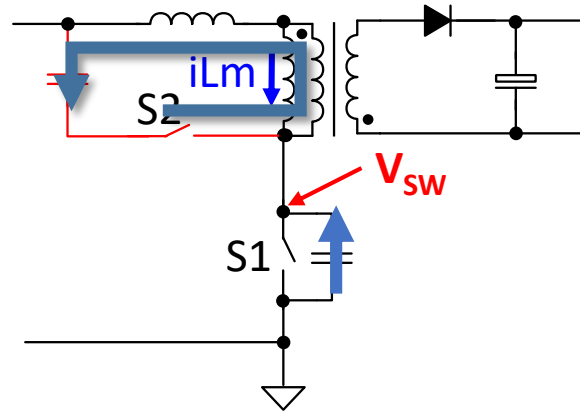

- Negative i_{L_m} discharge S1 C_{oss}
- S1 can be turned on later in ZVS


ACF Enables ZVS and High Frequency Switching

Lossless snubber

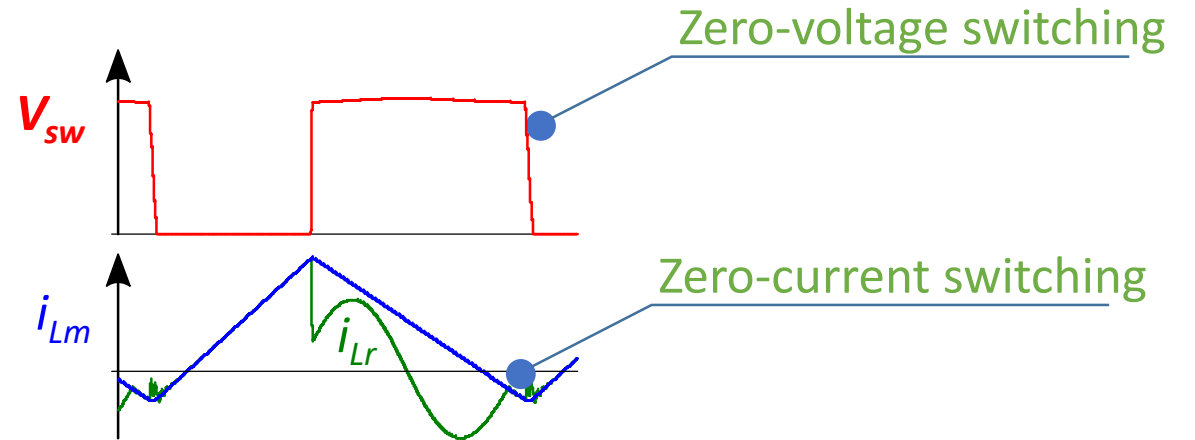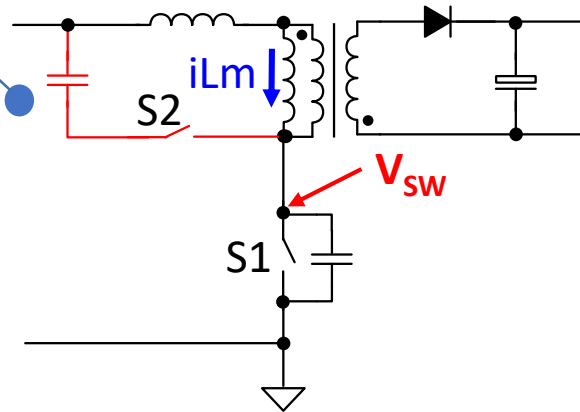


- No snubber losses, all leakage energy is recovered
- **ZVS turn-on over entire operation range**
- **ZCS turn-off for output rectifier**
- Clean waveforms reduce EMI
- Enable small adapter design with high frequency switching

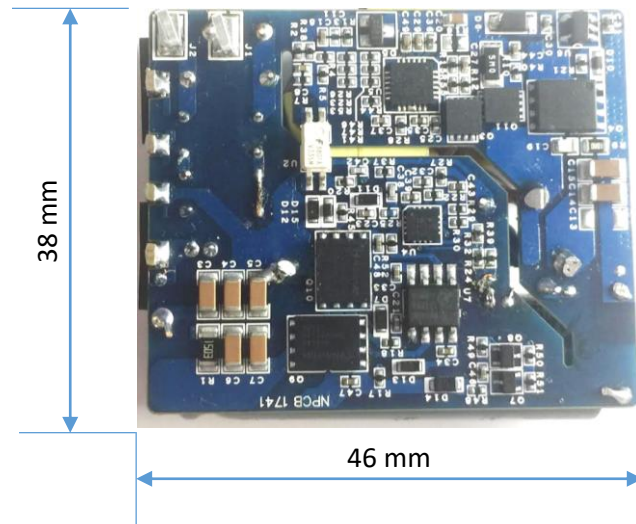65W USB-PD ACF: *World's Smallest Adapter*




- Input : Universal AC (85-265V_{AC}, 47-63Hz)
- Output : USB-PD (5-20V) (65W)
- Frequency : 300~400kHz(Full Load)
- **Primary FET : NV6115 (160 mΩ) + NV6117 (110 mΩ) GaN Power ICs**
- **Controller(ACF) : UCC28780**
- **Magnetic Core : N49**
- Size : 38 x 46 x 15.5 mm = 27 cc uncased
43 x 51 x 20.5 mm = 45 cc with 2.5 mm case
- **Efficiency : 93.4% at 90 V_{AC}, Full Load**
- **Power Density : 2.4 W/cc (39 W/in³) uncased
1.5 W/cc (24 W/in³) cased**
- Construction : 4-layer, 2-oz Cu PCB, SMT powertrain
"No heatsink" design

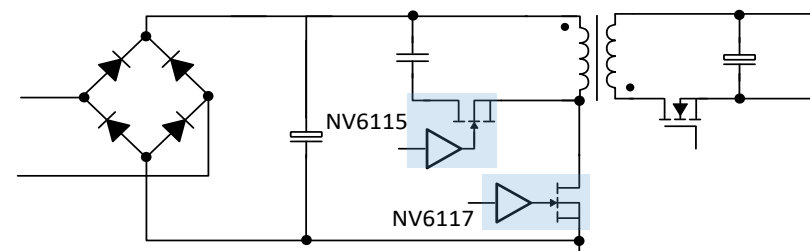

65W USB-PD ACF

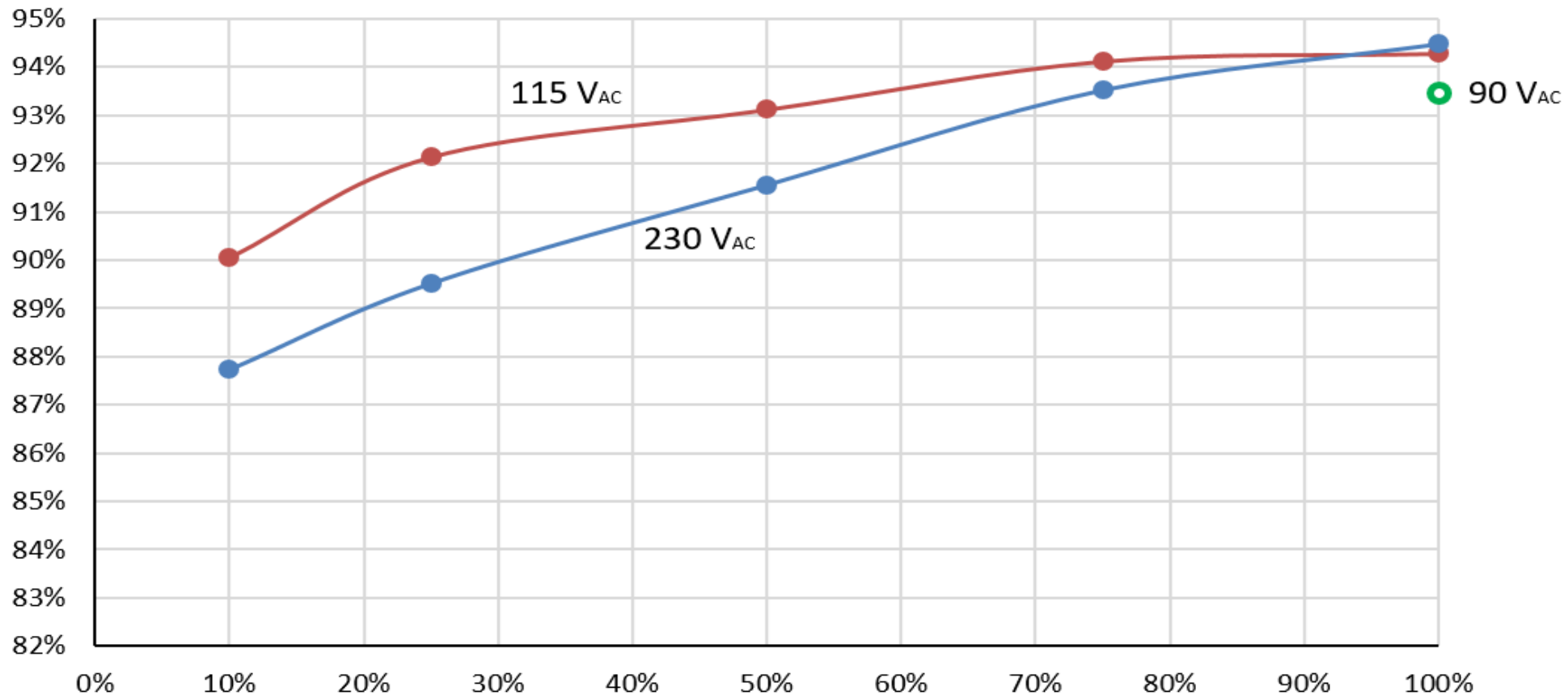
Efficiency at 20 V_{OUT} (25°C, no airflow)




Efficiency (25°C, no airflow)

Controller(ACF) : UCC28780

4-point Average Efficiency

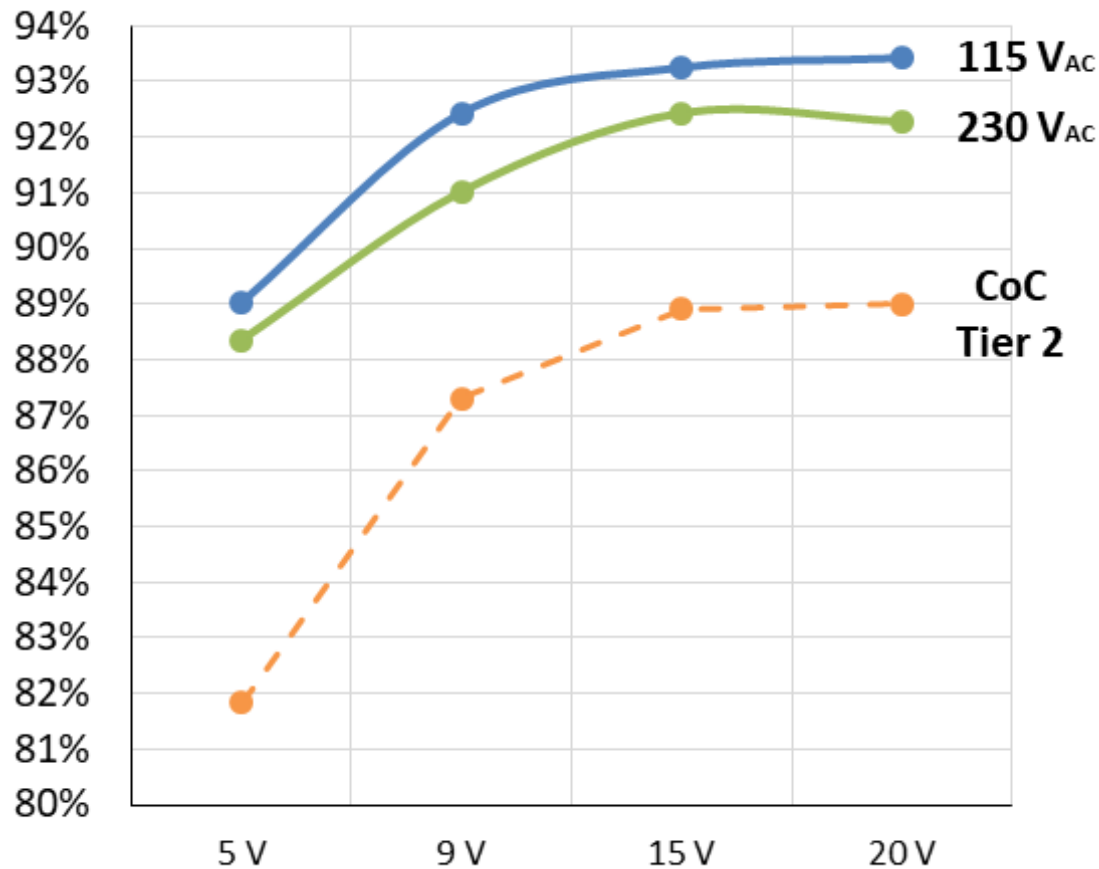


10% Load Efficiency


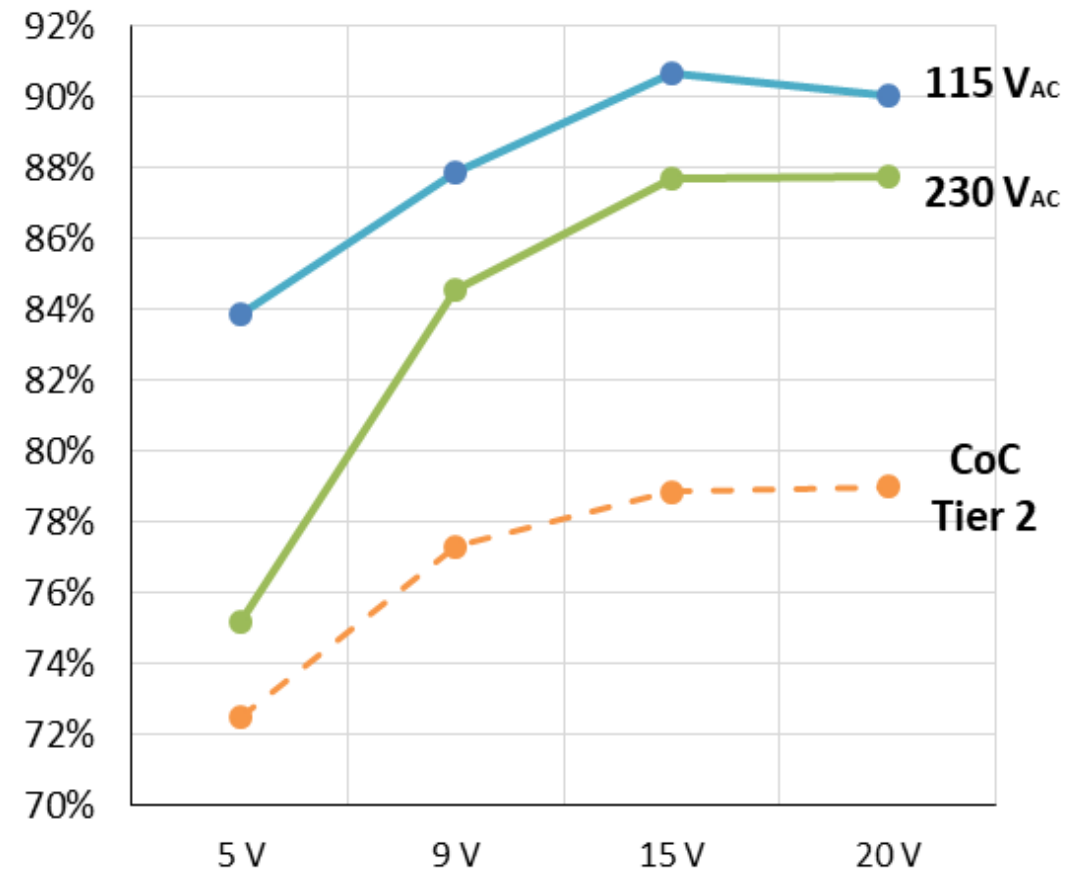


- Standby: 25 mW at 115 V_{AC}, 40 mW at 230 V_{AC} (CoC Tier 2 spec is < 75mW, DoE Level VI spec <= 210 mW)

600kHz 65W Planar Prototype

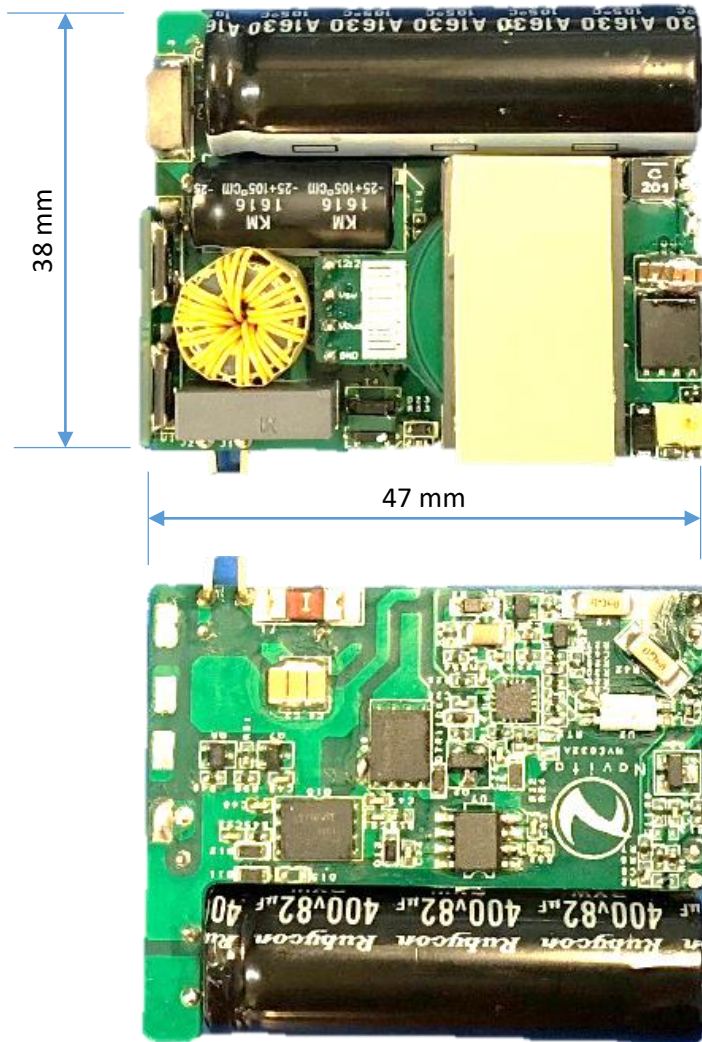


- Input : Universal AC (85-265V_{AC}, 47-63Hz)
- Output : Fixed 20 V (65W)
- Powertrain : NV6115 (160 mΩ) + NV6117 (110 mΩ) GaN Power ICs
- Control : ACF = TI UCC28780
- Frequency : 500-600 kHz
- Size : 38 x 47 x 12.5 mm = 22 cc uncased
43 x 52 x 17.5 mm = 39 cc with 2.5 mm case
- Power Density : 2.9 W/cc (47 W/in³) uncased
1.7 W/cc (27 W/in³) cased
- Construction : 4-layer, 2-oz Cu PCB, SMT powertrain
“No heatsink” design

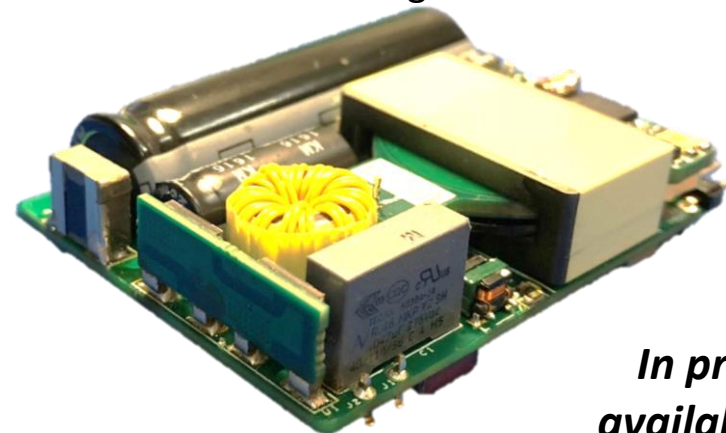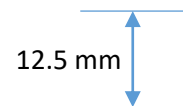



*In progress,
available Q2'18*

1MHz 150 W



State-of-the-art Si 12W/in³

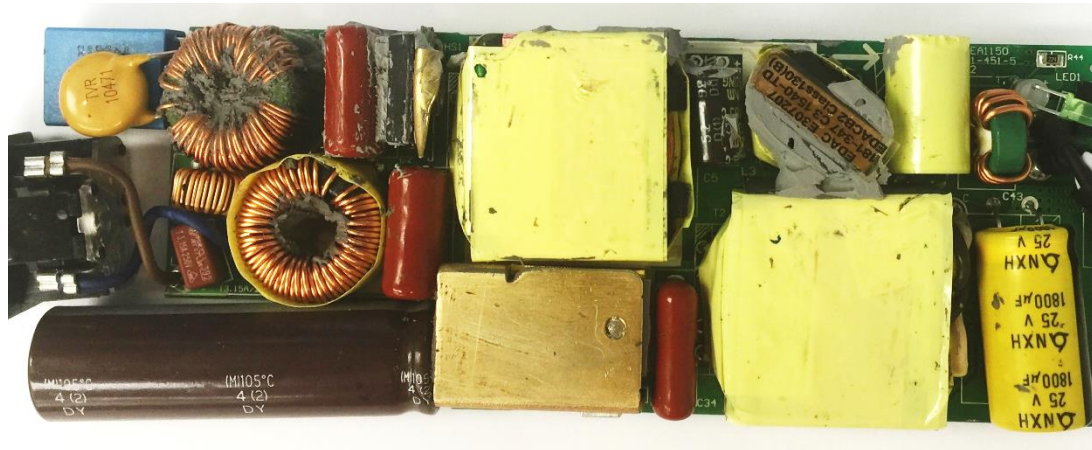

1MHz GaN 35W/in³

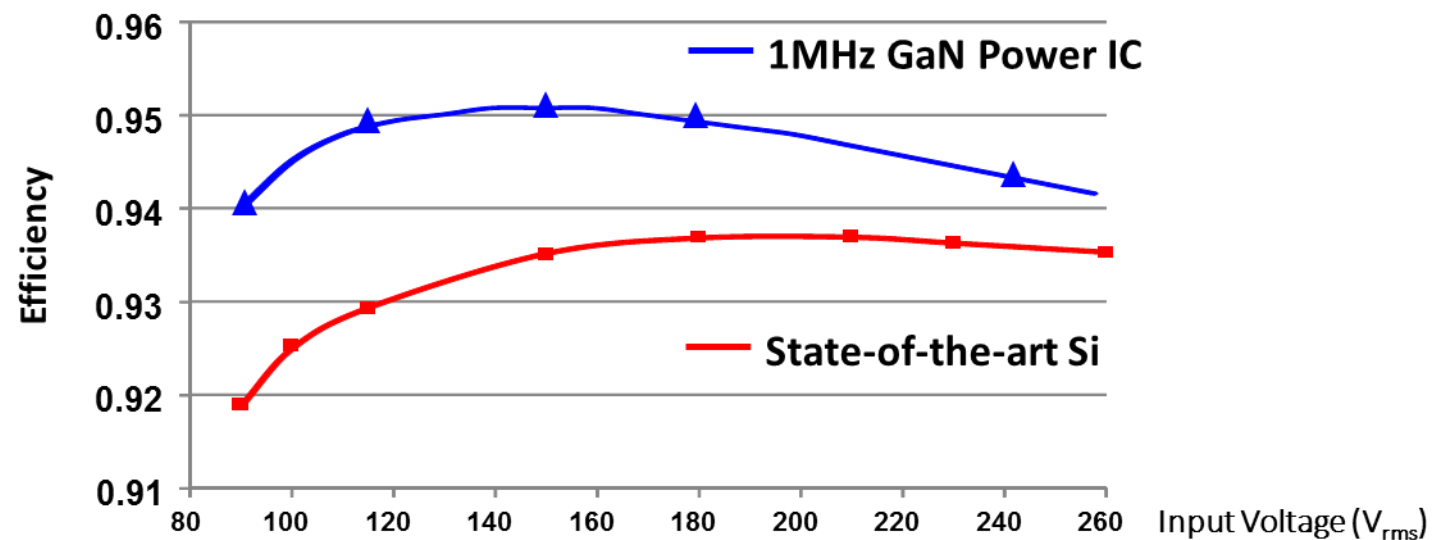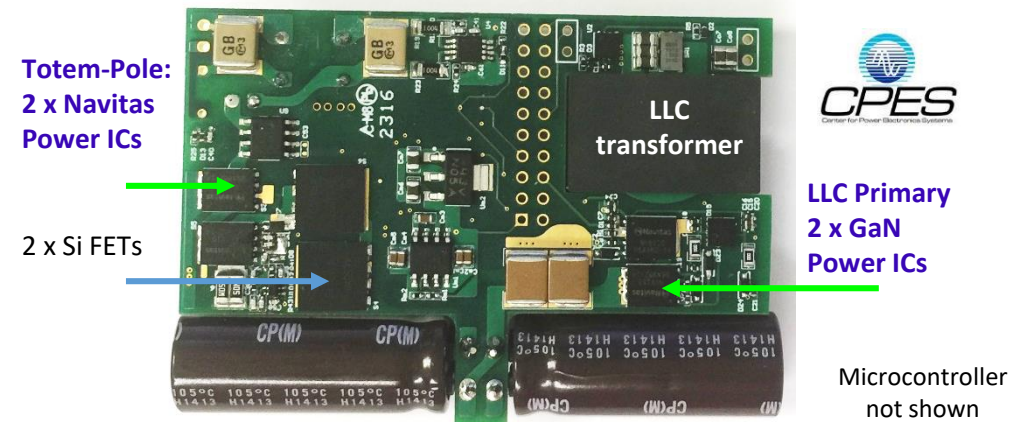


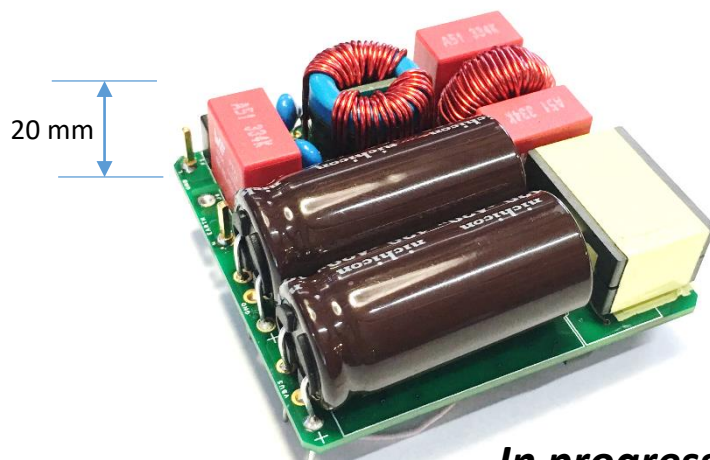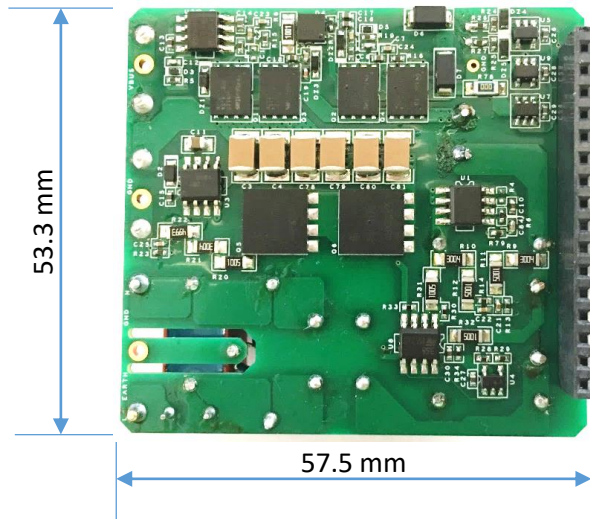1.2 MHz, 300W Totem-Pole PFC (Preliminary)



In progress, report available APEC'18

- Input : Universal AC ($85\text{-}265V_{AC}$, $47\text{-}63\text{Hz}$)
- Output : 400V (300W)
- Fast FETs : NV6117 ($110\text{m}\Omega$) GaN Power ICs
- Slow (AC) FETs : Si Superjunction ($62\text{m}\Omega$)
- Frequency : $300\text{-}1,200\text{ kHz}$
- Size : $53.3 \times 57.5 \times 20\text{ mm} = 62\text{ cc uncased}$ (*DSP controller board not included*)
- Power Density : 4.9 W/cc (80 W/in^3) uncased
- Target Efficiency : $98.5\% @ 220V_{AC}$, $98\% @ 110V_{AC}$, 97.5% at $90V_{AC}$, full load

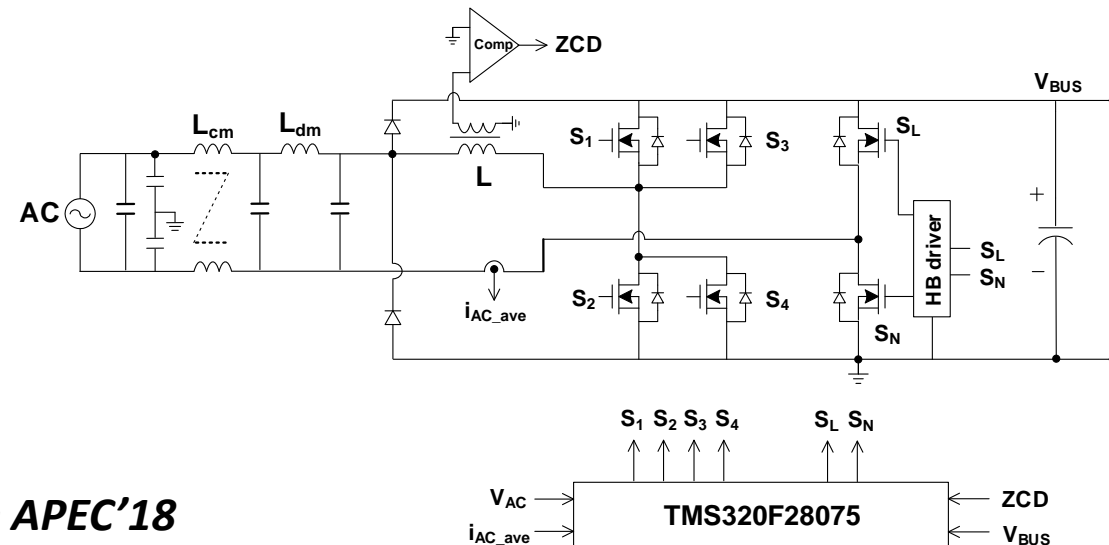

Summary

■ Navitas GaN Power IC

Enable

- Market adoption of HF magnetics
- ACF topology adoption in low power application
- HF ASIC for ACF, TP-PFC, LLC, SR invention

&

Next Generation High Power Density Adaptor

GaN



GaN Power ICs: Integration Drives Performance



纳微 Navitas

65W USB-PD