

APEC
2023



MARCH 19-23, 2023

ORANGE COUNTY CONVENTION CENTER | ORLANDO, FL

New GaNSense Half-Bridge IC Enables Next Gen High-Frequency, High-Efficiency, High-Density Topologies

Tom Ribarich

Sr. Dir. Strategic Marketing, Navitas Semiconductor


tom.ribarich@navitassemi.com



Presentation Outline

- GaNFast Power IC Evolution
- GaNSense Half-Bridge IC
- Loss Less Current Sensing
- Soft Switching
- High-Speed Topologies
- 140W-1C TTP+AHB Charger
- Motor Drive Inverter
- Conclusions & Questions

GaNFast Power IC Evolution

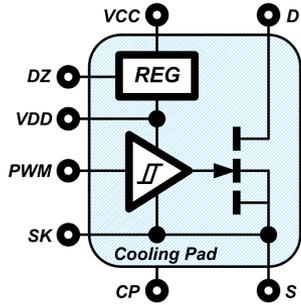


GaNFast™

- Enable GaN
- Int. gate drive + dV/dt ctrl
- Int. LDO
- Regulated gate drive voltage
- Wide range VCC & PWM
- 2kV ESD
- 650VDScont/800VDSmax
- Large cooling pad



QFN6x8

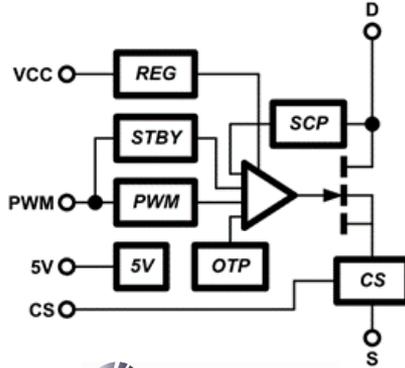


GaNSense™

- High performance GaN
- Loss-less current sensing (+0.5% efficiency)
- Int. gate drive + LDO + VREF + dV/dt ctrl
- OCP + OTP protection circuits
- Wide range VCC & PWM
- 2kV ESD
- 700VDScont/800VDSmax
- Large cooling pad



QFN6x8

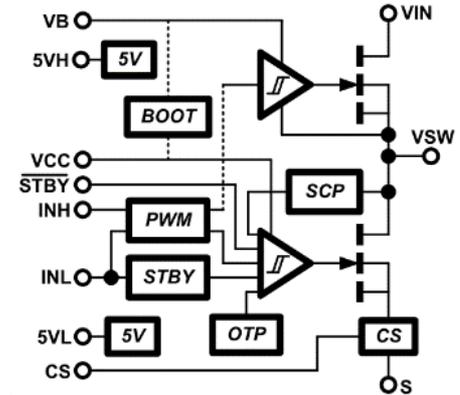


GaNSense™ Half-Bridge

- High performance GaN half-bridge
- Int. level shift + bootstrap
- Loss-less current sensing (+0.5% efficiency)
- Int. gate drive + LDO + VREF + dV/dt ctrl
- OCP + OTP protection circuits
- Wide range VCC & PWM
- 2kV ESD
- 650VDScont/800VDSmax
- Large cooling pads




QFN6x8

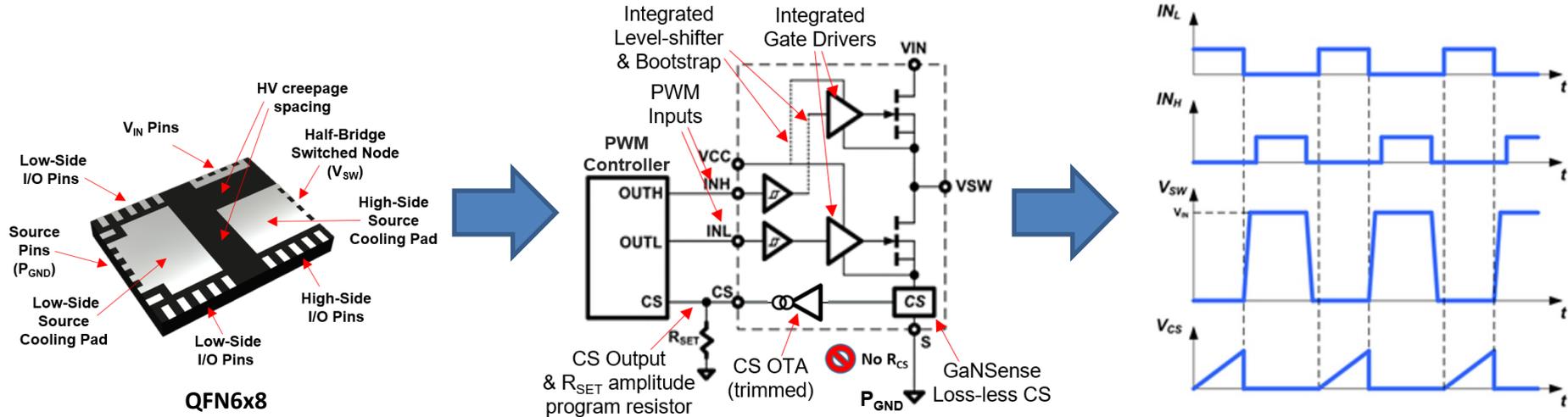GaNSense Half-Bridge IC = Highest Integration, Smallest Size, Highest Efficiency & Largest Cooling Pads




Loss Less Current Sensing = +0.5% EFF Benefit & No PCB Hot-Spot

No R_{SENSE} = +0.5% Efficiency Benefit

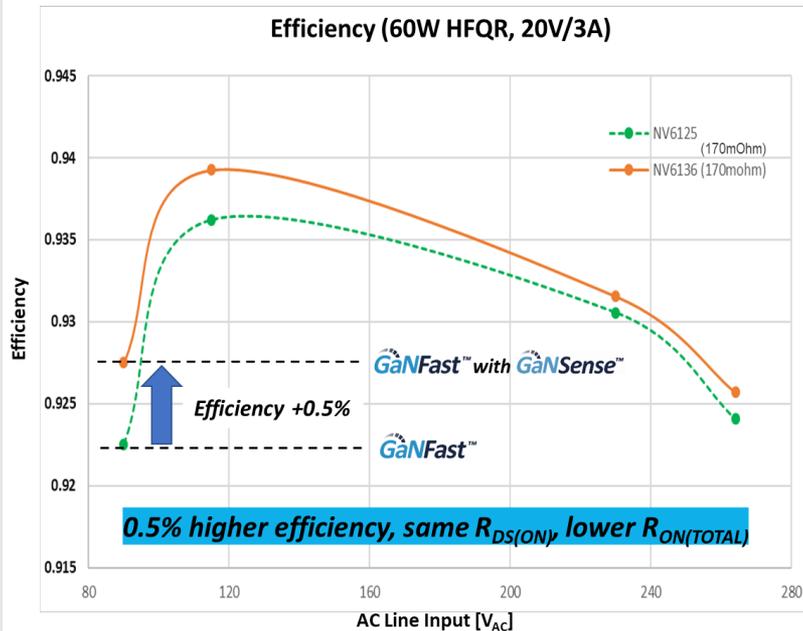

No R_{SENSE} = No PCB Hot-Spot

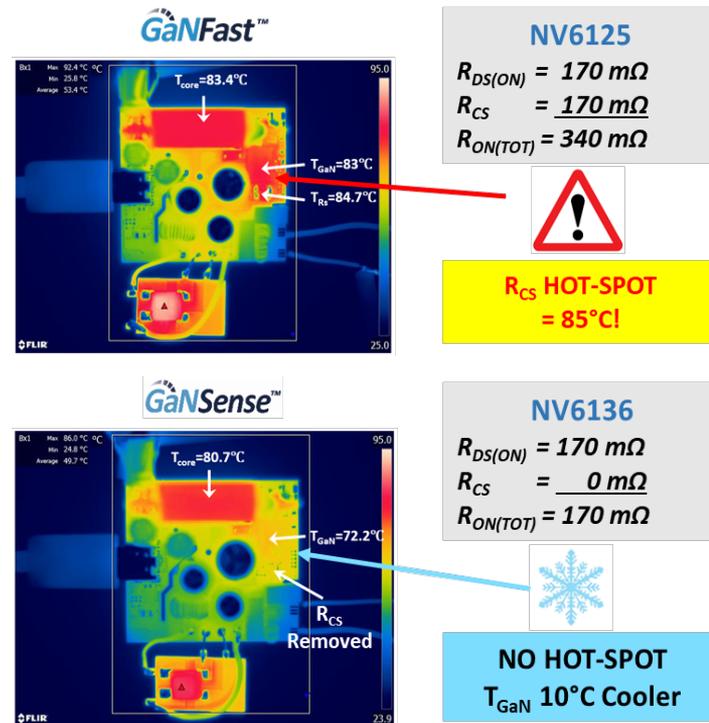

Soft Switching + GaNFast Power ICs = High Frequency & High Efficiency

Primary Silicon FET & external RCS Power Loss:

$$P_{FET} = P_{COND} * k + P_{DIODE} + P_{T-ON} + P_{T-OFF} + P_{DR} + P_{QRR} + P_{QOSS}$$

P_{COND} → $R_{DS(ON)}$ Loss
 k → Duty Cycle Loss
 P_{DIODE} → Reverse Conduction Loss
 P_{T-ON} → Switch-ON Transition Loss
 P_{T-OFF} → Switch-OFF Transition Loss
 P_{DR} → Gate Drive Loss
 P_{QRR} → Reverse Recovery Loss
 P_{QOSS} → Output Capacitance Loss

$$P_{RCS} = P_{COND} \rightarrow R_{CS} \text{ Loss}$$


Primary GaNFast Power IC & GaNSense Loss-Less Current Sensing Power Loss:

$$P_{FET} = P_{COND} * I_{MINIMIZED} + P_{DIODE} * I_{MINIMIZED} + P_{T-ON} + P_{T-OFF} + P_{DR} + P_{QRR} + P_{QOSS}$$


$$P_{RCS} = P_{COND}$$

Soft-switching and GaNFast Power ICs **ELIMINATE** turn-on & reverse recovery losses & **MINIMIZE** drive, deadtime, and device charging losses
 GaNSense loss-less current sensing **ELIMINATES** RCS conduction losses

Enabling Next Gen, High Speed Topologies

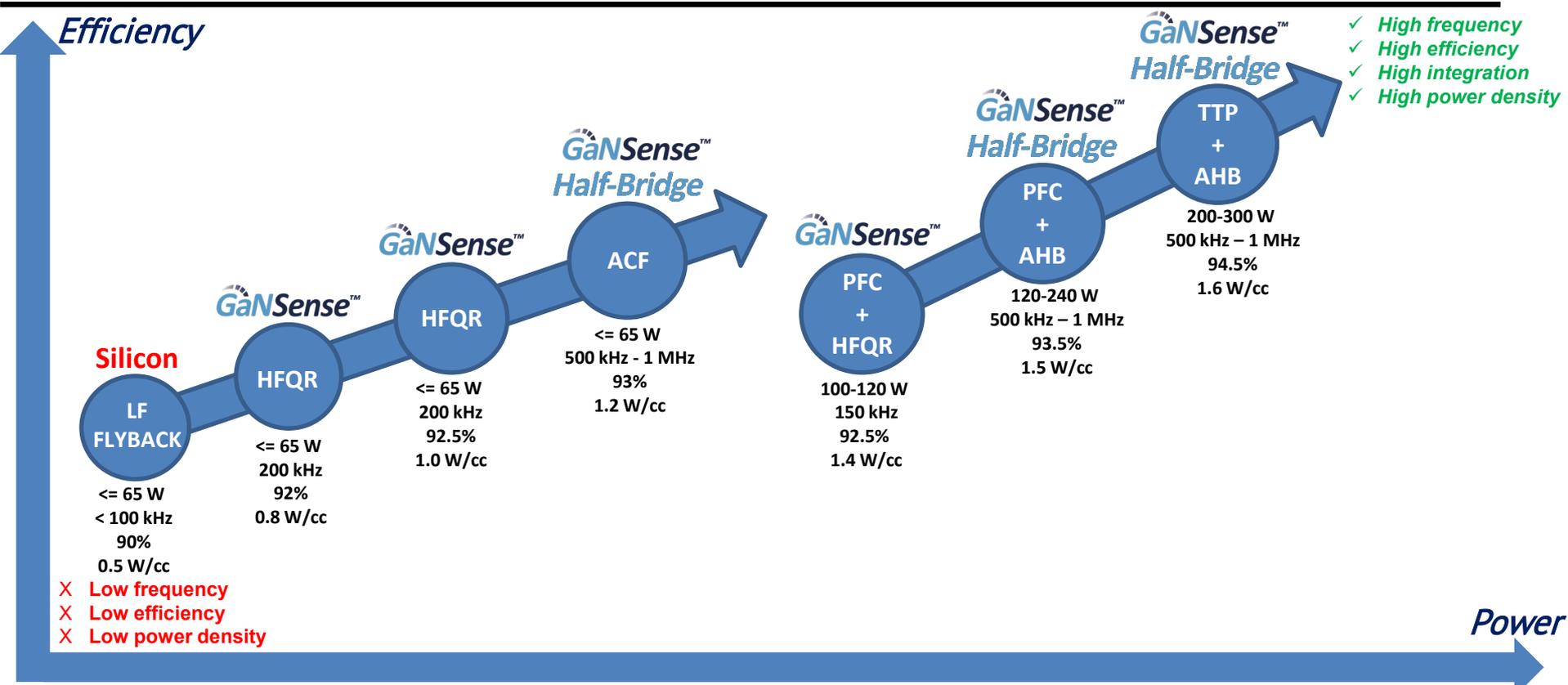


AHB = Asymmetrical Half-Bridge

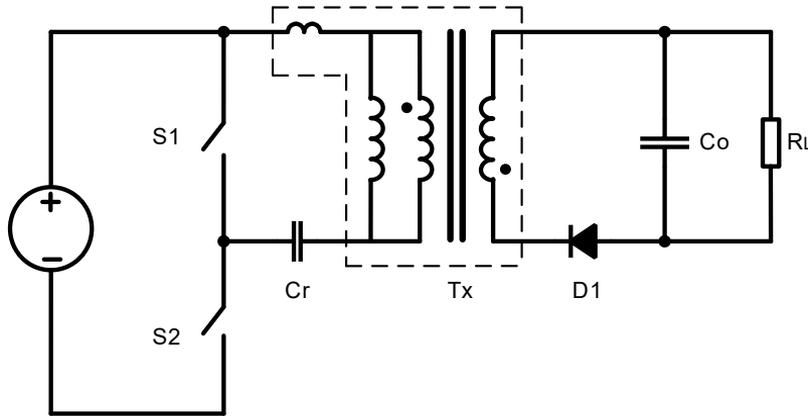


AHB Benefits

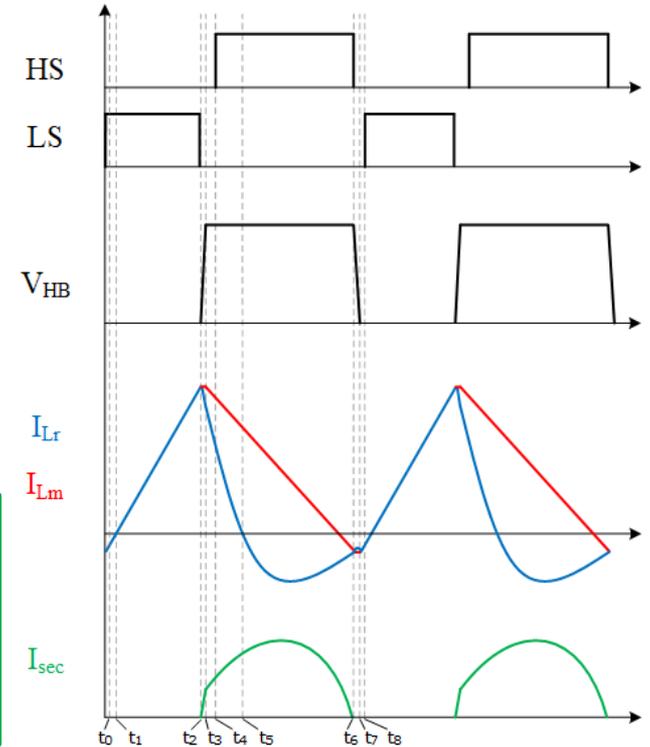
- ✓ **High efficiency** → **Reduces losses, enables small charger size**
- ✓ **ZVS operation** → **Enables HF, reduce component size/cost**
- ✓ **No reflected V_{out}** → **Reduced VDS stress**
- ✓ **Variable V_{out}** → **Enables USB-C PD3.1**




TTP = Totem Pole PFC

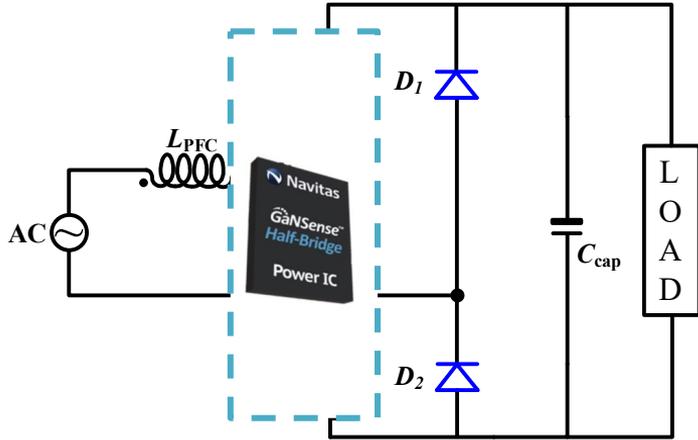

Positive AC line cycle

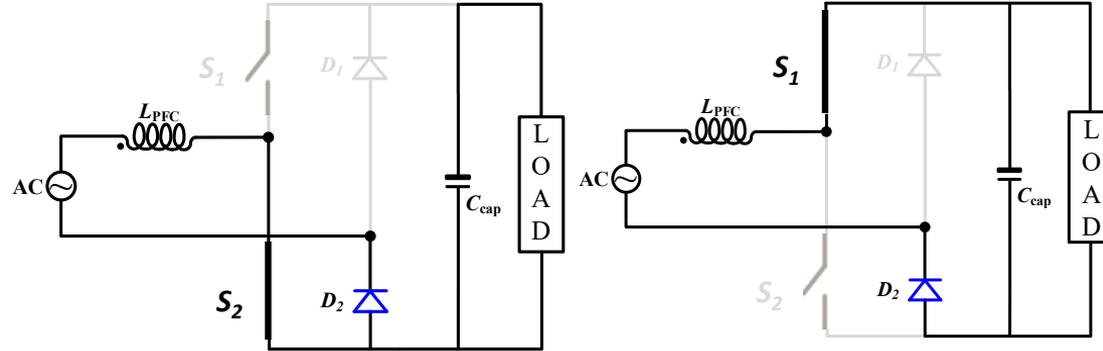

Negative AC line cycle

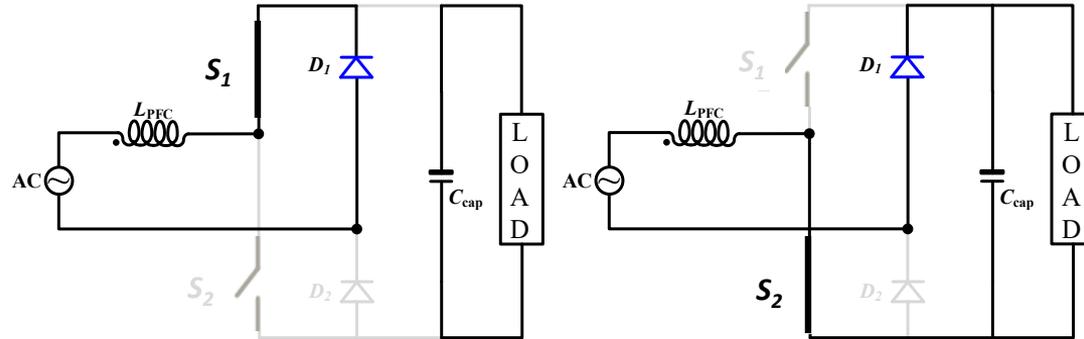




TTP Benefits

- ✓ **No Input Bridge** → **High efficiency**
- ✓ **GaN Zero Qrr** → **CRM & CCM modes**
- ✓ **GaN High Frequency** → **Small inductor size**

140W-1C TTP+AHB = 130cc = 1.1W/cc

PFC Inductor Planar XFMR

NV6247C

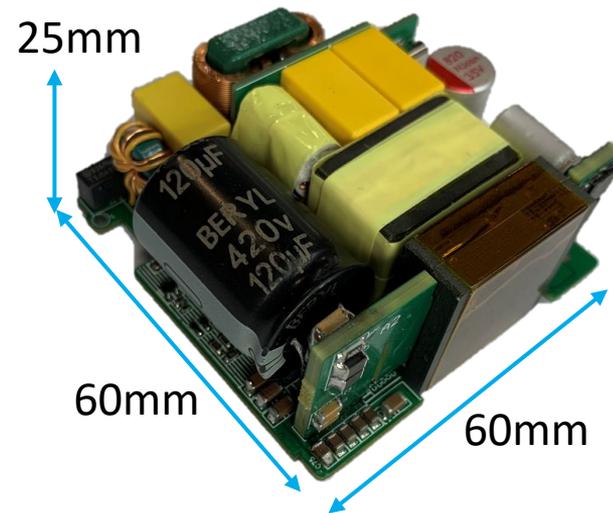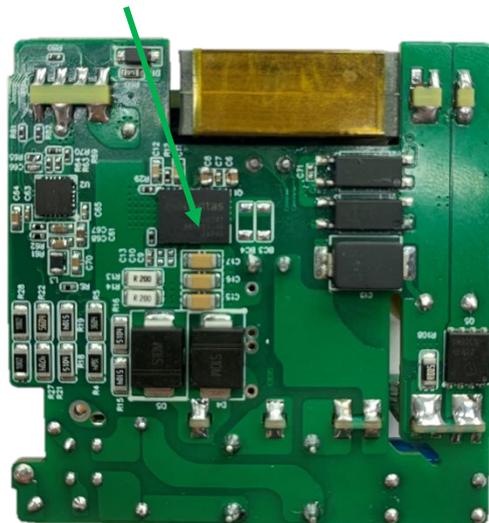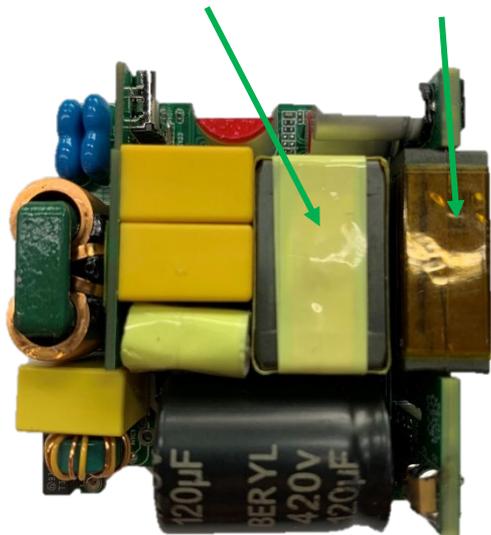

- ✓ PCBA size: 60 x 60 x 25mm = 90cc
- ✓ Cased size (est.) = 65 x 65 x 30mm = 130cc
- ✓ Power Density = 1.1 W/cc


Clean & Sinusoidal TTP Waveforms

Boost Circuit Waveforms ($V_{in}=115VAC$, $P_o=140W$)




- Clean Boost Circuit Waveforms
- CRM Operating Mode

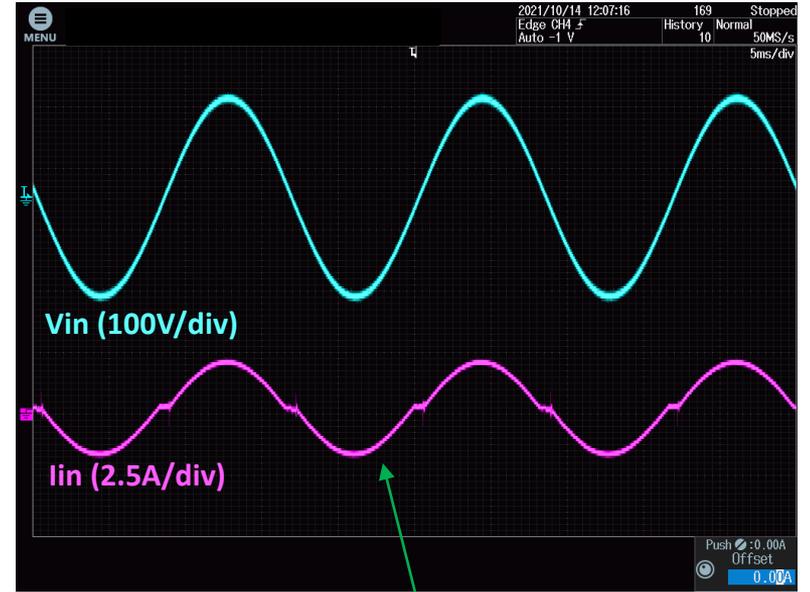AC Input Waveforms ($V_{in}=115VAC$, $P_o=140W$)




- Sinusoidal Input Current
- High Power Factor = 0.997

Clean & Smooth AHB ZVS Waveforms

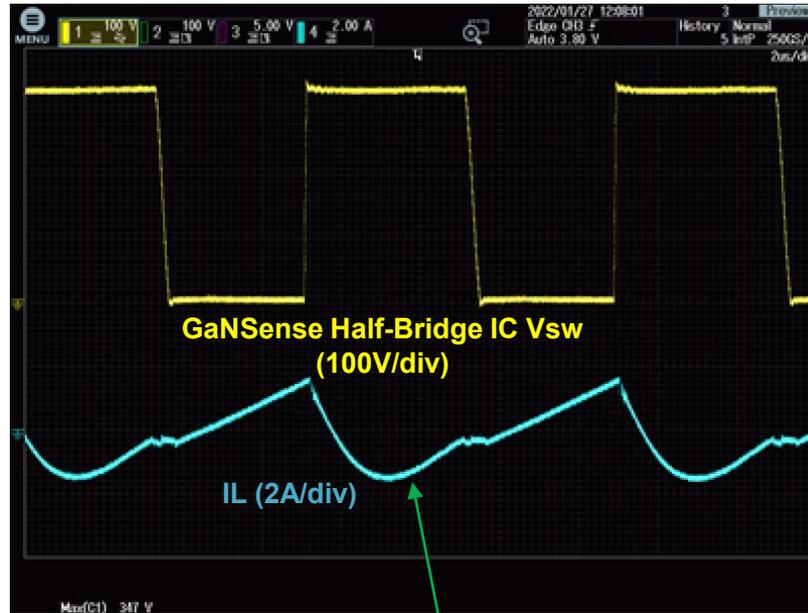

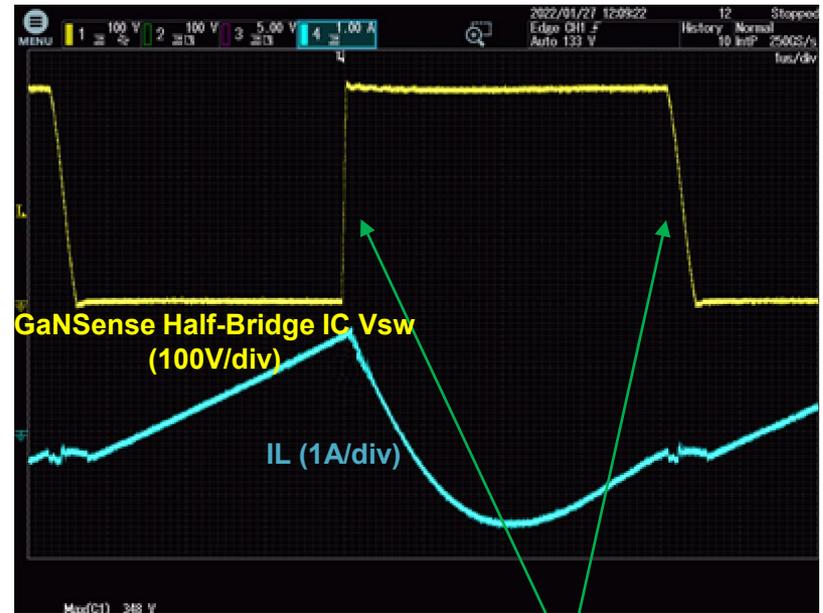
- AHB Tank Current
- Resonant Mode Operation




- GaN Half-Bridge Switched Node
- Resonant ZVS Switching

Highest Efficiency = Lowest Losses = Smallest Size


4 Point Efficiency

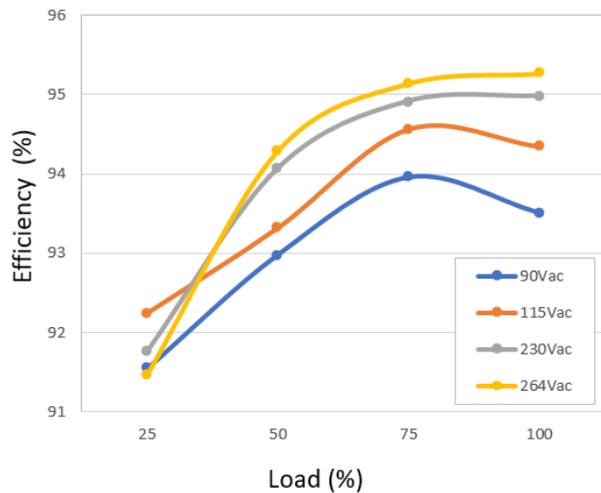

Average Efficiency

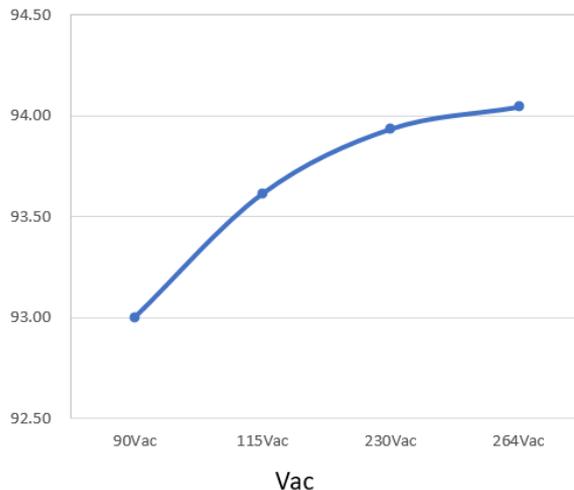


Max Load Efficiency

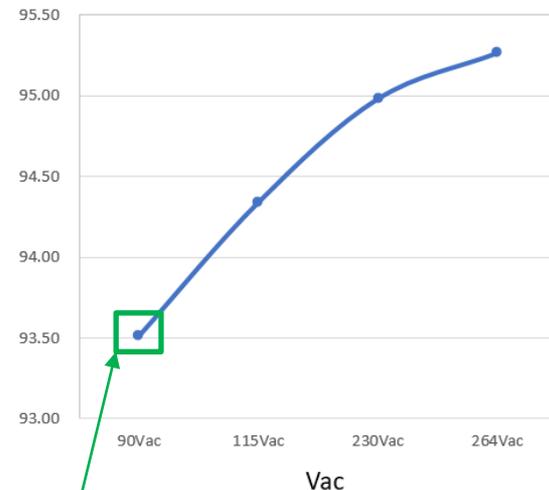


- EFF = 93.5% @ 90VAC/140W/20V/7A
- +1% EFF increase vs existing solutions!

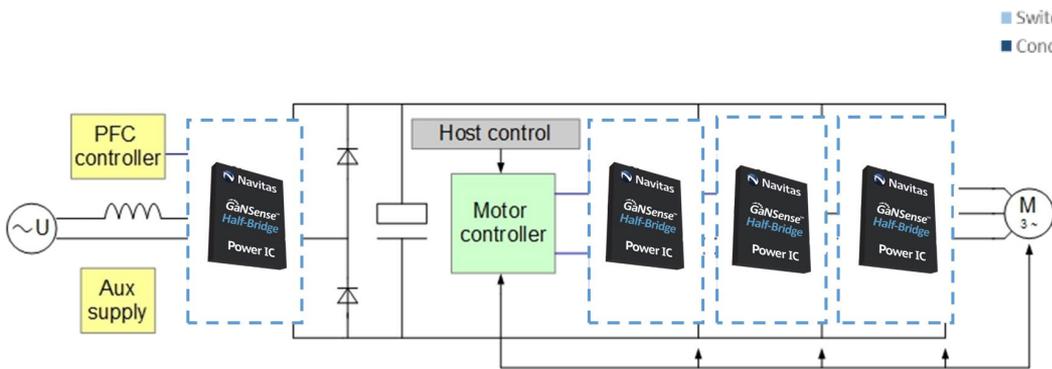GaNSense Half-Bridge ICs Enable Inverter Motor Integration



■ Switching Losses
■ Conduction Losses

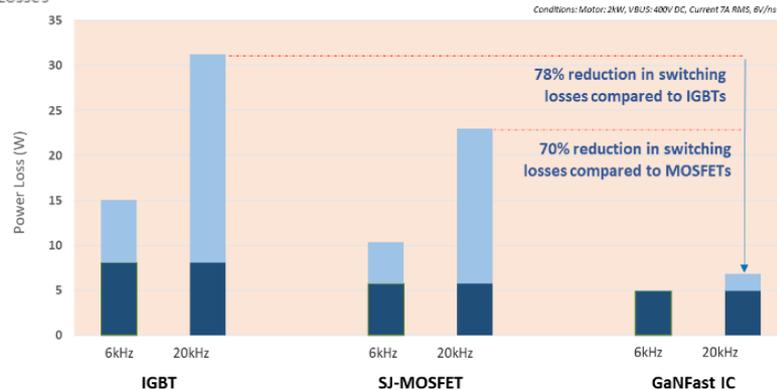Power Loss Comparison between IGBT, SJ-MOSFET, and GaFast IC in Motor Drives




- **Motor Drive:** compact, high efficiency, reduced thermal management
- **TTP PFC:** highest efficiency, fewest components and smallest footprint
- **Aux Supply:** compact, efficient HFQR topology

- GaN Power ICs benefits for 2kW motor drive
 - Inverter efficiency increases 2.5% (96%→ 98.5%)
 - Total losses reduced 50% (15W→6.8W)
 - Significant reduction in cost, weight and size of thermal management (heatsink, fans, etc.)


Ref: "Autonomous GaN Power ICs Deliver High-Performance, Reliable Motor Drives", [white paper](#), Hesener, May 2022

Fast, Smooth, Cool & Clean Motor Drive


> 99% Efficiency

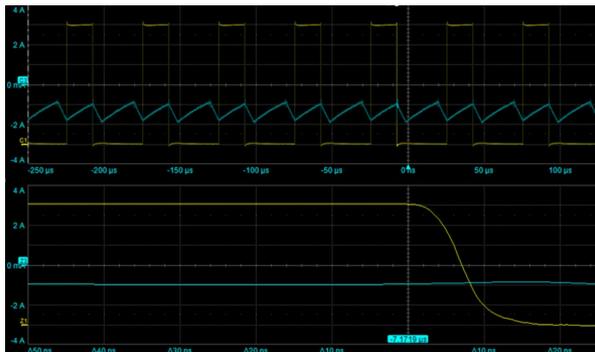


✓ Fast & Smooth Switching

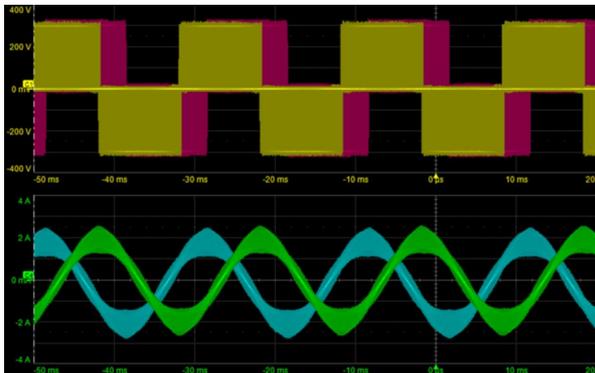


✓ Clean Sinusoidal Waveforms

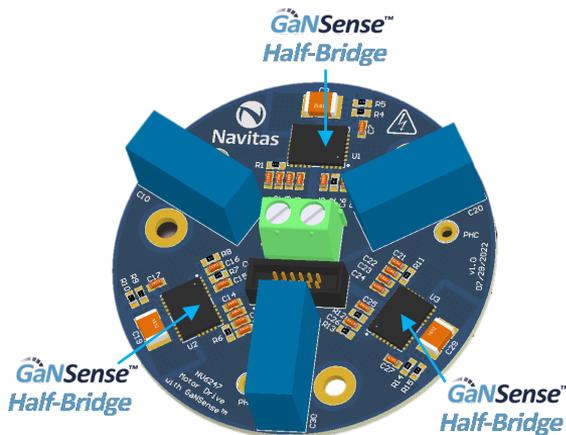

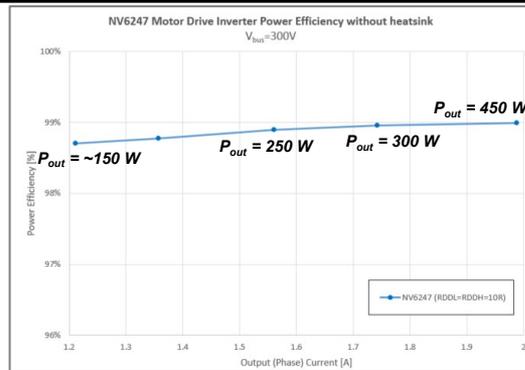Navitas 300W
3-phase Motor
Inverter Board



✓ Peak Efficiency > 99%

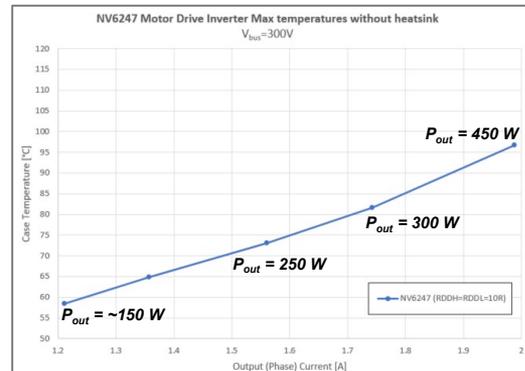

✓ Cool Temperatures w/out Heatsinks

Acknowledgements & Questions

Special Thanks To:

- *Xiucheng Huang (Navitas)*
- *Akos Hodany (Navitas)*

