



# State-of-the-Art Mobile Charging: Topologies, Technologies and Performance

PSMA Industry Session IS05: Mobile Applications

Tom Ribarich, Dir. Systems Engineering, [tom.ribarich@navitassemi.com](mailto:tom.ribarich@navitassemi.com)


Stephen Oliver, VP Sales & Marketing, [stephen.oliver@navitassemi.com](mailto:stephen.oliver@navitassemi.com)

March 29<sup>th</sup> 2017


# Getting to Fast...

- Topology / technique
  - Hard-switch → Soft switch (ZVS)
  - New technology enables new topologies to be commercially viable
- Switch technology
  - Si Bipolar → Si FET → Discrete / Cascoded GaN → GaN Power ICs
- Magnetic Materials
  - New compounds / alloys, optimized for high frequency


# Fast → Small

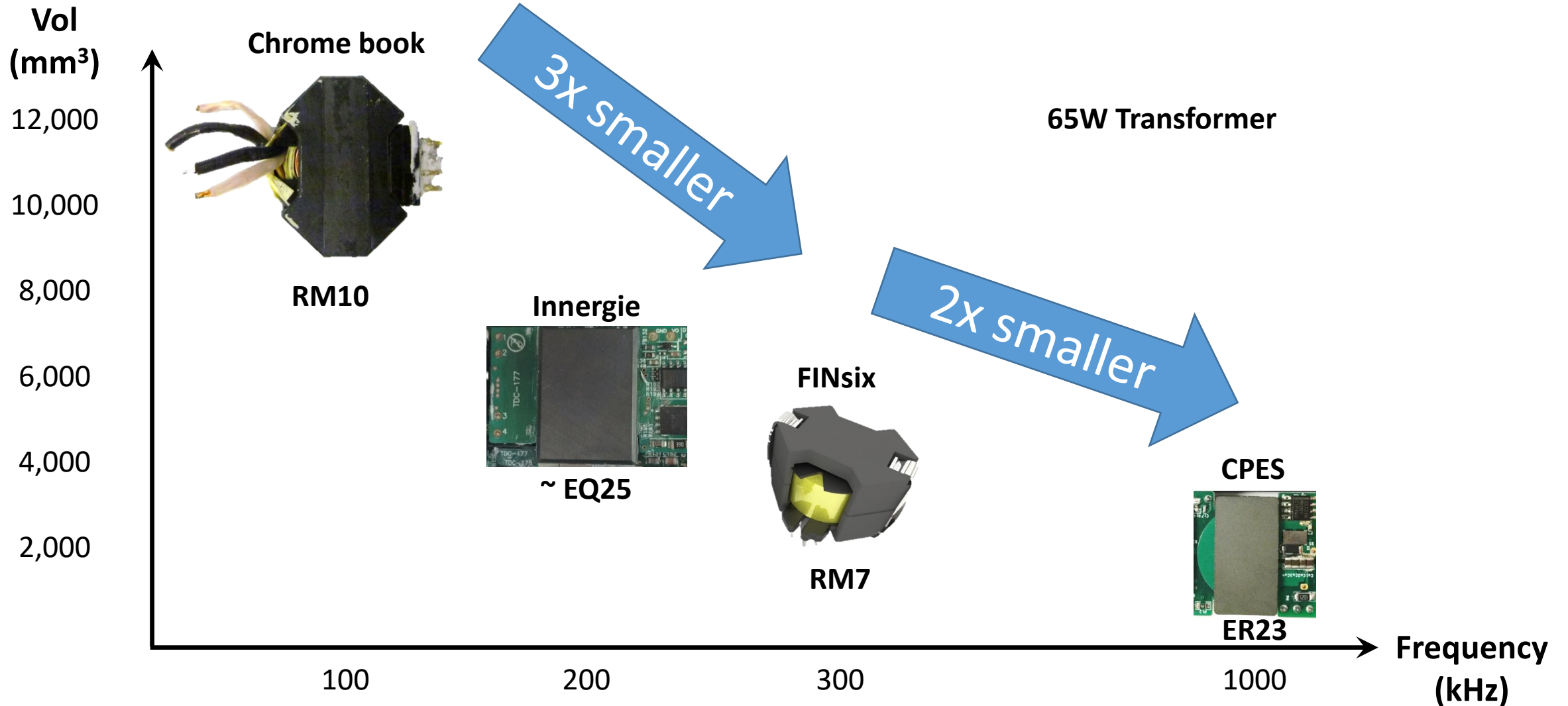

# Adapter Density 2016:


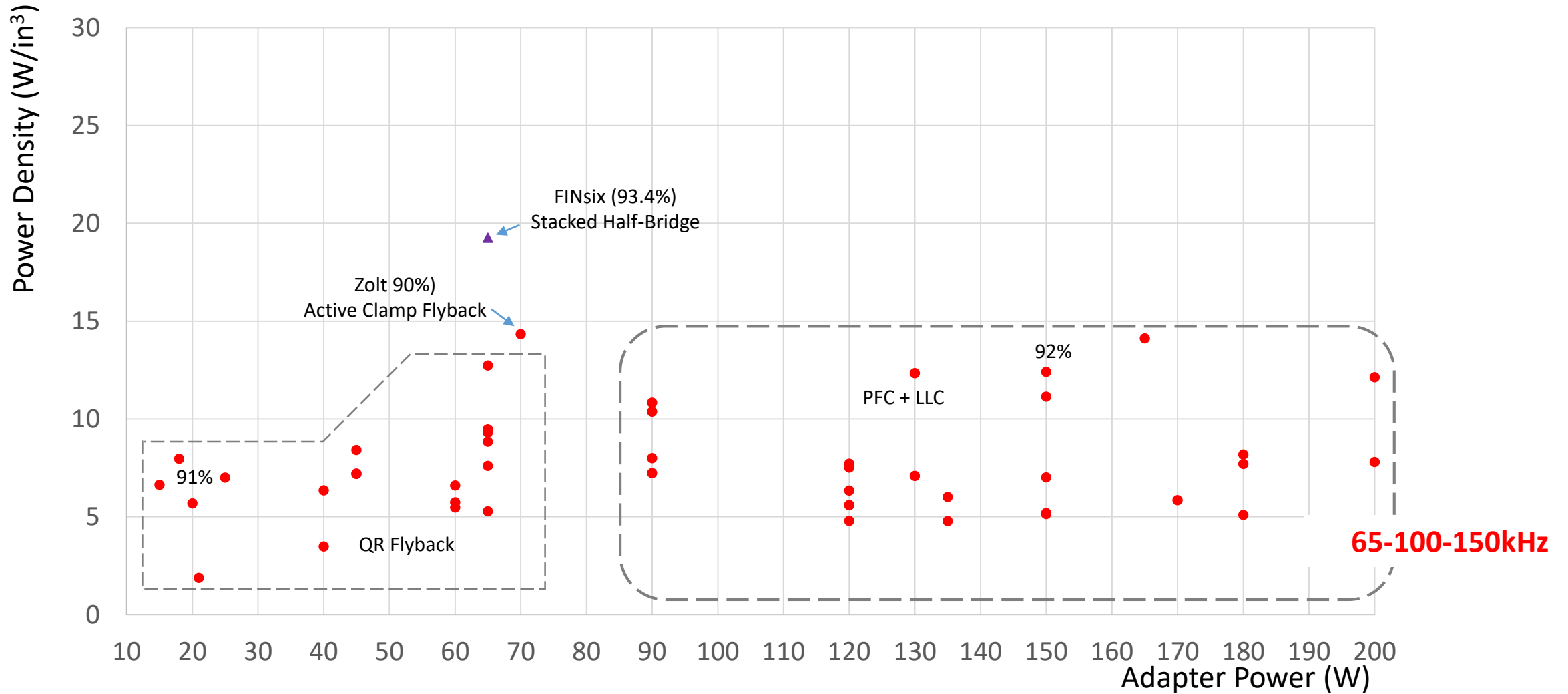


# Frequency Drives Size

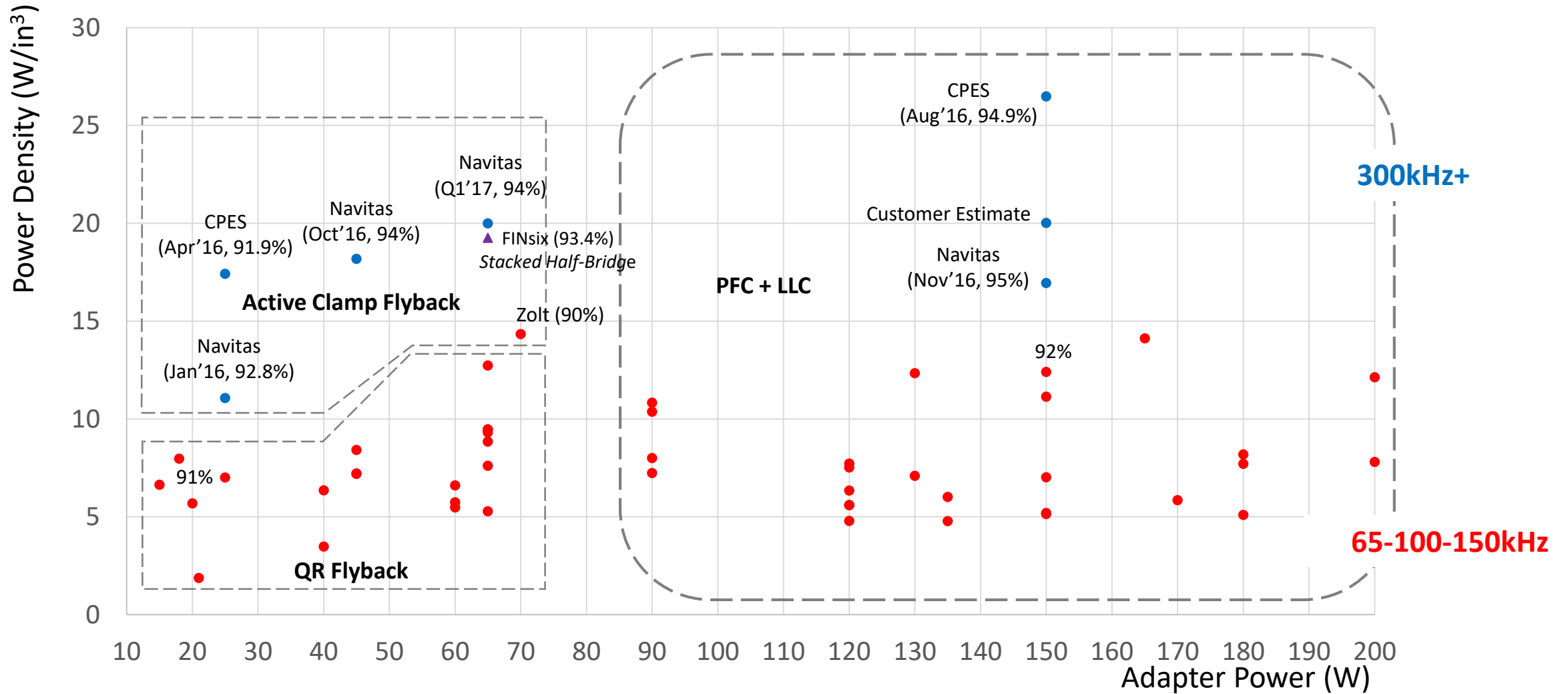
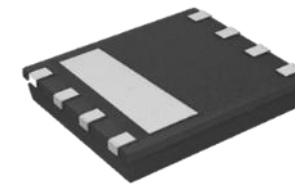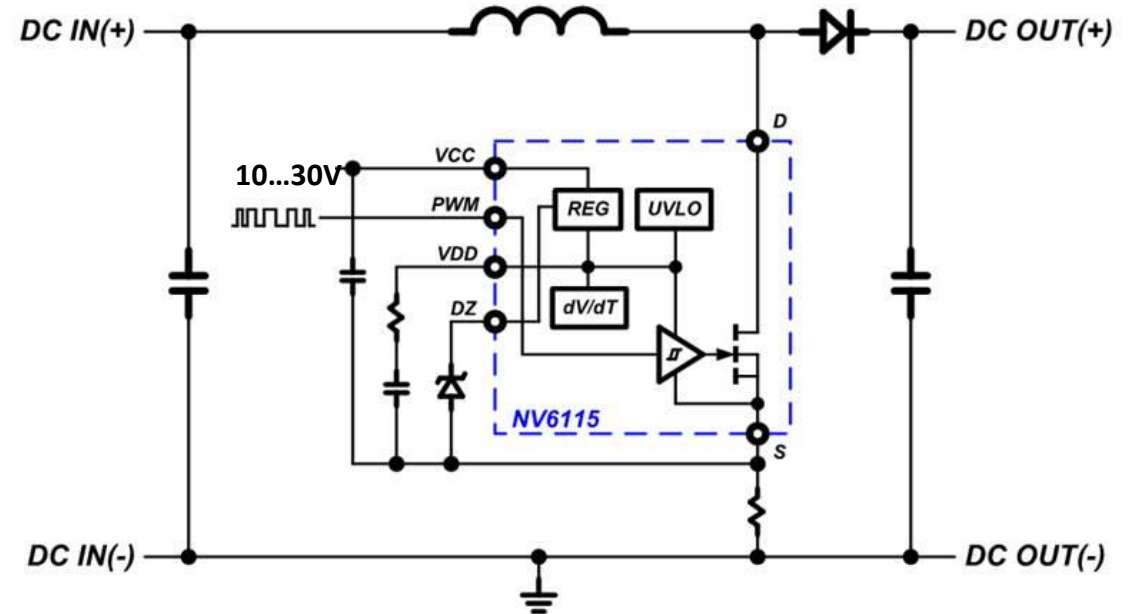
# GaN Power IC: High-Speed FET, Driver & More


- Proprietary AllGaN™ technology
- **Monolithic** integration of GaN FET, GaN Driver, GaN Logic
- 650 V eMode
- 20x lower drive loss than silicon (<35 mW at 1 MHz)
- Driver impedance matched to power device
- Very fast (prop delay and turn-on/off of 10-20 ns)
- Zero inductance turn-off loop
- High dV/dt immunity (200 V/ns) with control
- Digital input
- Complete layout flexibility



QFN 5x6mm
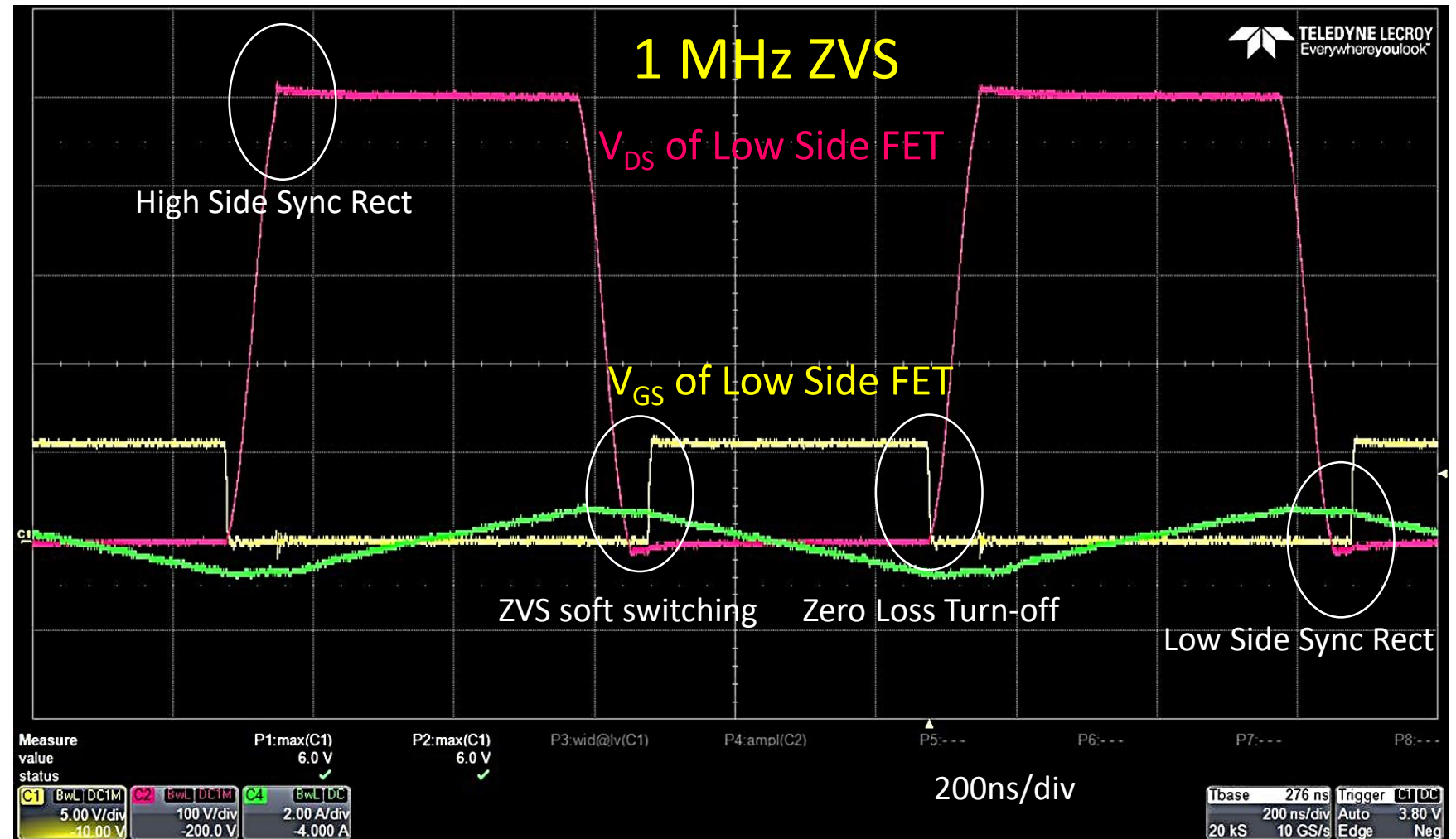
# GaN Power IC – *Fast & Efficient*


- 500 V Switching
- No overshoot / spike
- No oscillations
- ‘S-curve’ transitions
- Zero Loss Turn-on
- Zero Loss Turn-off
- Sync Rectification
- High frequency
- Small, low cost magnetics



# Half-Bridge iDrive GaN Power IC




PQFN 6x8 mm

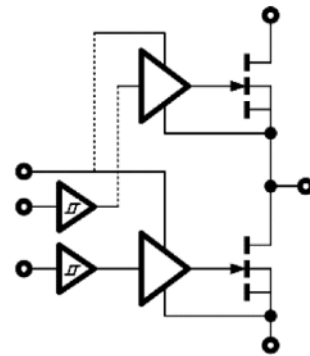

Simplified Schematic


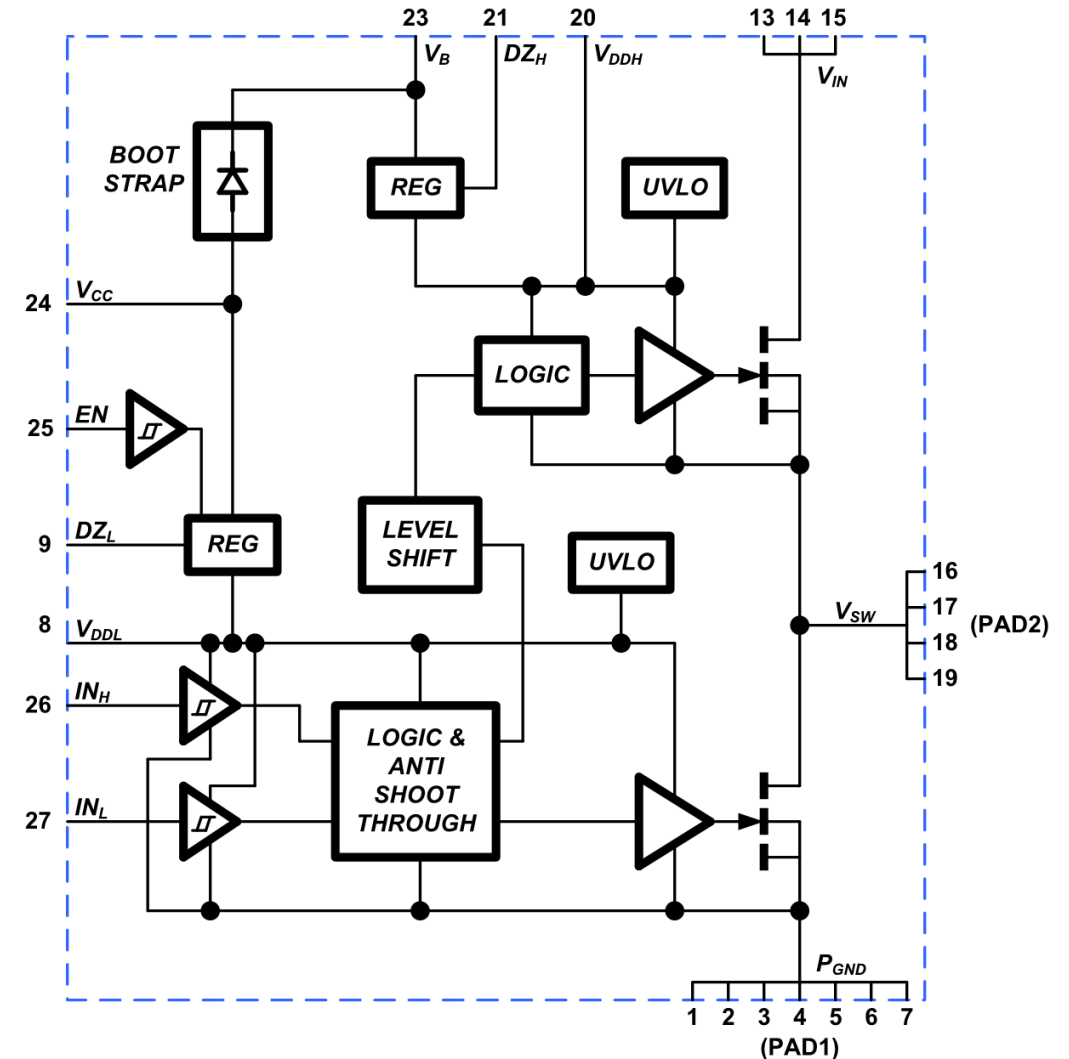
- Internal level-shift, bootstrap
- Range from (2x) 160-560 mOhm (650V)
- Single component
- Ground-referenced control
- Active Clamp Flyback, Half-Bridge, LLC, etc.







# High Frequency Magnetics

## N59 optimized for 2MHz

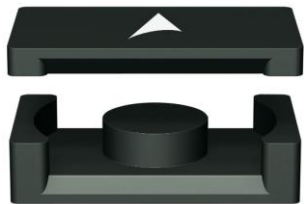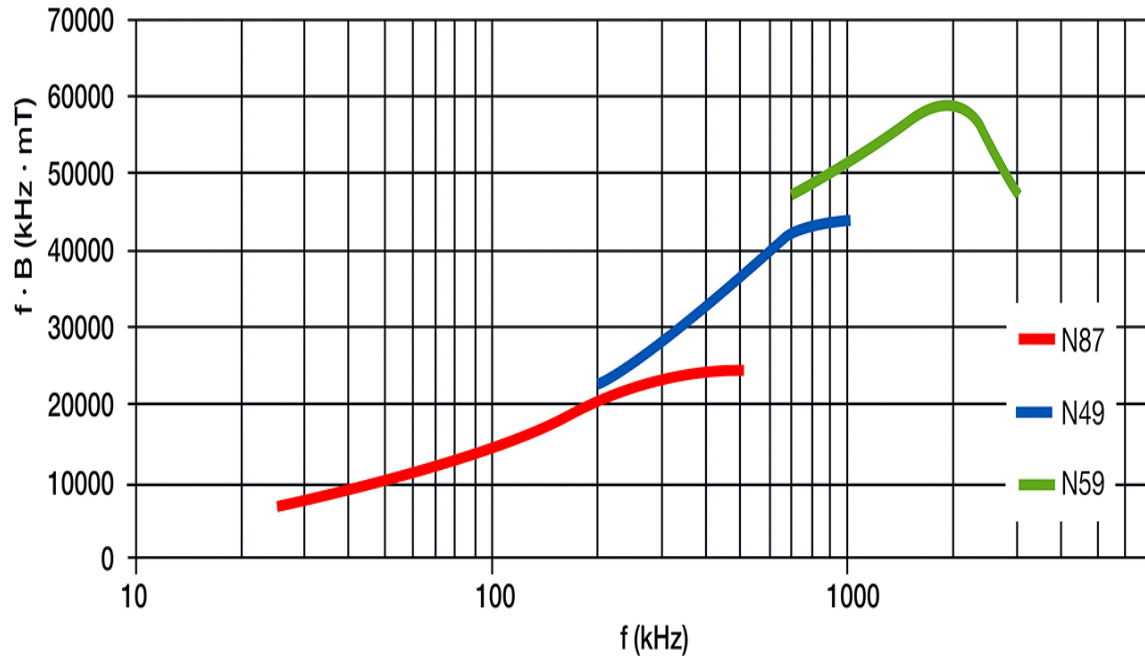

## 3F & 4F up to 10MHz

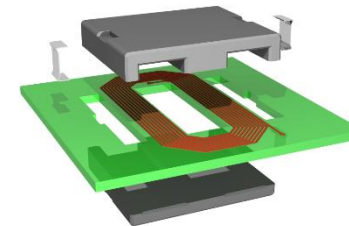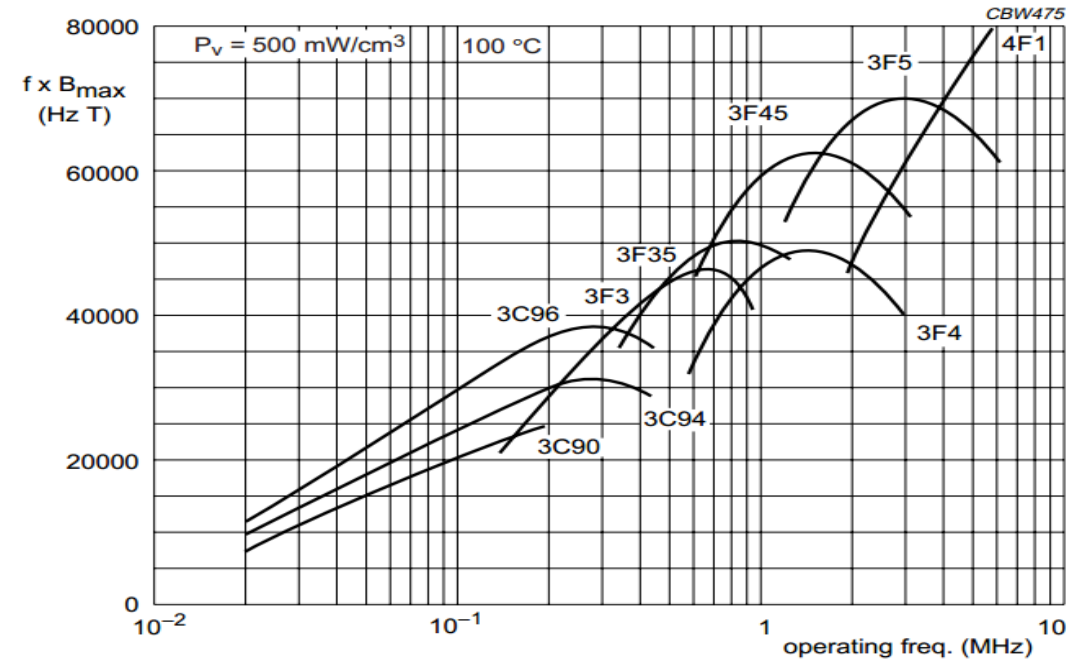

TDK/EPCOS N59/PC200  
Hitachi Metals ML91S  
ACME P61


: <https://en.tdk.eu/tdk-en/374108/tech-library/articles/products---technologies/products---technologies/low-losses-at-high-frequencies/1206400>  
: <http://www.hitachi-metals.co.jp/e/press/news/2016/n0404.html>  
: <http://www.acme-ferrite.com.tw/en/material.asp>, <http://www.acme-ferrite.com.tw/investor/m3.pdf>

# Fast Chargers ... going "GaN Fast"
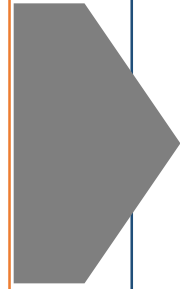
## 3x Fast Charging with 50% Energy Savings

**Existing Si-based  
15W**


**100 kHz  
Up to 6.5 W/in<sup>3</sup>  
88%**



**AllGaN™ 2016  
25W**

*2x Faster Charging*

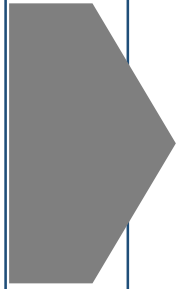**300-500 kHz  
11 W/in<sup>3</sup>  
>92%**



**AllGaN™ 2017  
25W**

*3x Faster Charging*

**>1 MHz  
17.5 W/in<sup>3</sup>  
>95%**



Smartphones & Tablets






Fast-charging Drones




AR / VR & Wearables
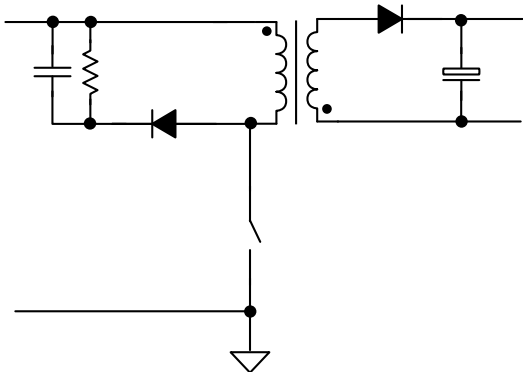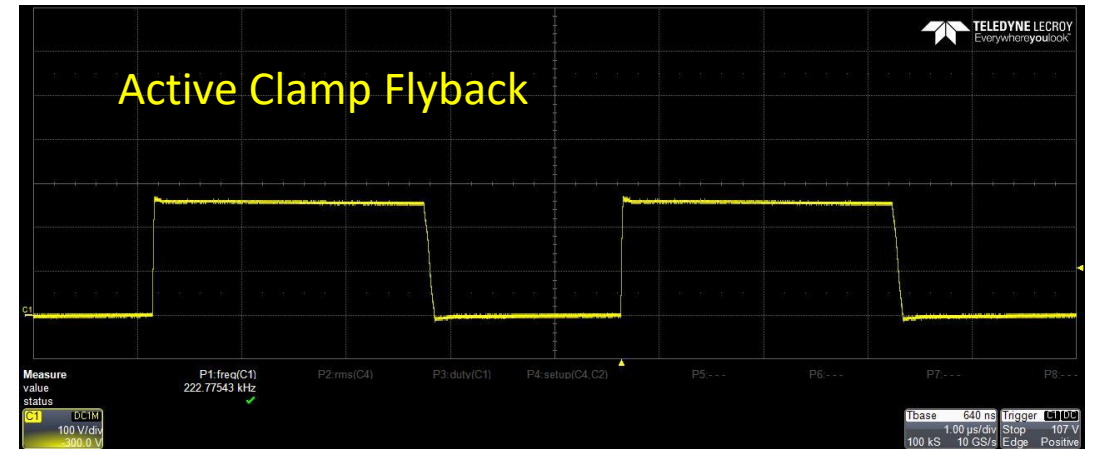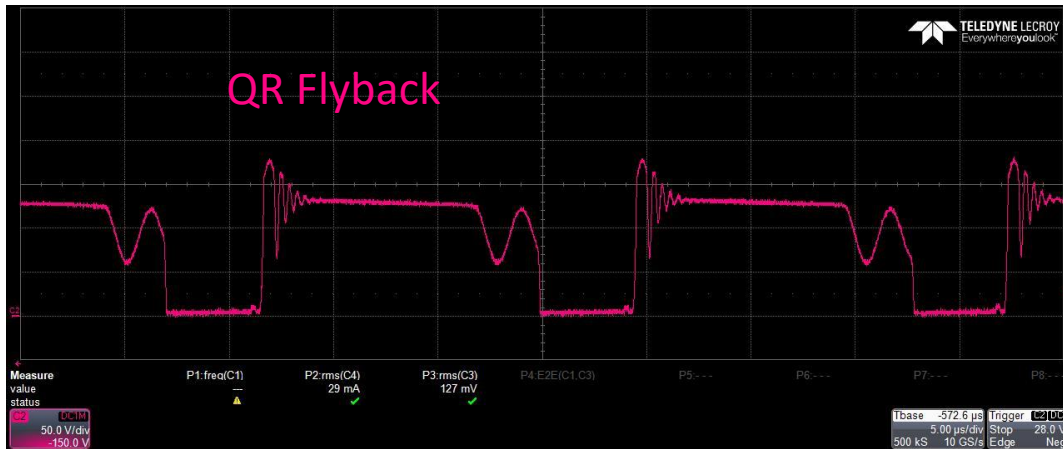
# Quasi-Resonant (QR) vs. Active Clamp Flyback (ACF)



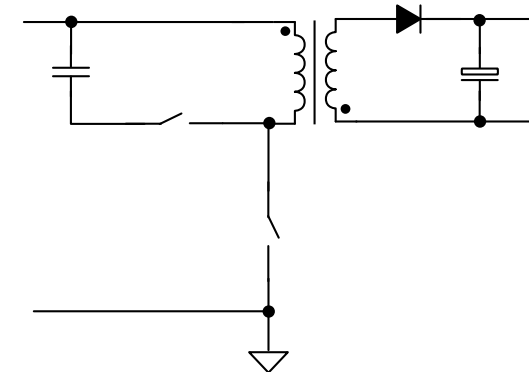- High loss in RCD snubber circuit
- Partial hard switching at high line
- Losses increase with switching frequency




- No resistor needed in the snubber: no snubber loss
- Full range zero-voltage switching (ZVS): no switching loss
- ACF enables high switching frequency


# 25W ACF: 66% More Power



Original 15 W case


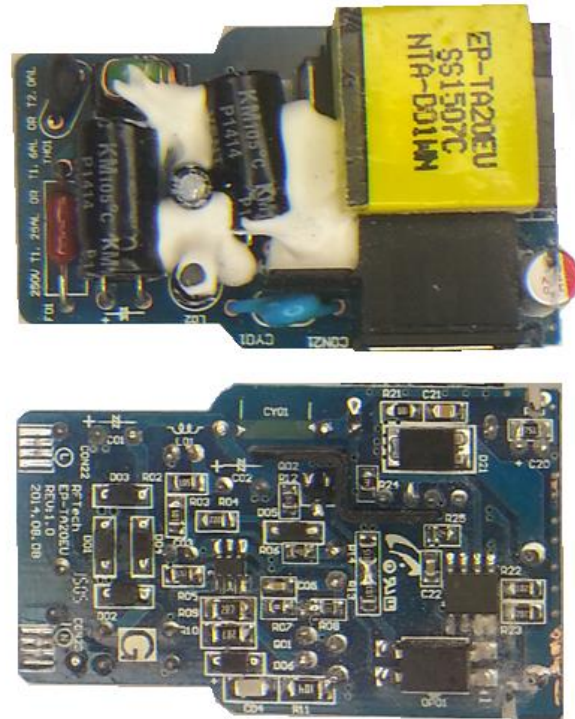


Original 15 W  
Si-based QR Flyback  
~100 kHz

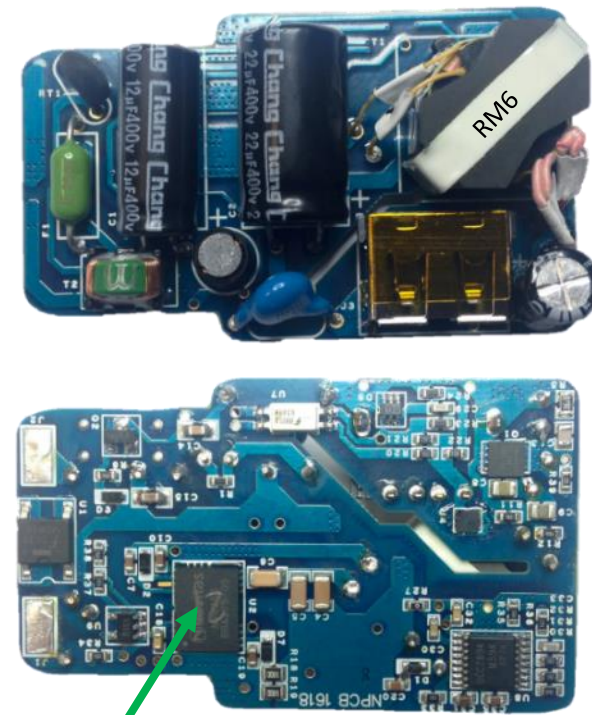


NV6250  
Upgraded 25 W  
Half-Bridge GaN Power IC ACF  
~400 kHz


# 45W ACF

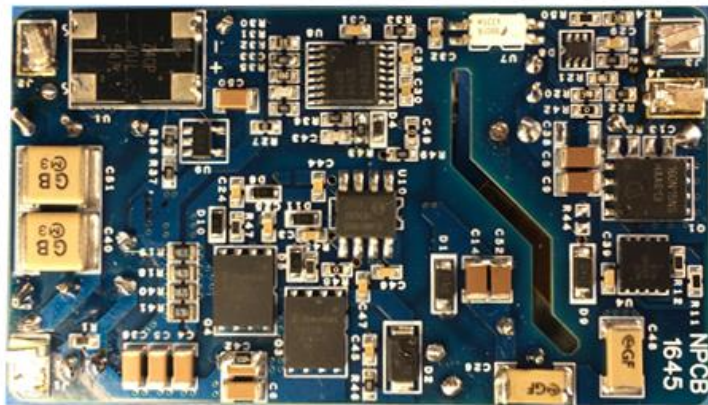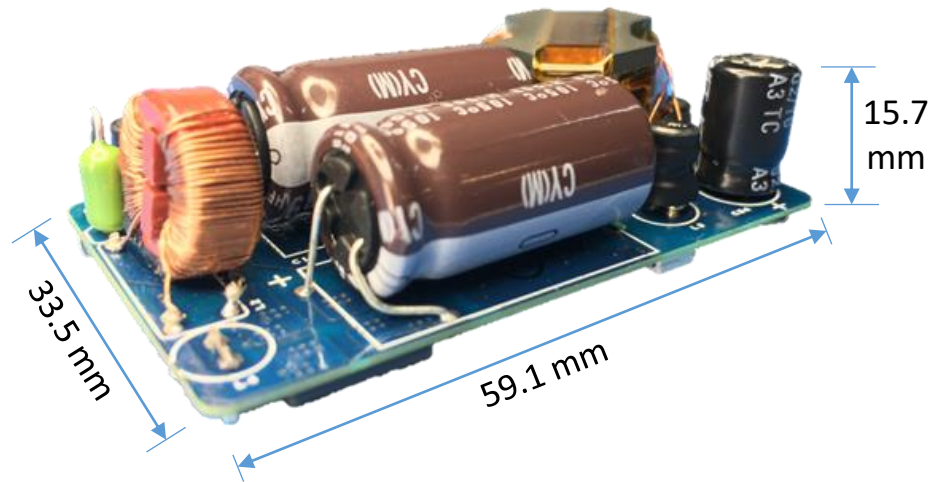

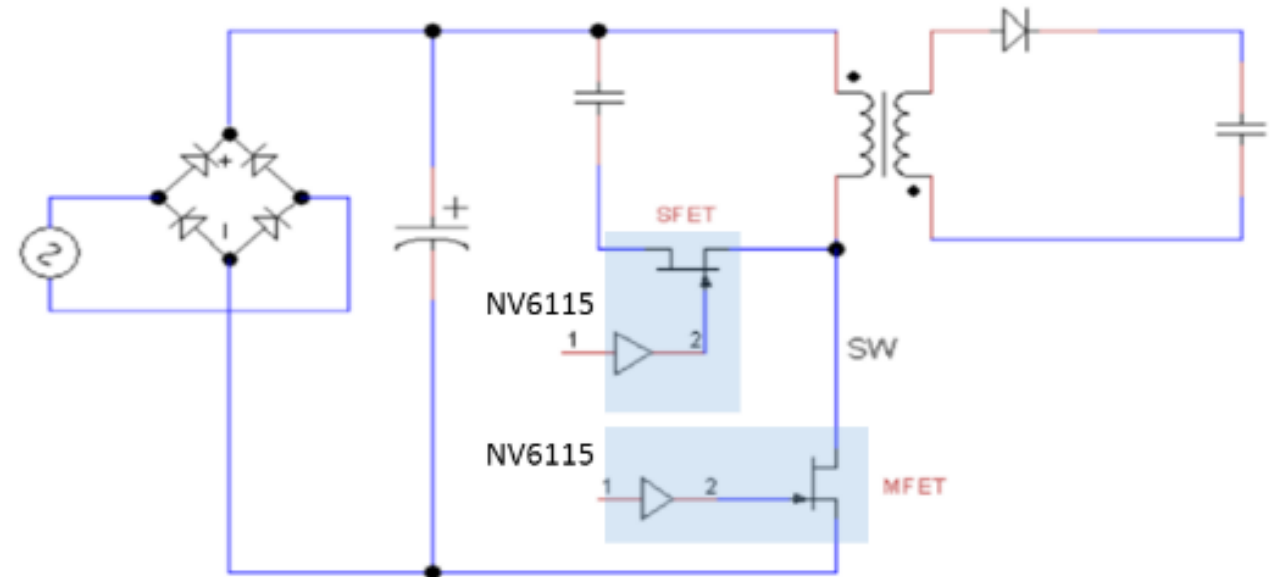- 94.5% efficient at 220V (94.2% at 120V<sub>AC</sub>, 93.1% at 90V<sub>AC</sub>)
- 23.7 W/in<sup>3</sup> density (uncased)
- 15.7mm profile



# 45W CrCM ACF Operation


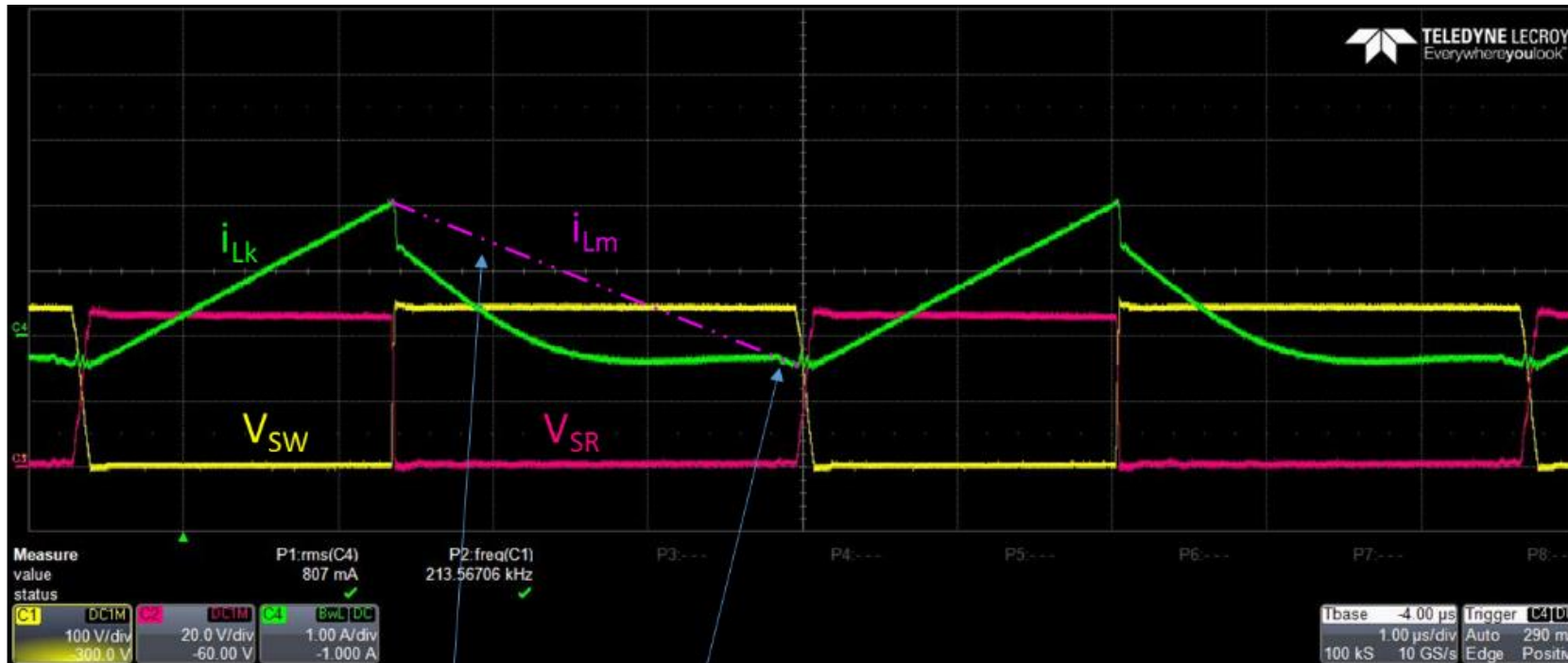


Magnetizing current (drawing)


Inductor current merges with magnetizing current, achieves SR ZCS turn-off

- Switch-node voltage ( $V_{SW}$ ), SR FET voltage ( $V_{SR}$ ), leakage current ( $i_{LK}$ ) and magnetizing current ( $I_{Lm}$ )
- $120V_{AC}$ ,  $0.2A$  load,  $F_{SW} = 210kHz$
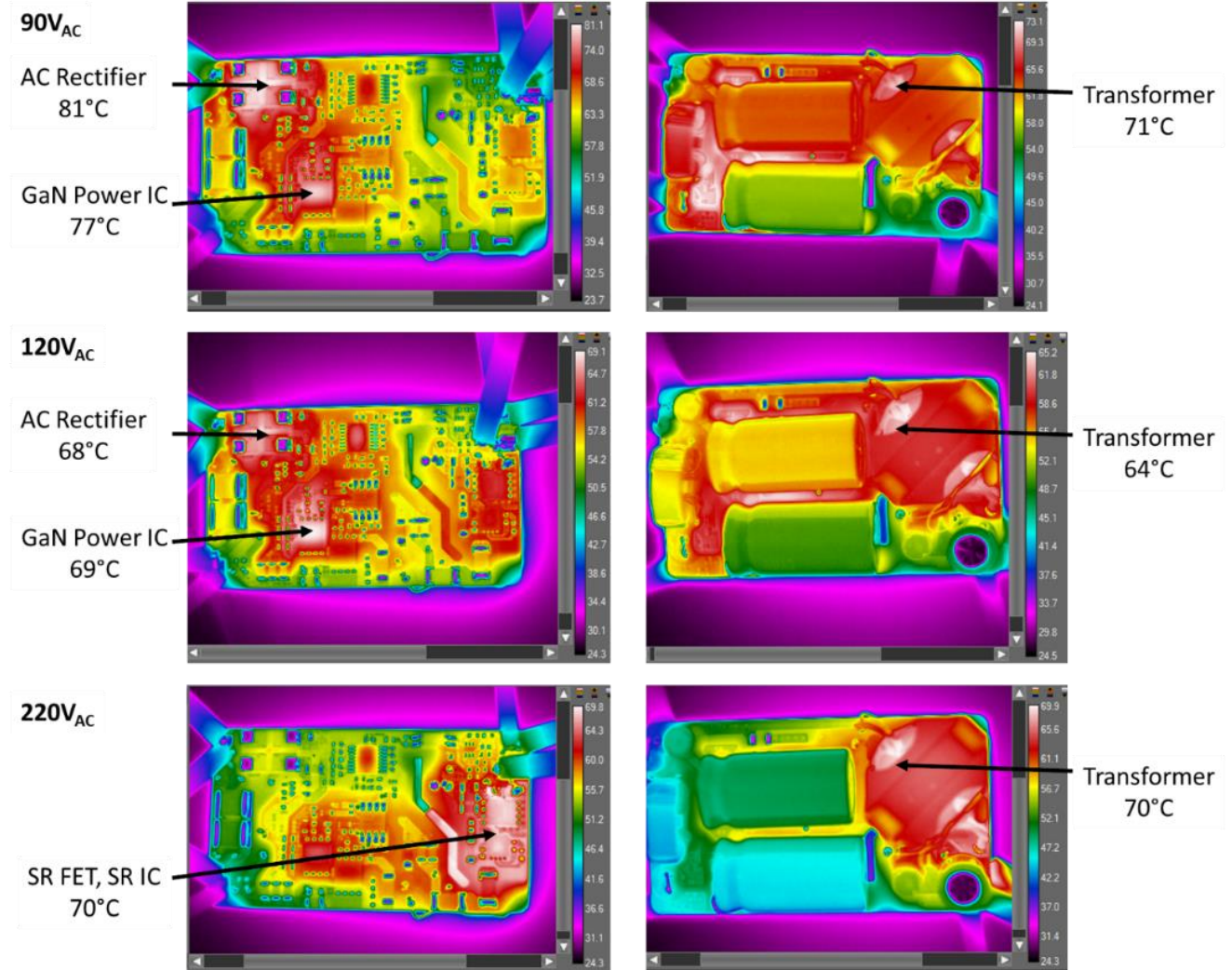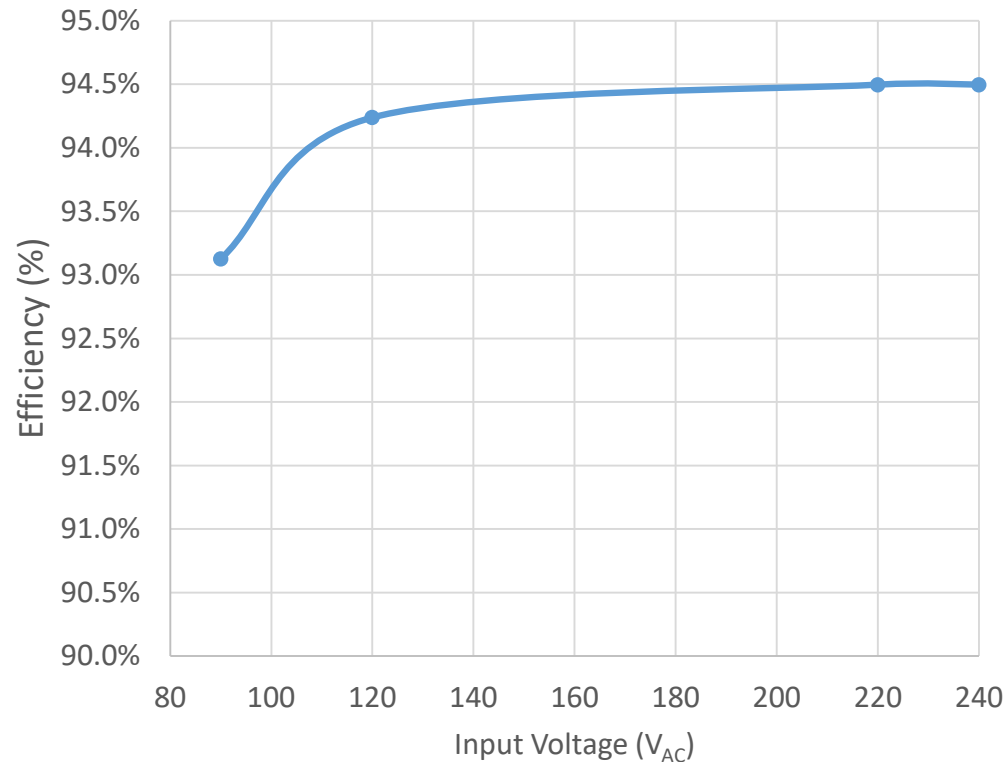
# 45W ACF: High Efficiency, Cool Temperatures


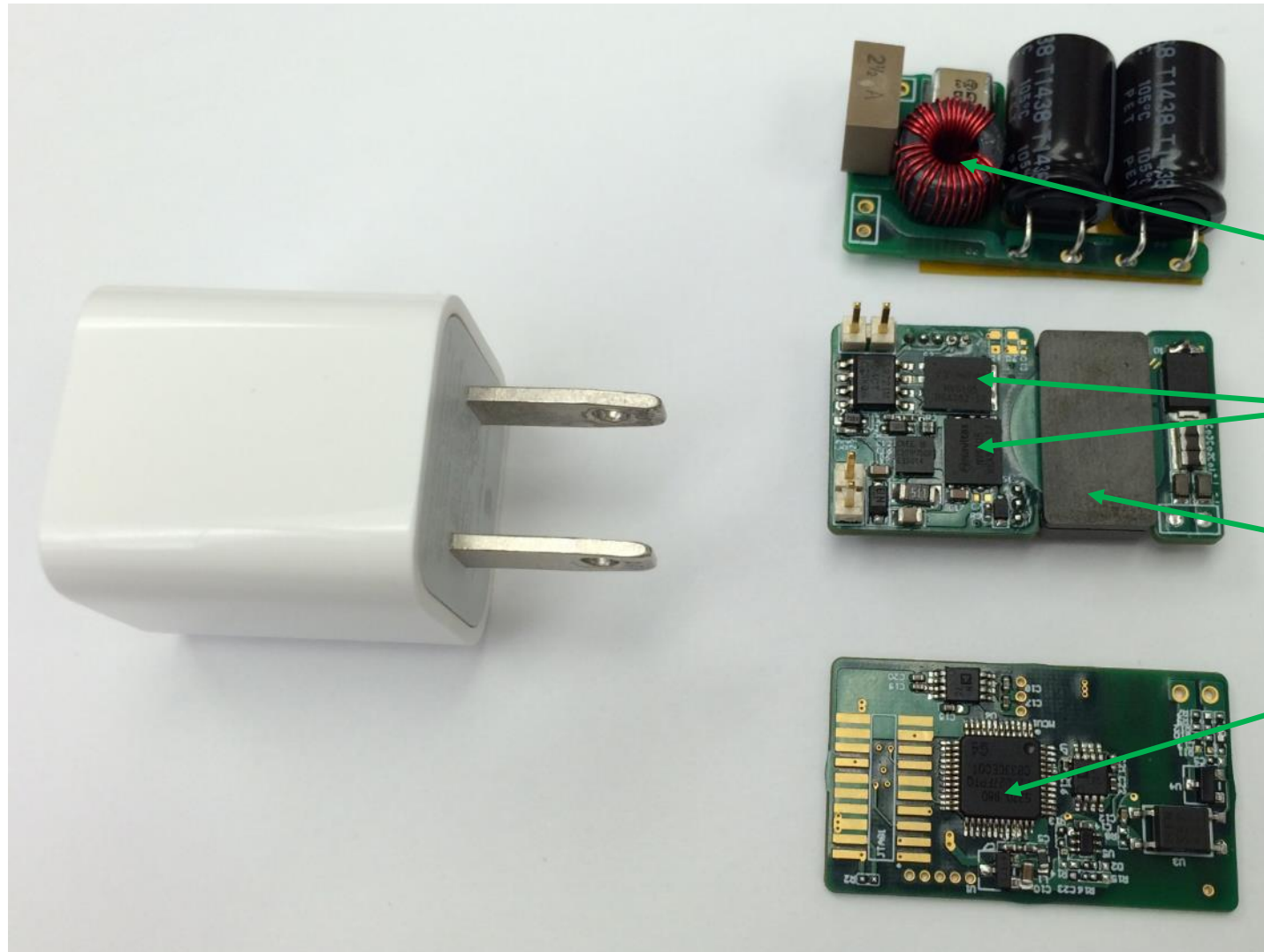
# 1 MHz, 25 W, 17 W/in<sup>3</sup> (cased) ACF (CPES 2016)




- Single-stage EMI
- Navitas GaN Power ICs
- Planar transformer
- DSP (for prototype)




# MHz+ 25 W ACF

$F_{SW}=1.5\text{MHz}$

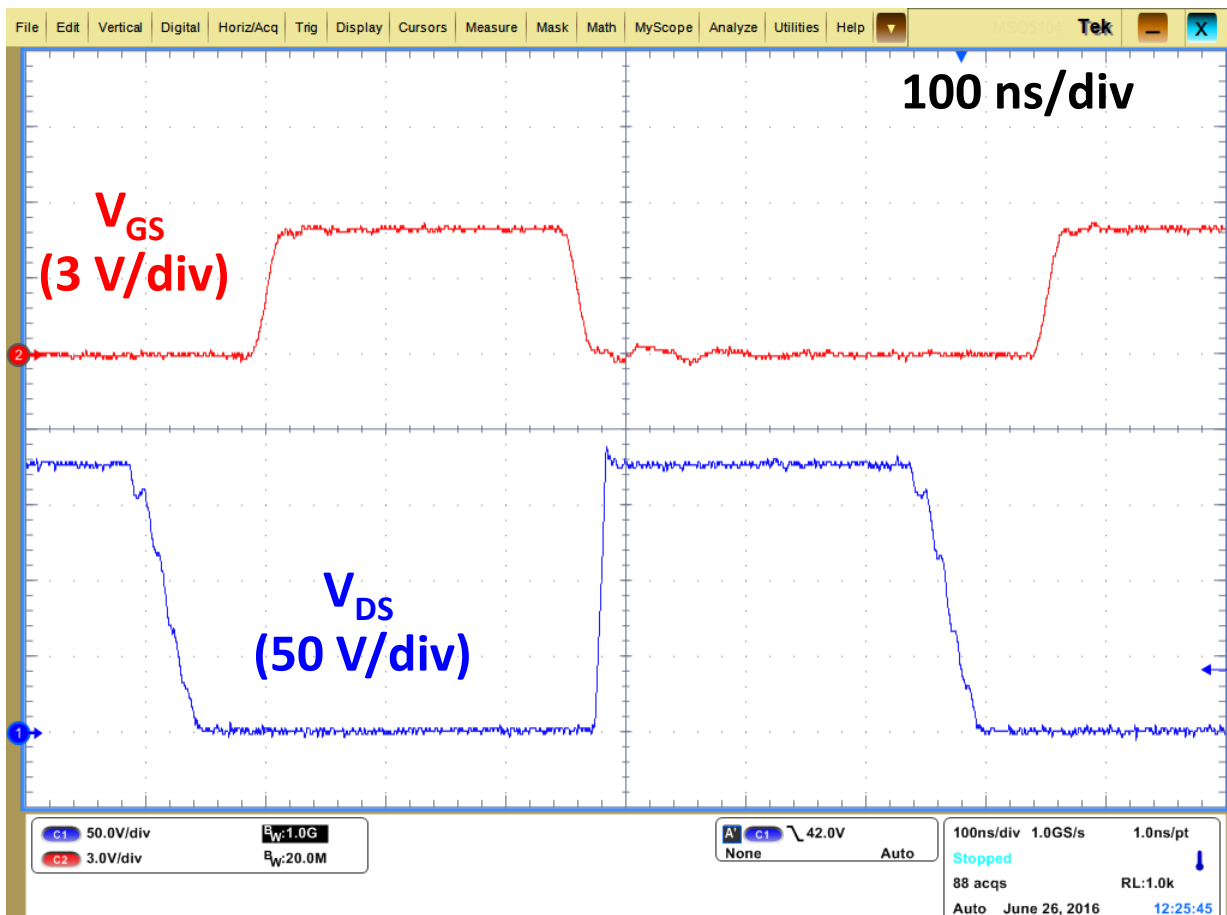

## Efficiency vs. Load

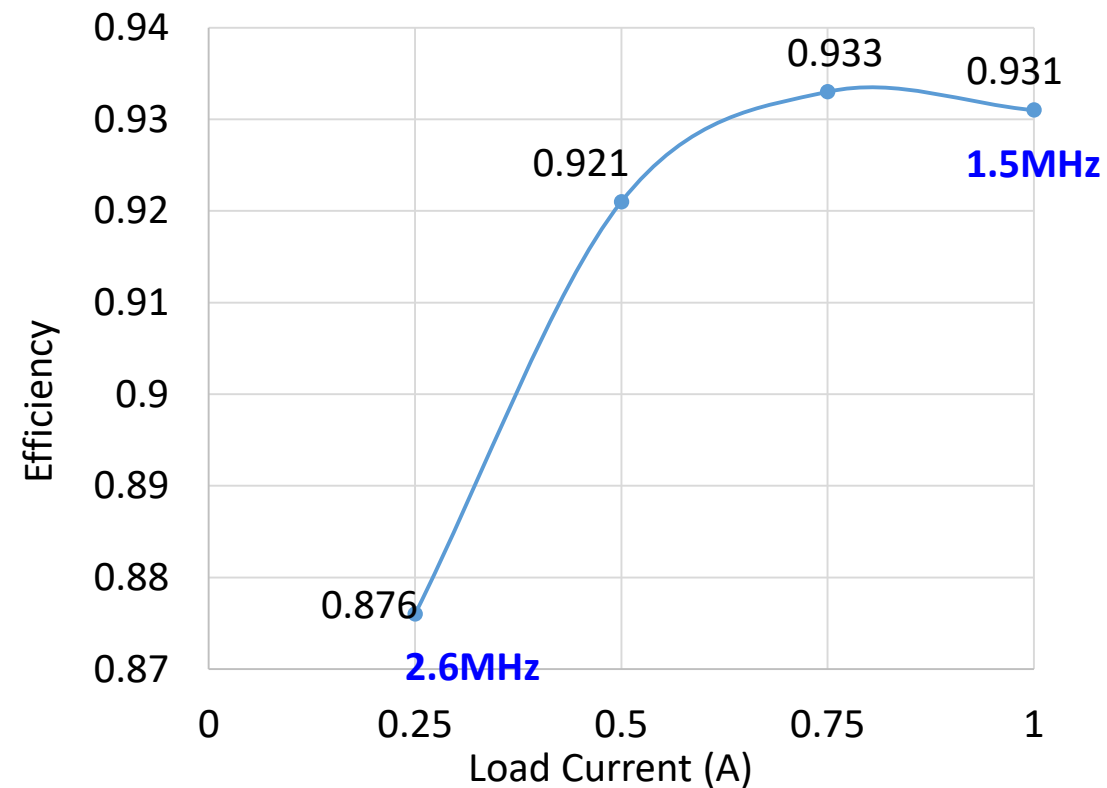

\* Exclude bridge and EMI filter loss

# GaN Power ICs enable Hi-Density Adapters

## 3x Higher Density with 50% Energy Savings


**Existing Si-based  
150W**



**100 kHz  
5-10 W/in<sup>3</sup>  
88%**

**AllGaN™ 2016  
150W**


*2x Higher Density*



**300-500 kHz  
17 W/in<sup>3</sup>  
>93%**

**AllGaN™ 2017  
150W**

*3x Higher Density*



**>1 MHz  
26.5 W/in<sup>3</sup>  
>95%**




Ultra-thin LED TV

All-in-One  
PCs




Next-Gen  
Gaming Consoles

# 150W AC-19V

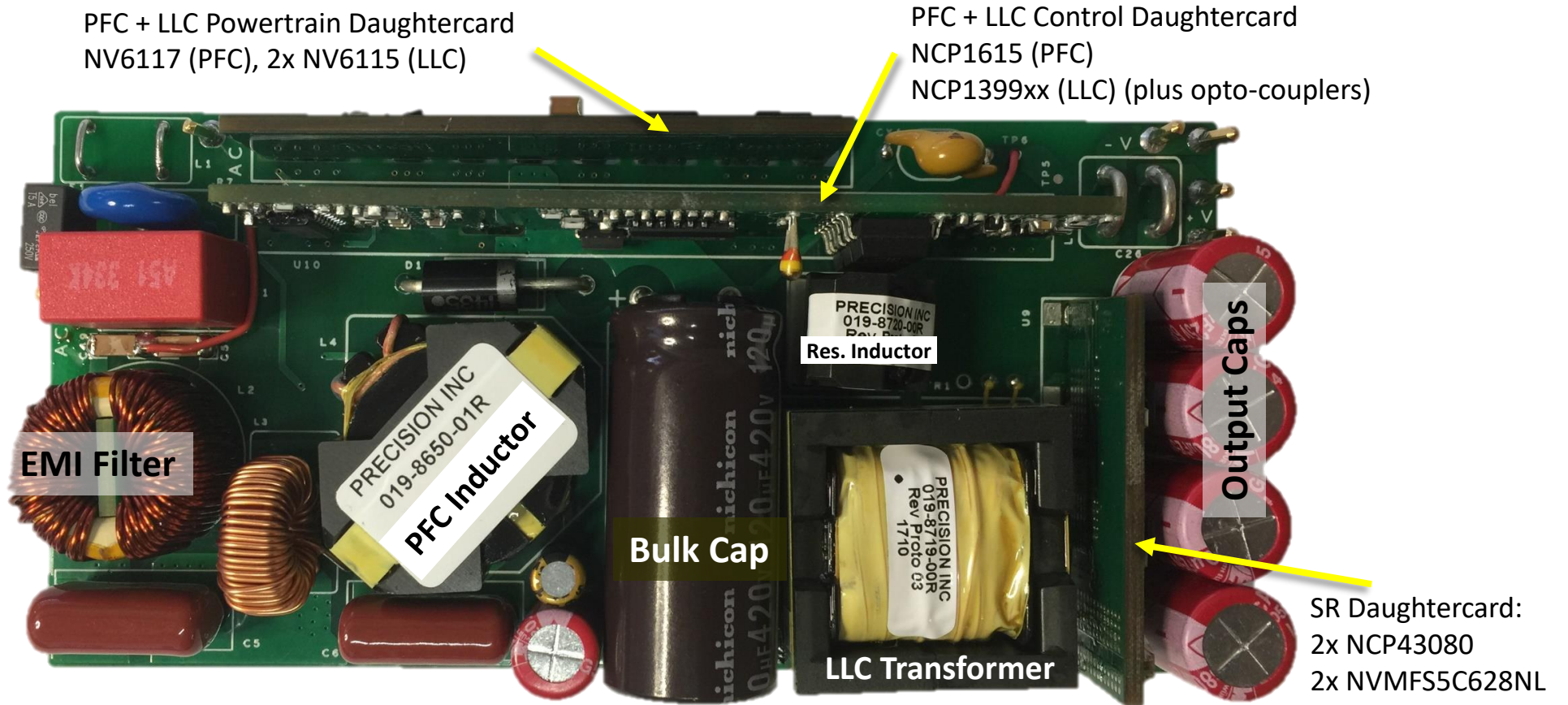

# Schematics (Complete Board)

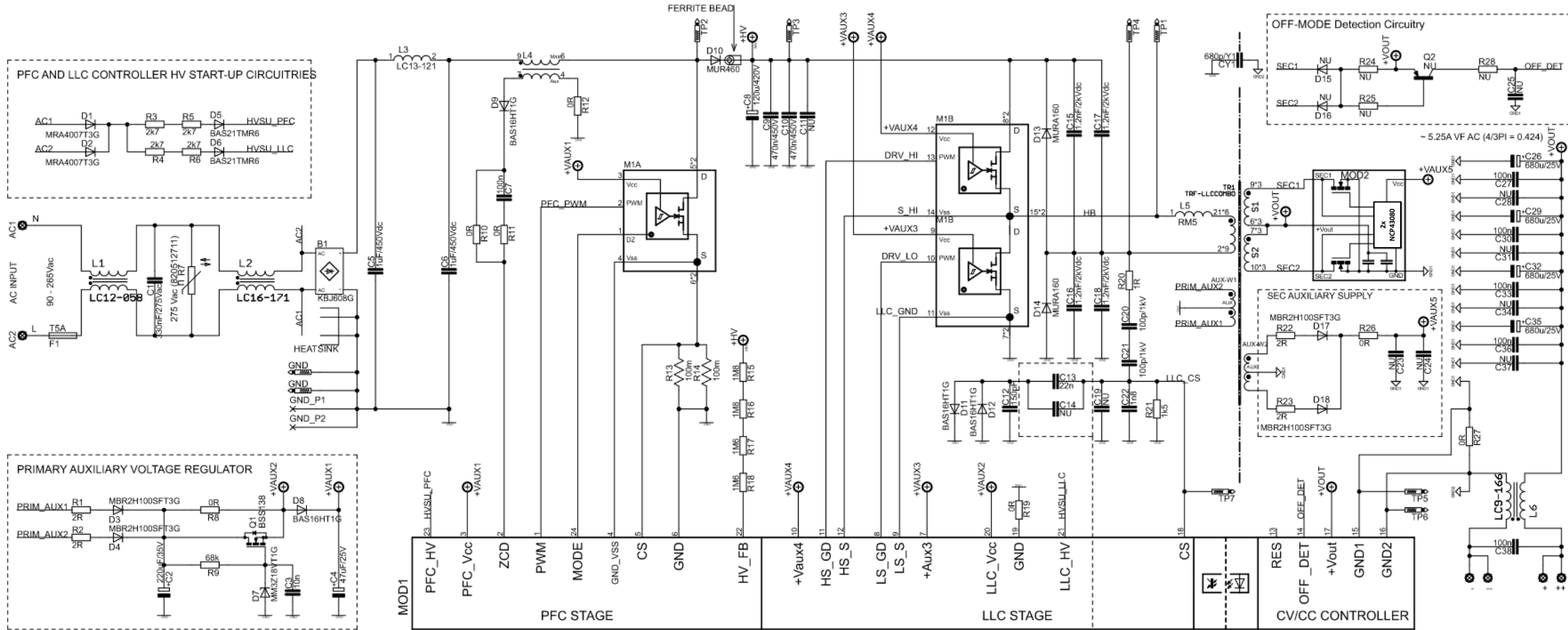



Integrated Xformer	22nF
Discrete Xformer	8.2nF

POWER PART ONLY

# Schematics (Complete Board)


## HV Start-Up + X2 Cap Discharge
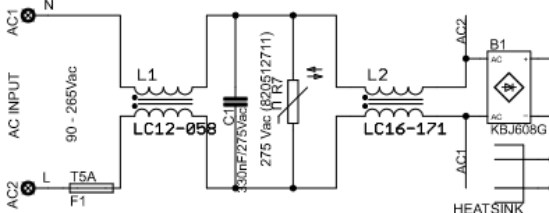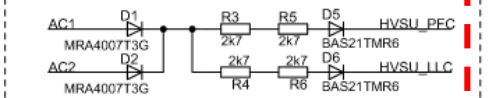
### PFC AND LLC CONTROLLER HV START-UP CIRCUITRIES



### EMI + Rectifier

### Aux V<sub>CC</sub> Supply

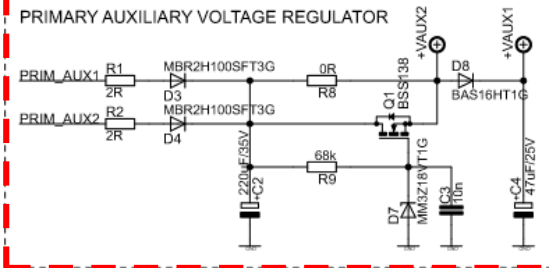


## EMI

## Boost PFC

## LLC

## SR + Output Reg

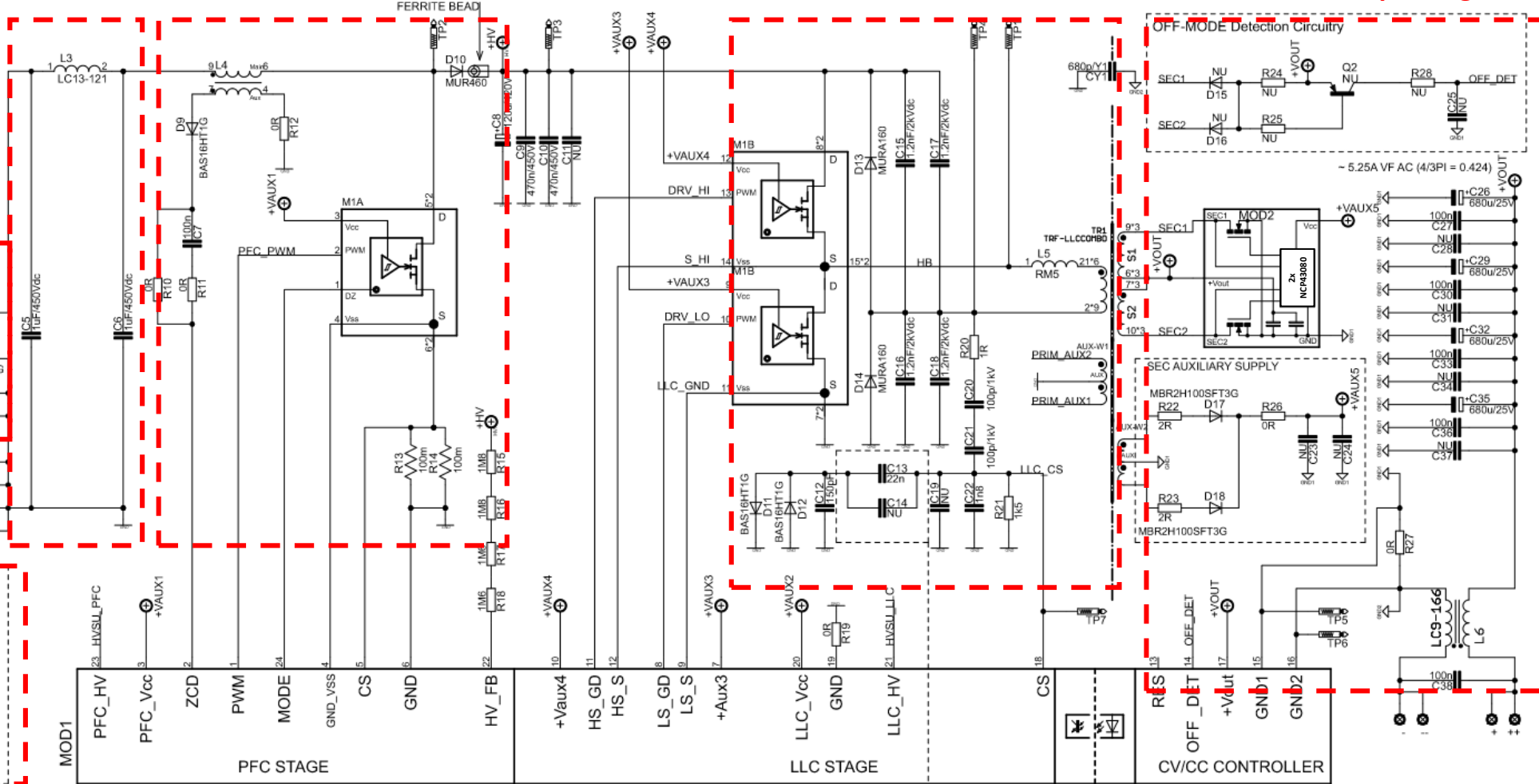


Integrated Xformer	22nF
Discrete Xformer	8.2nF


POWER PART ONLY
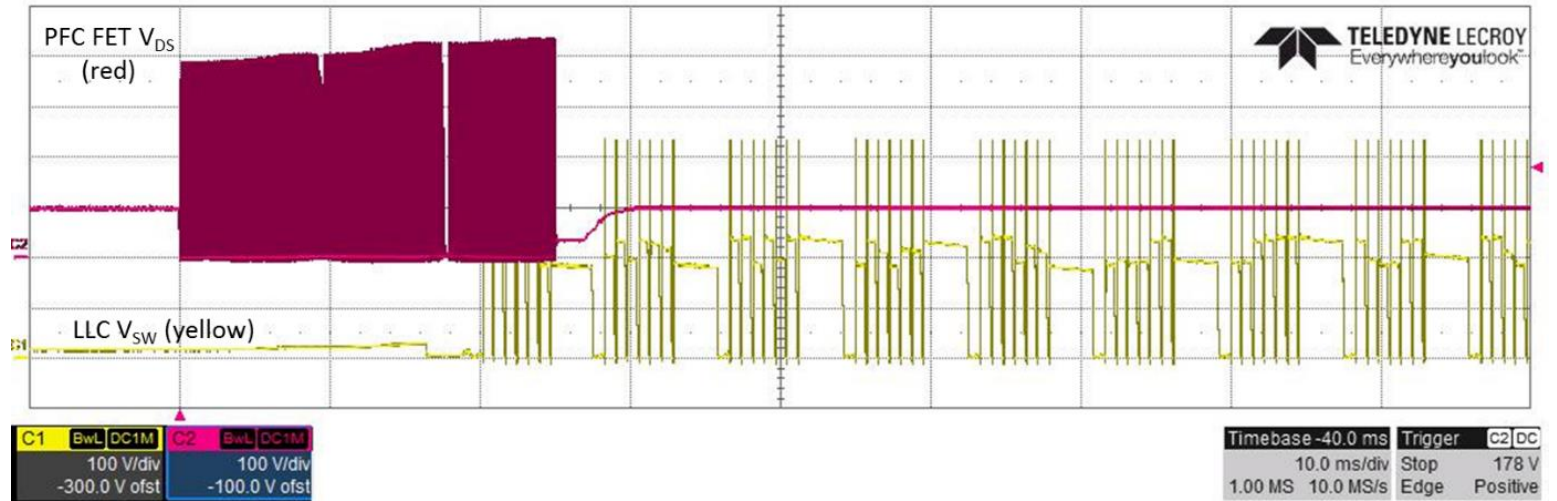
# PFC Waveforms

PFC FET  $V_{DS}$ , LLC  $V_{SW}$  at start-up




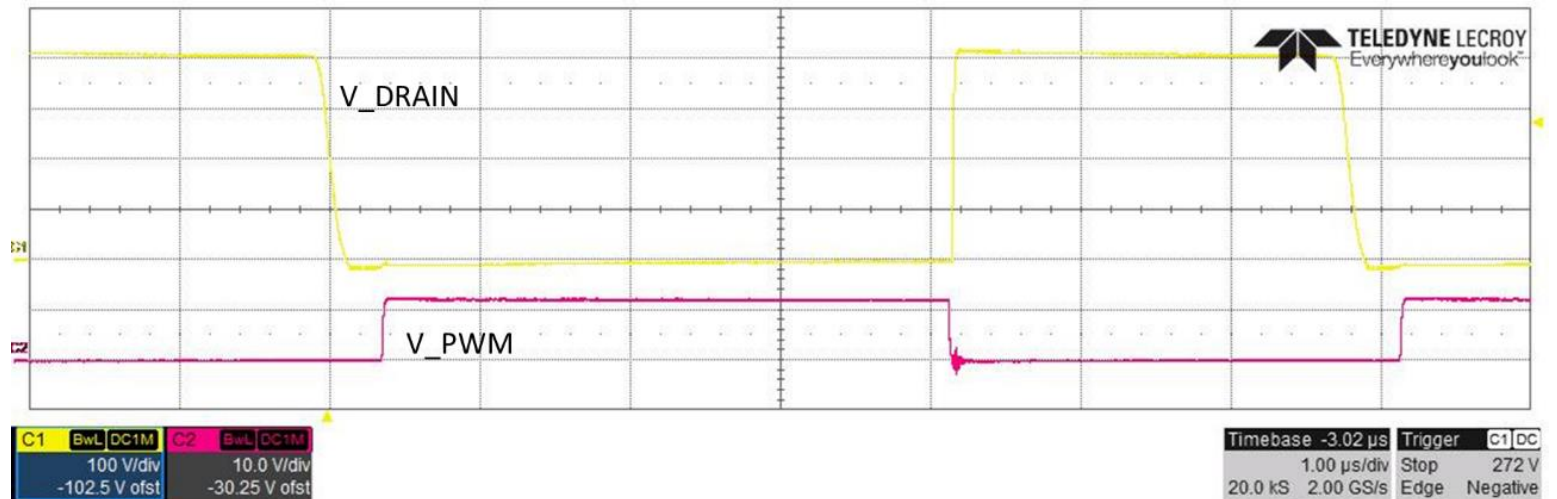PFC switching (zoom), 220V<sub>AC</sub>, 150W



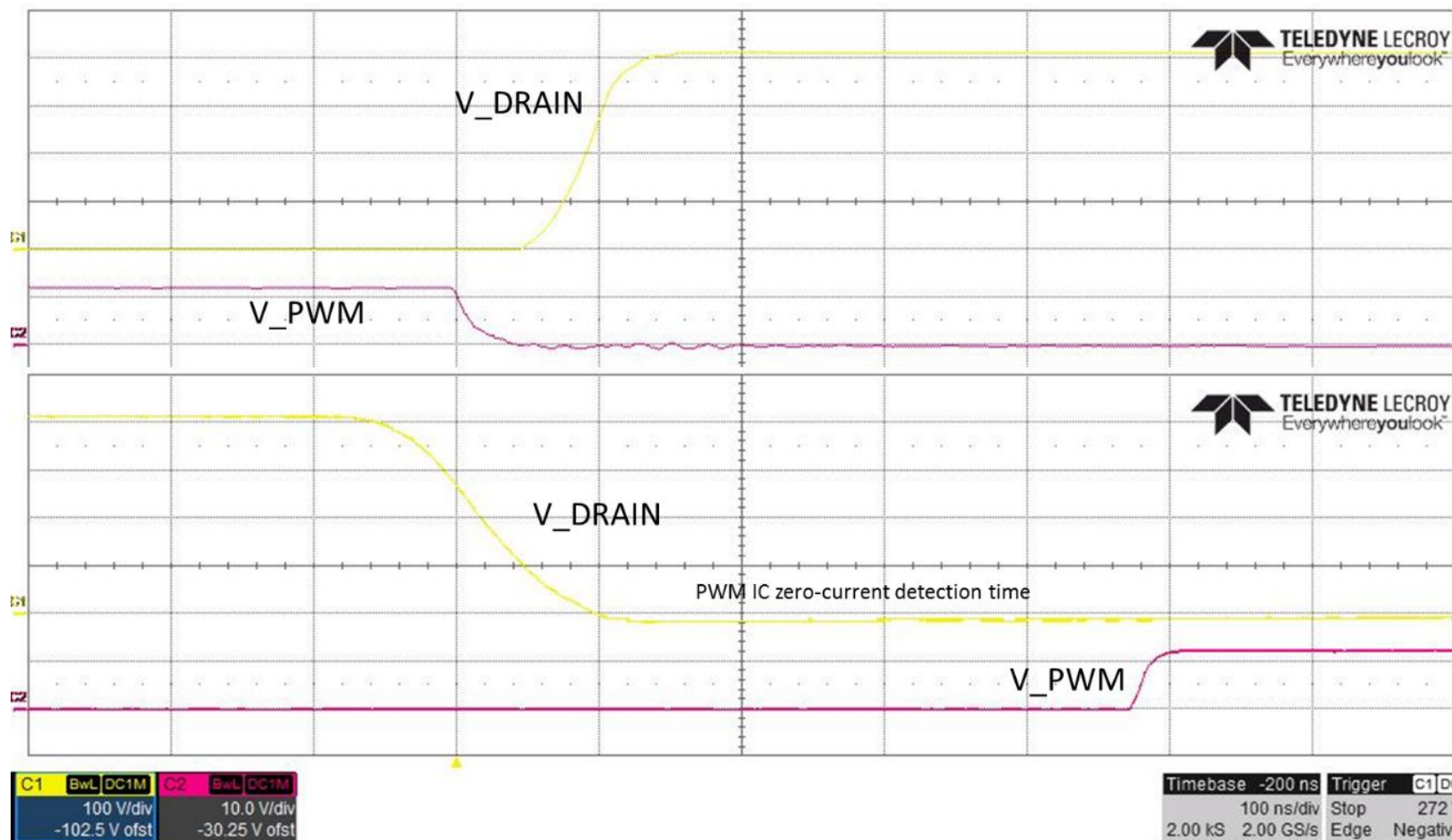
# PFC Waveforms


PFC switching (zoom), 220V<sub>AC</sub>, 150W




# LLC Waveforms

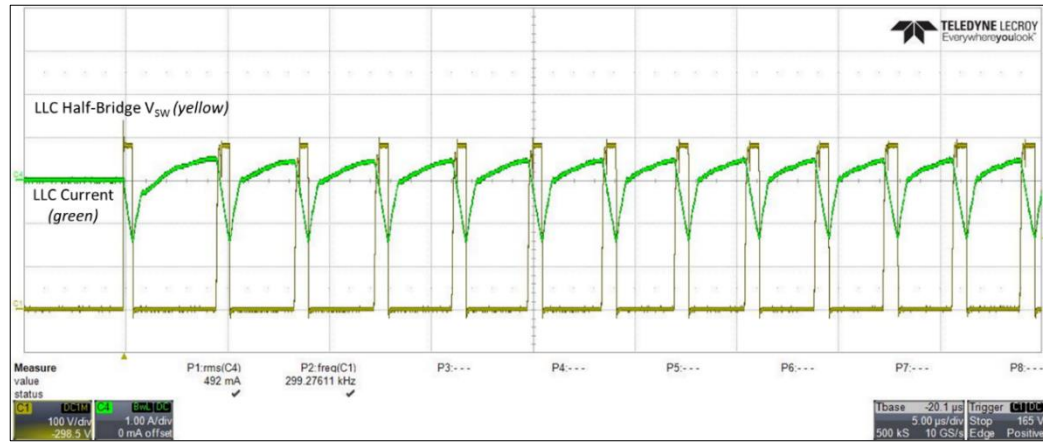

LLC  $V_{sw}$ , open load,  $19V_{OUT}$

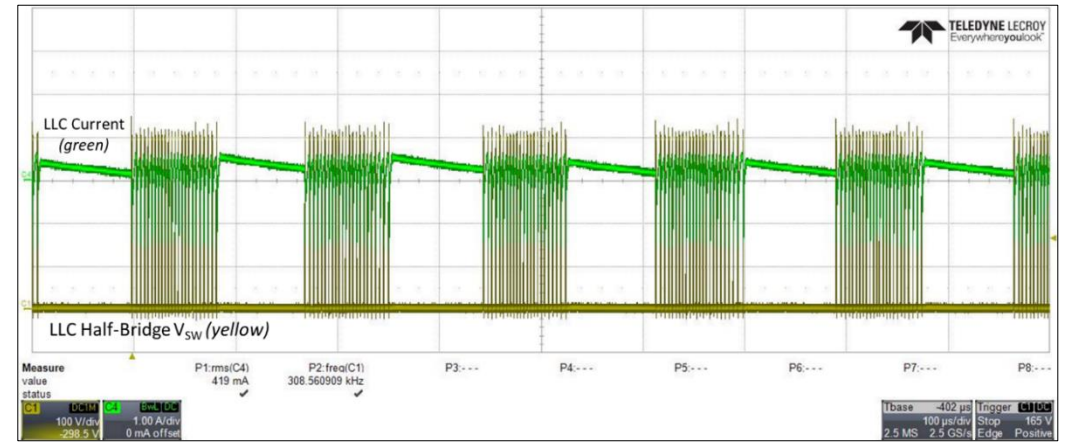


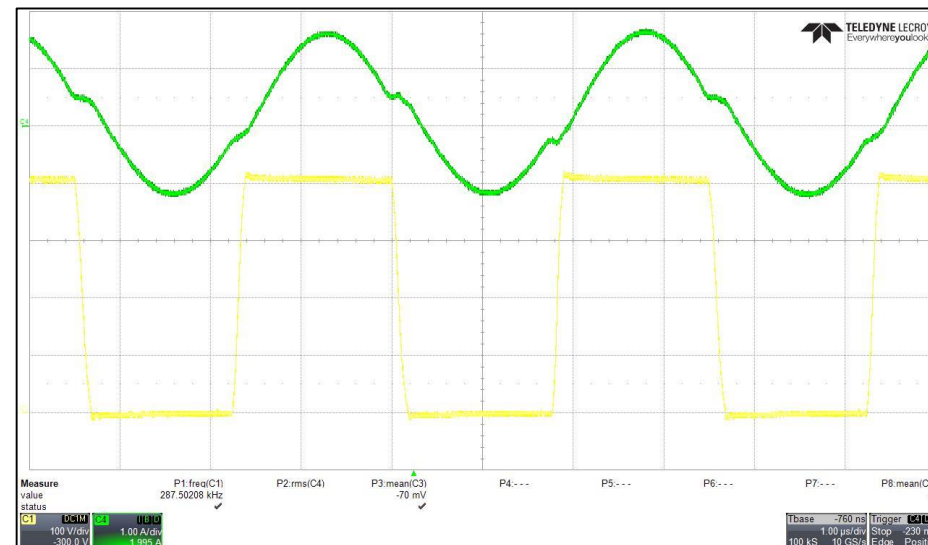
LLC  $V_{sw}$ , skip-mode,  $19V_{OUT}$ , 1A






LLC  $V_{sw}$ ,  $I_L$ ,  $19V_{OUT}$ , 8A



# 150W: Running Cool

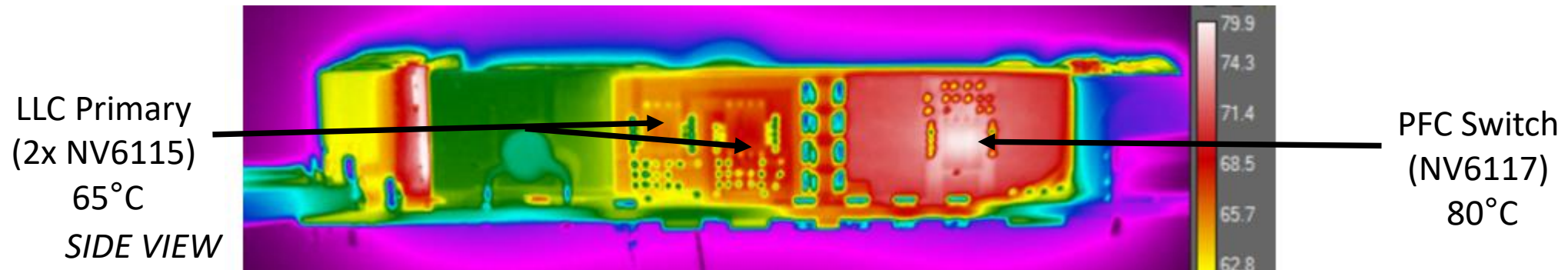
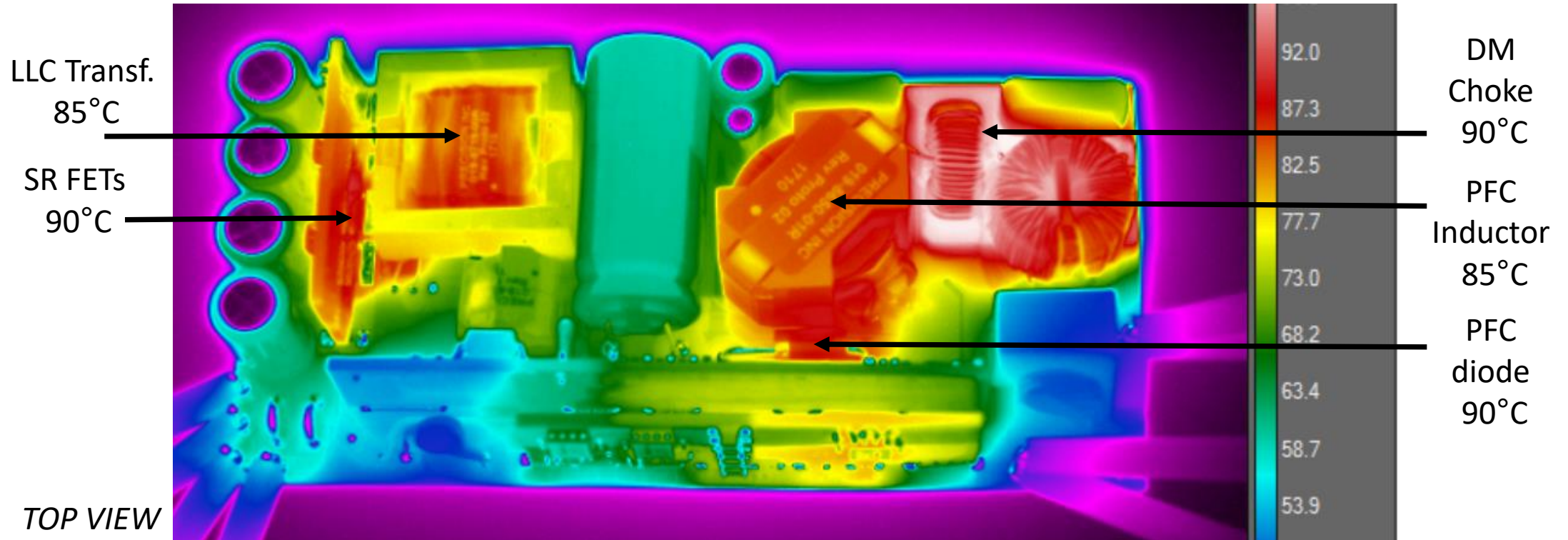


# 150W AC-19V, ~300 kHz

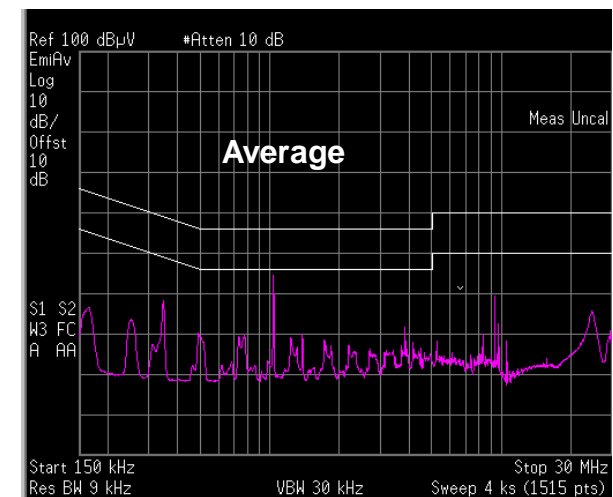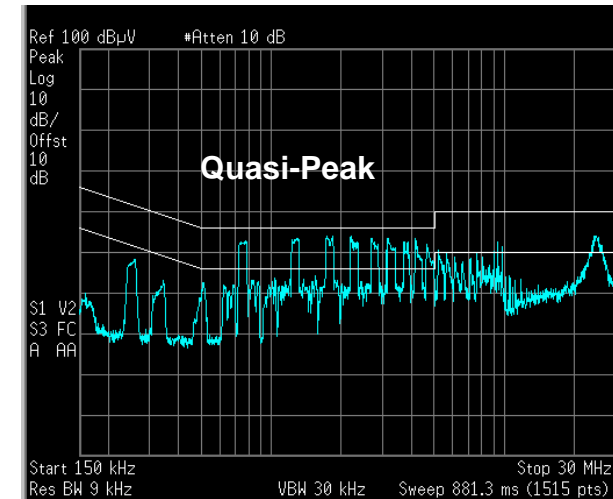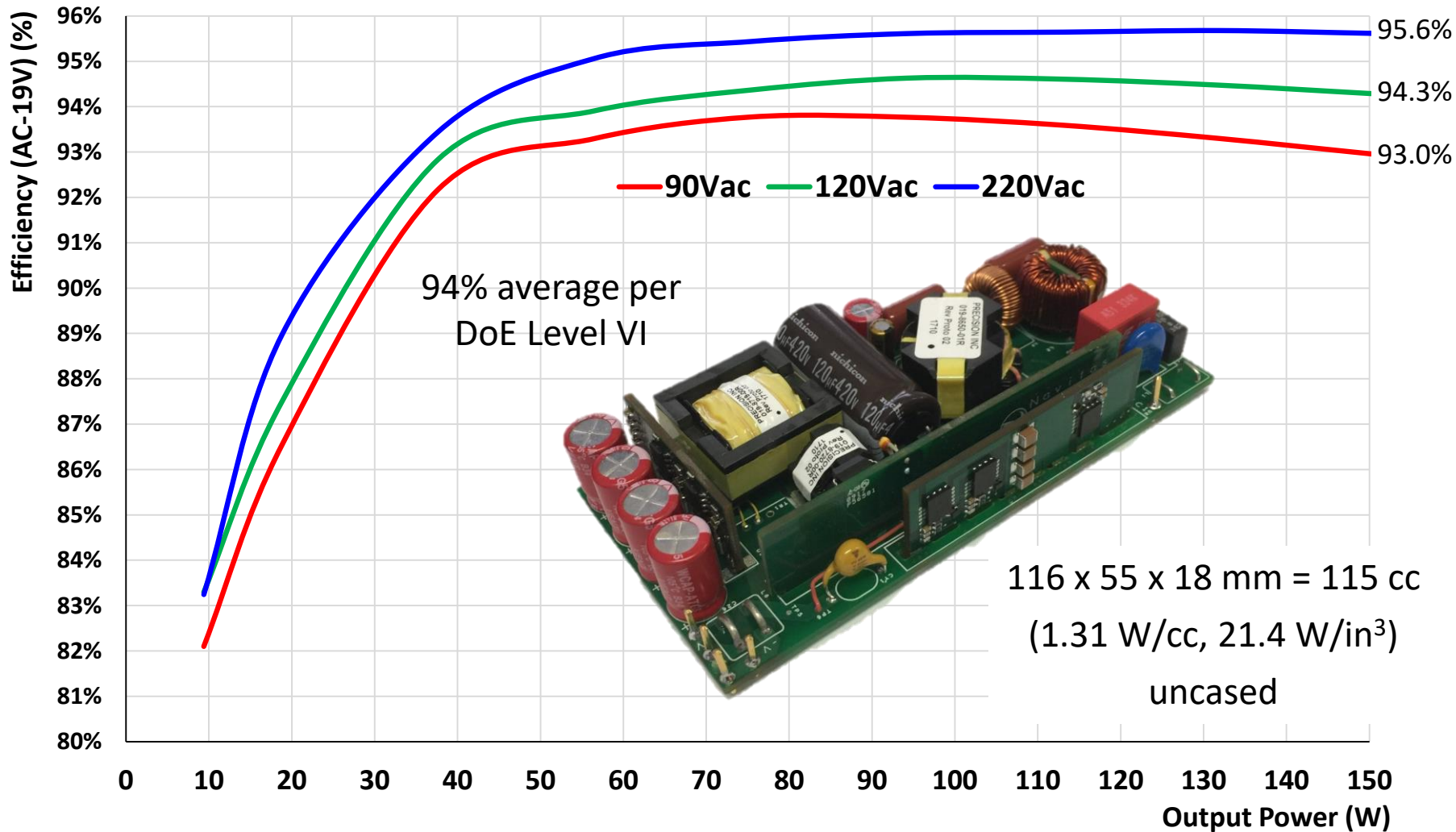


# 150W, 19V: GaN Power IC vs. Si

Part#	Technology	V	Pack	$R_{DS(ON)}$ (typ. m $\Omega$ )	$Q_G$ (typ. nC)	$C_{OSS(er)}$ (typ. pF)	$R \times Q_G$ (m $\Omega$ .nC)	$R \times C_{OSS(er)}$ (m $\Omega$ .pF)
<a href="#">STL34N65M5</a>	Si FET	650	8x8	99	62.5	63	6,187	6,237
<a href="#">IPL60R199CP</a>	Si FET	600	8x8	180	32	69	5,760	12,420
<a href="#">IPL60R299CP</a>	Si FET	600	8x8	270	22	46	5,940	12,420
NV6115	GaN Power IC	650	5x6	160	2.5	30	400	4,800
NV6117	GaN Power IC	650	5x6	110	4	45	440	4,950
<b>GaN Benefit</b>							<b>14x</b>	<b>1.5-2.5x</b>

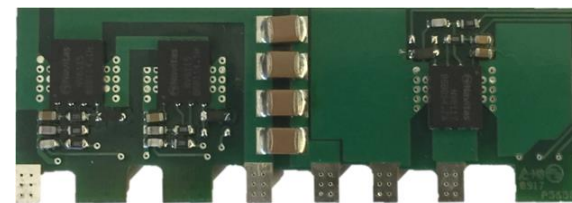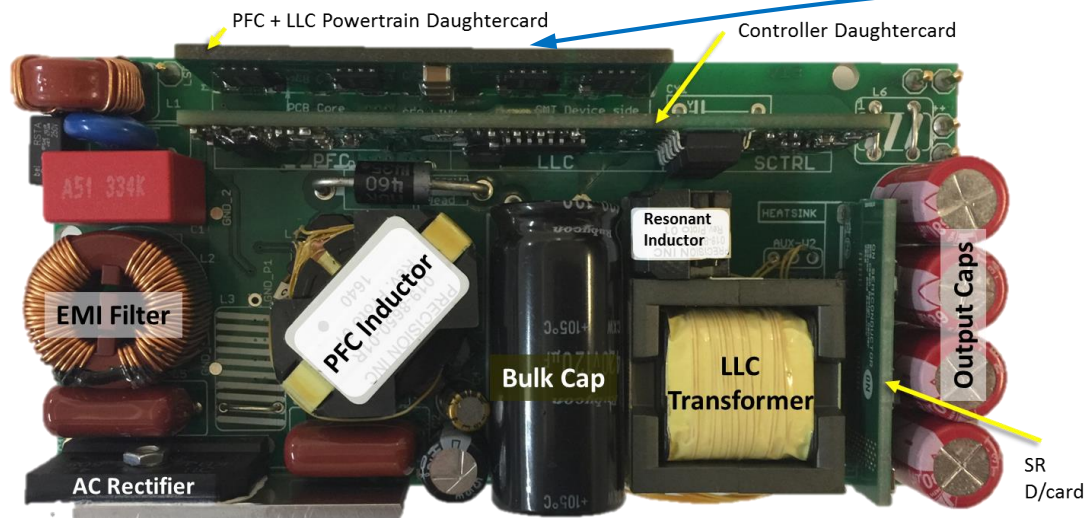


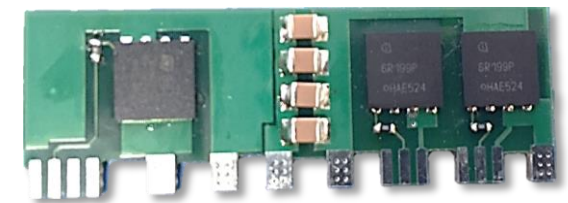Navitas GaN Power ICs (5x6mm QFN)  
PFC = 1x NV6117, LLC = 2x NV6115




Si FETs (8x8mm QFN)  
a) PFC = 1x IPL60R299CP, LLC = 2x IPL60R299CP  
b) PFC = 1x IPL60R199CP, LLC = 2x IPL60R299CP
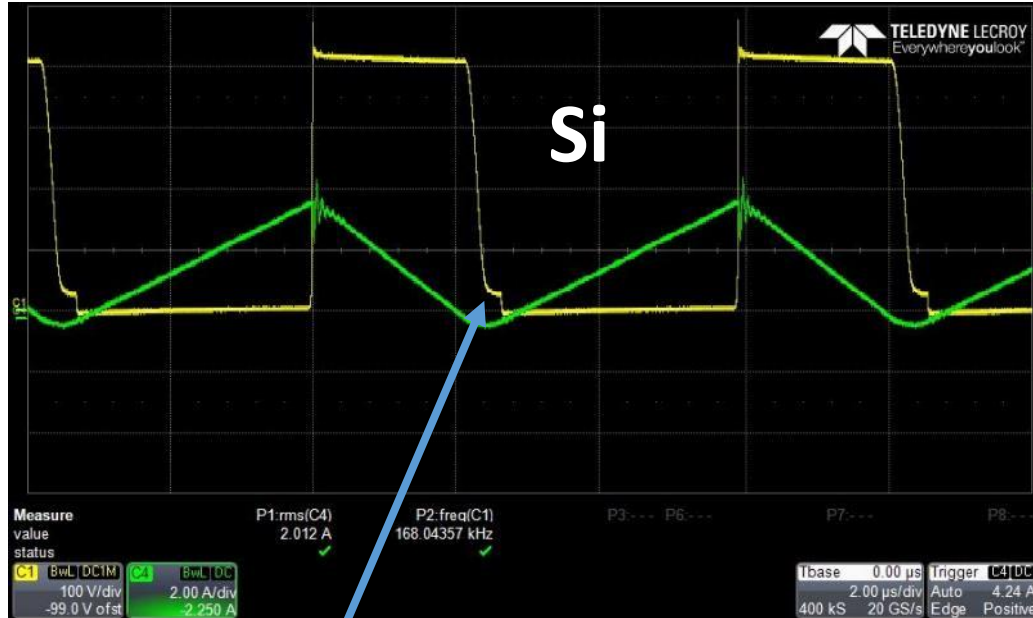
# Si Starts Hard Switching as Frequency Increases



120V<sub>AC</sub>, Si CP partial hard-switching (~200kHz)

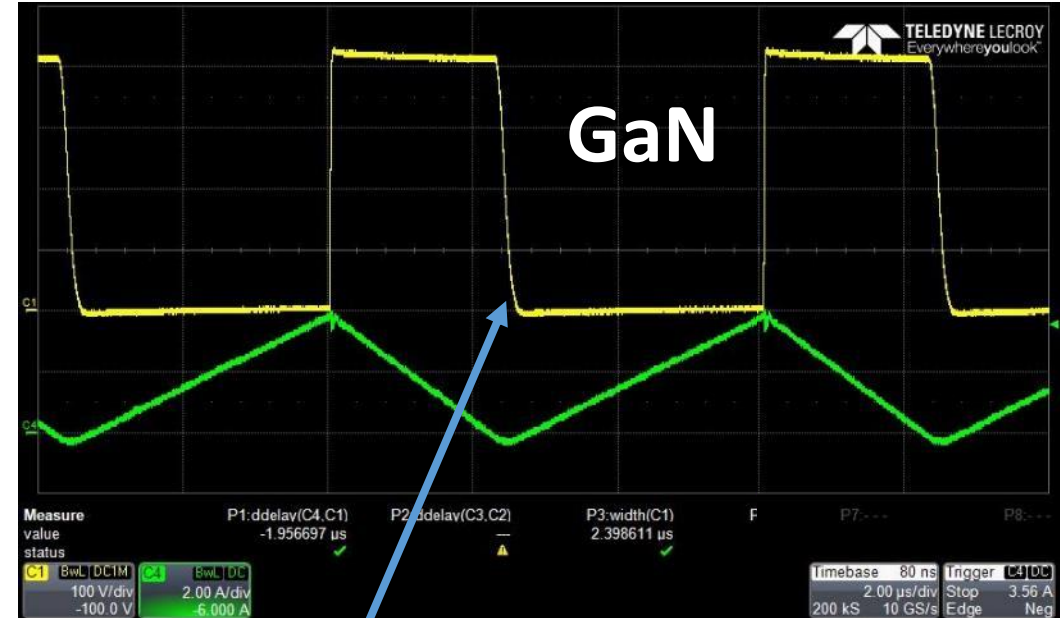- Voltage spikes
- Partial hard-switching (loss)



120V<sub>AC</sub>, GaN clean ZVS waveforms (~200kHz)

- No voltage spikes / overshoot
- Clean ZVS turn-on transition
- Minimize deadtime for low reverse conduction loss

# GaN vs. Si



## High Power Density and High Switching Frequency Adapter


- Ultra high-power density up to 22 W/ in<sup>3</sup>
- Very high Efficiency up to 96 % with GaN Power FETs
- The smallest dimensions 4.6 x 1.96 x 0.78 in
- Performance ensured by NCP1399, NCP1615, NCP43080
- Up to 94 % Efficiency with Silicon Super-Junction MOSFETs

### Typical applications

- High Power Laptop Adaptors, Power supplies, Power chargers
- 150 W Output Power @ 19 V with ~8.5 A current limit



Efficiency [%] vs. Output power [W]

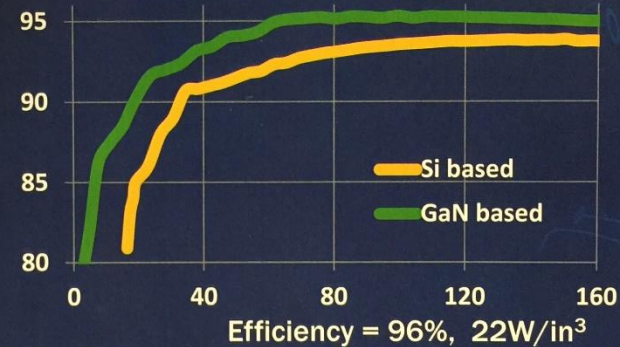

Efficiency = 94%, 13W/in<sup>3</sup>




### Higher switching frequency enables:


- Up to 40% volume reduction, Power Density almost doubled
- Compact design / balanced price
- Keep high efficiency

# MHz 150W Totem-pole + LLC (CPES 2016)



PFC

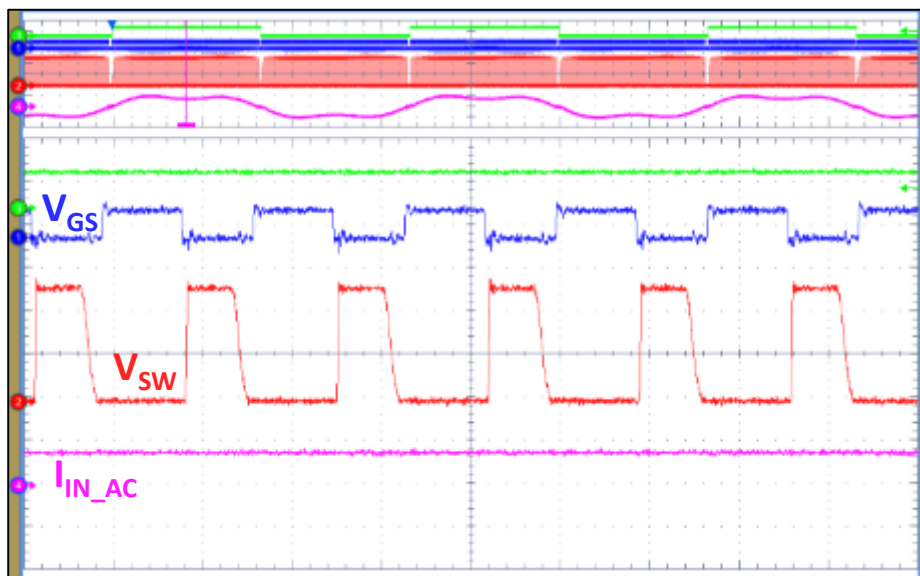

LLC

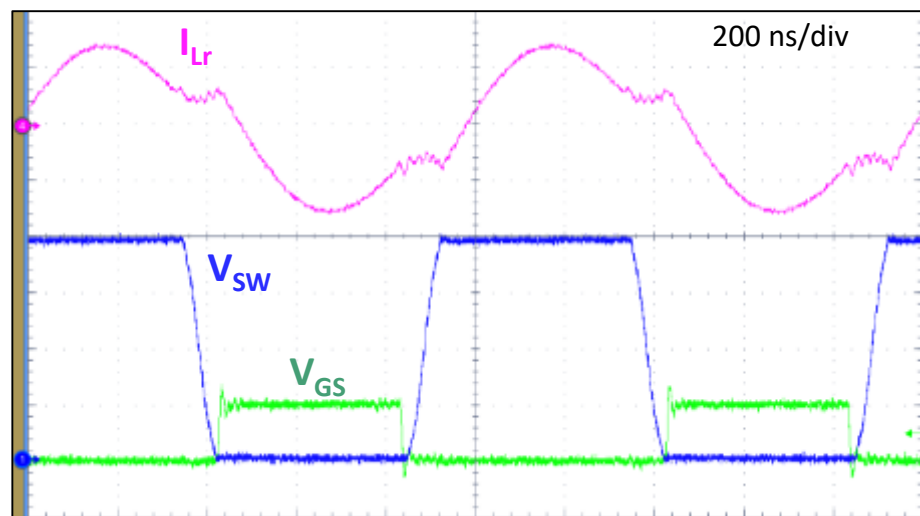

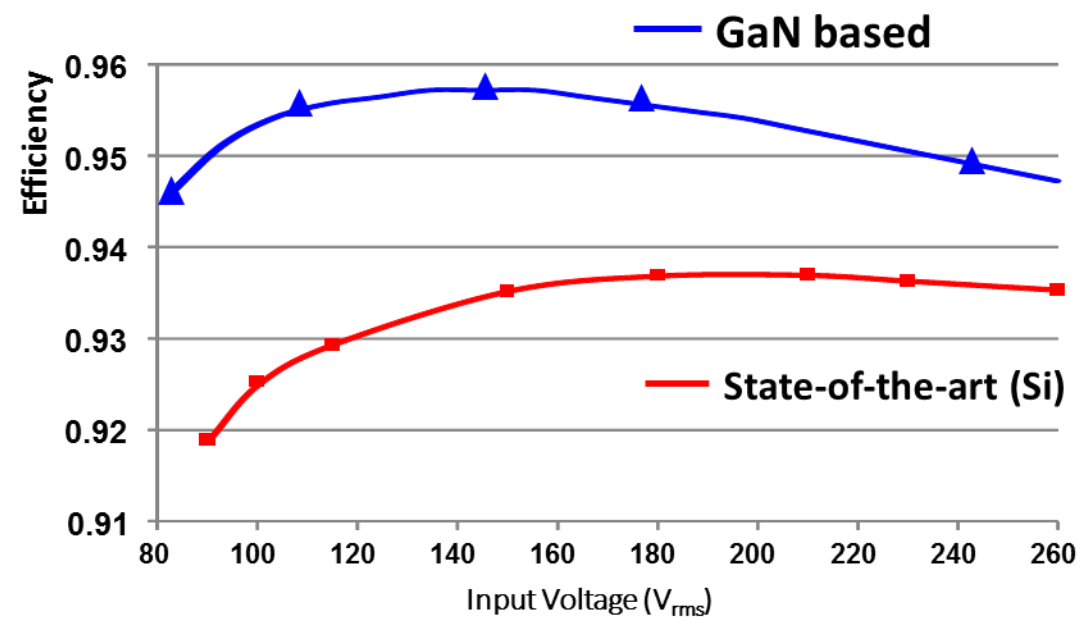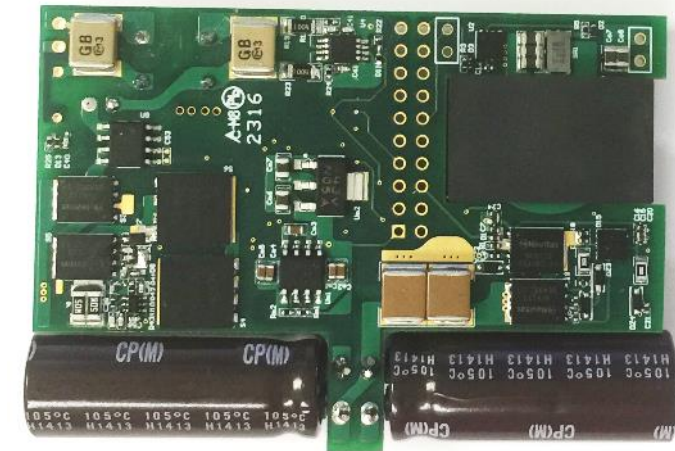GaN-based  
Power Density  
=  $35 \text{ W/in}^3$   
(uncased)



# Pop Quiz! How do we shrink our power supplies?

- A. Select the right ZVS topology
- B. Increase switching frequency
- C. Select the right magnetic material
- D. Select the right GaN Power IC
- E. Increase efficiency
- F. **All of the above**
- G. None of the above...  
...use hard-switching topologies and Silicon switching < 100kHz.